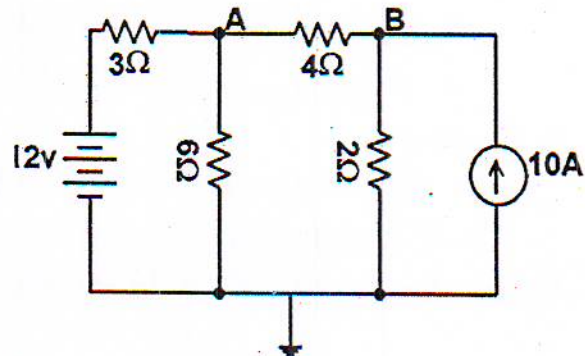




**Answer (4) Questions Only**  
**(each question of 15 mark )**

**Q1 :** Using Thevenin's theorem ,calculate the current flowing through the ( $4\Omega$ ) resister shown in figure 1

Figure 1.



**Q2:**

Find the power dissipated in ( $6\Omega$ ) resistance of the circuit shown in figure 2 applying Kirchhoff's voltage & current laws.


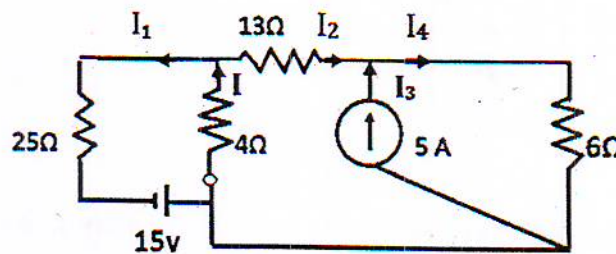


figure2

**Q3:**

- Explain the relation between current and voltage in the basic component of electrical circuit.
- Find the equivalent resistance of the circuit given in figure 3 between A and B , between E and F

Fig 3

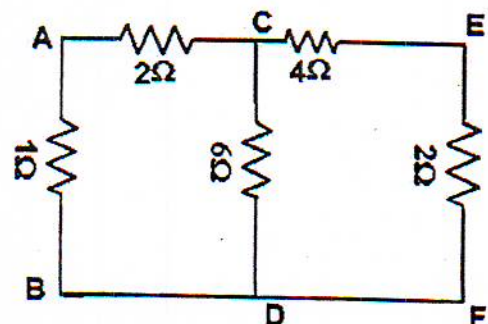




**Q4:**

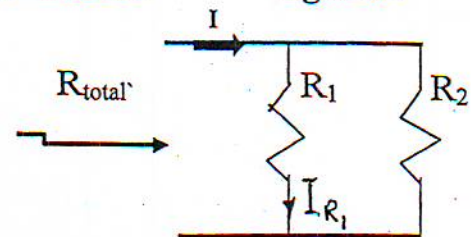A. Copper coil has a wire diameter of (1 mm) and a length of (1 km).  
Connected in parallel to another coil made of Aluminum its diameter is (1mm). Find the length of the Aluminum wire if : figure 4

- $R_{total} = 9.738 \Omega$
- $\rho_{Copper} = 0.0159 \mu\Omega\text{-m}$
- $\rho_{Aluminum} = 0.0254 \mu\Omega\text{-m}$ .



B. Explain :

- 1- Ohm's law, 1st law of Kirchhoff.
- 2- The elements of the electrical circuits.

C. How the current flows in the electrical circuit?

**Q5:** Prove that the current in resistance ( $R_1$ ) shown in figure 4 above is:

$$I_{R_1} = I \times \frac{R_2}{R_1 + R_2}$$

**Q6:** Find the current in  $17\Omega$  resistor of the network shown in figure 5 by using

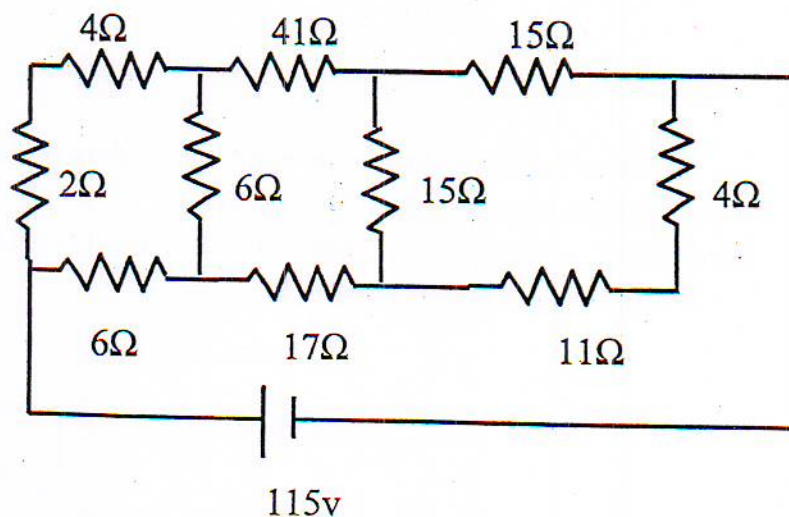


Figure 5

*Good luck*