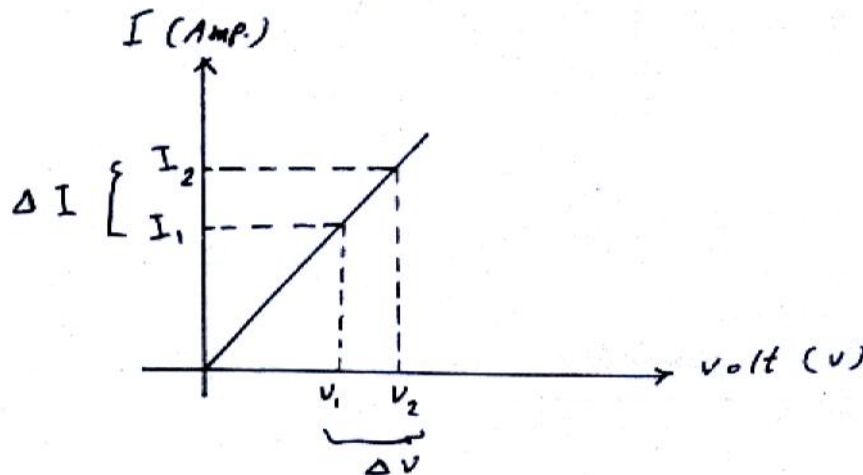


Ohm's Law :- Ohm's law states that the voltages (V) across a resistor (R) is directly proportional to the current (I) flowing through the resistor .





$$\text{Slop} = \frac{\Delta I}{\Delta V} = \frac{1}{R}$$

$$\frac{V}{I} = \text{constant} = R$$

$R = \frac{V}{I}$	$\Omega ; \Rightarrow V = I \cdot R ; I = \frac{V}{R}$
-------------------	--

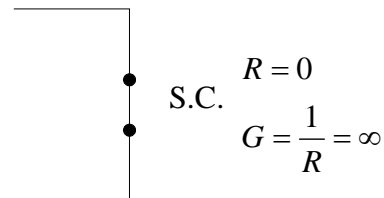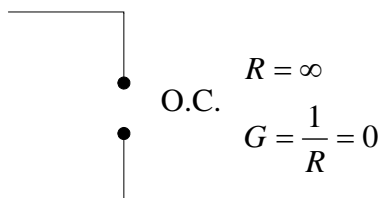- ❖ The resistance of short circuit element is approaching to zero.
- ❖ The resistance of open circuit is approaching to infinity.



Hence $G = \frac{1}{R} = \frac{I}{V}$ Siemens (S) or mhos (\sim) .


Electrical Energy (W) :-

$$\because P = \frac{W}{t} \Rightarrow W = P . t \quad \text{KWh}$$

$$\begin{aligned} W &= P . t \\ &= (V . I) . t \\ &= (I^2 . R) . t \\ &= \left(\frac{V^2}{R} \right) . t \end{aligned}$$

$$\text{Energy in KWh (W)} = \frac{\text{Power(P)} \times \text{time(t)}}{1000}$$

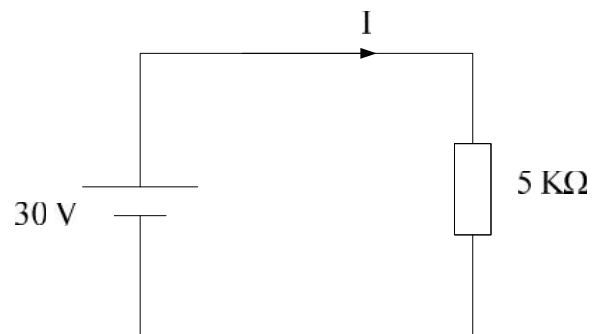Example : For the following circuit diagram , calculate the conductance and the power ?



Solution :

$$I = \frac{V}{R} = \frac{30}{5 \times 10^3} = 6mA$$

$$G = \frac{1}{R} = \frac{1}{5 \times 10^3} = 0.2m^{\wedge}$$


$$P = I.V = (6 \times 10^{-3}) \times 30 = 180mW$$

$$\text{or } P = I^2 . R = (6 \times 10^{-3}) \times (5 \times 10^3) = 180mW$$

$$\text{or } P = V^2 . G = (30)^2 \times (0.2 \times 10^{-3}) = 180mW$$

$$\text{or } P = \frac{V^2}{R} = \frac{(30)^2}{(0.2 \times 10^{-3})} = 180mW$$

Efficiency (η) :-

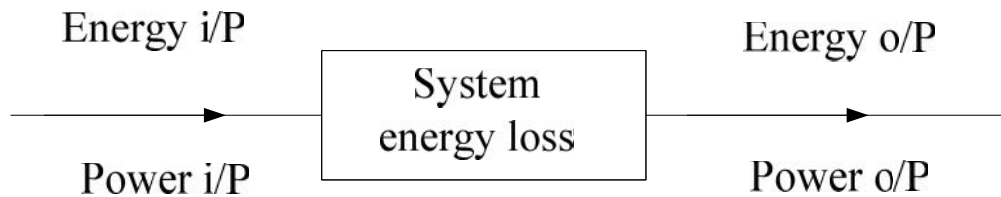

$$W_{i/p} = W_{o/p} + W_{loss}$$

$$\frac{W_{i/p}}{t} = \frac{W_{o/p}}{t} + \frac{W_{loss}}{t}$$

$$P_{i/p} = P_{o/p} + P_{loss}$$

$$\text{Efficiency (} \eta \text{)} = \frac{\text{Output power}}{\text{Input power}} \times 100\%$$

$$y = \frac{P_o}{P_i} \times 100\%$$

$$y = \frac{W_o}{W_i} \times 100\%$$



$$y_T = y_1 \times y_2 \times y_3 \times \dots \times y_n$$

Example: A 2 hp motor operates at an efficiency of 75 %, what is the power input in Watt, if the input current is (9.05) A, calculate also the input voltage?

Solution:

$$1 \text{ hours power (hp)} = 746 \text{ Watt}$$

$$y = \frac{P_o}{P_i} \times 100\%$$

$$0.75 = \frac{2 \times 746}{P_i} \Rightarrow P_i = \frac{1492}{0.75} = 1989.33W$$

$$P = E.I \Rightarrow E = \frac{P}{I} = \frac{1989.33}{9.05} = 219.82 \cong 220V$$

Example: What is the energy in KWh of using the following loads:-

- a) 1200 W toaster for 30 min.
- b) Six 50 W bulbs for 4 h.
- c) 400 W washing machines for 45 min.
- d) 4800 W electric clothes dryer for 20 min.

Solution :

$$W = \frac{P(W) \times t(h)}{1000}$$


$$W = \frac{1200 \times \left(\frac{30}{60}\right) + 6 \times 50 \times 4 + 400 \times \left(\frac{45}{60}\right) + 4800 \times \left(\frac{20}{60}\right)}{1000}$$

$$= \frac{600 + 1200 + 300 + 1600}{1000} = \frac{3700}{1000} = 3.7 KWh$$


D.C. Sources:-

The d.c. sources can be classified to:-

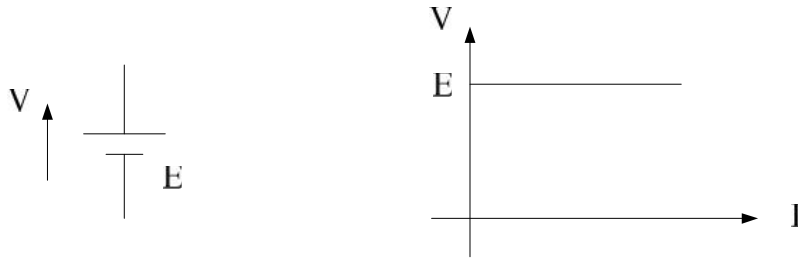- 1- Batteries .
 - Voltage
 - Amper - hours
- 2- generators .
- 3- Photo cells .
- 4- Rectifiers .



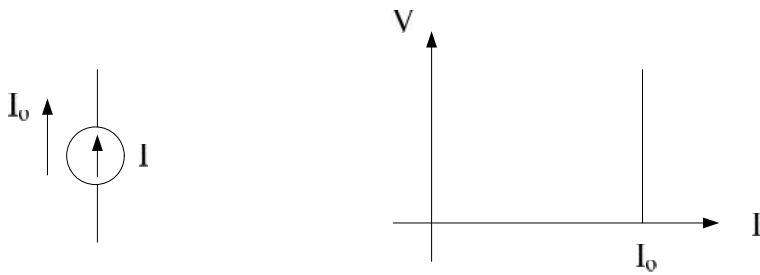$V = E = \text{constant voltage element}$




$I = I_0 = \text{constant current element}$

مصدر الفولتية يولد تيار و فولتية و لكن الفولتية تكون ثابتة .

مصدر التيار يولد تيار و فولتية و لكن التيار يكون ثابت .

Series Circuit :-

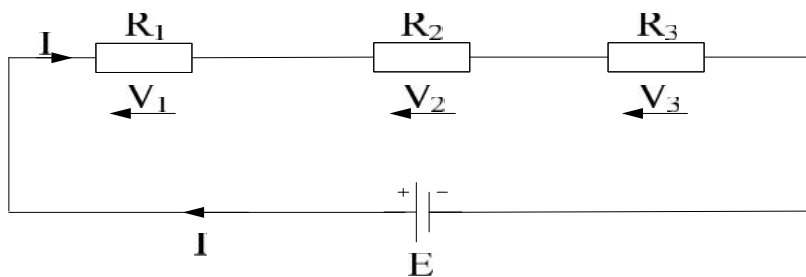

$$V_1 = I.R_1$$

$$V_2 = I.R_2$$

$$V_3 = I.R_3$$

$$E - V_1 - V_2 - V_3 = 0 \Rightarrow E = V_1 + V_2 + V_3$$

$$\therefore E = I.R_1 + I.R_2 + I.R_3$$

$$E = I.[R_1 + R_2 + R_3] = I.R_T$$



The current in the series circuit is the same through each series element &

$$R_T = R_1 + R_2 + R_3 + \text{-----} + R_N$$


$$I = \frac{E}{R_T} = \frac{V_1}{R_1} = \frac{V_2}{R_2} = \frac{V_3}{R_3}$$

$$P_t = P_1 + P_2 + P_3 = E.I$$

Voltage Source in Series:-

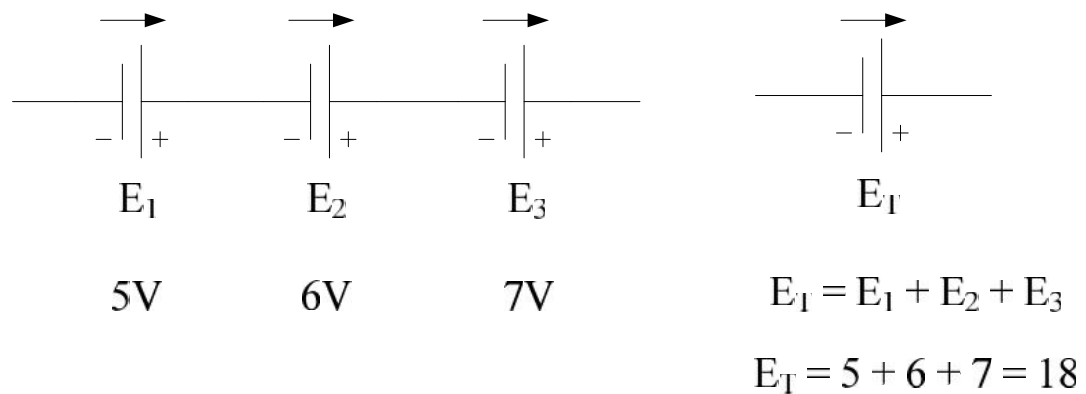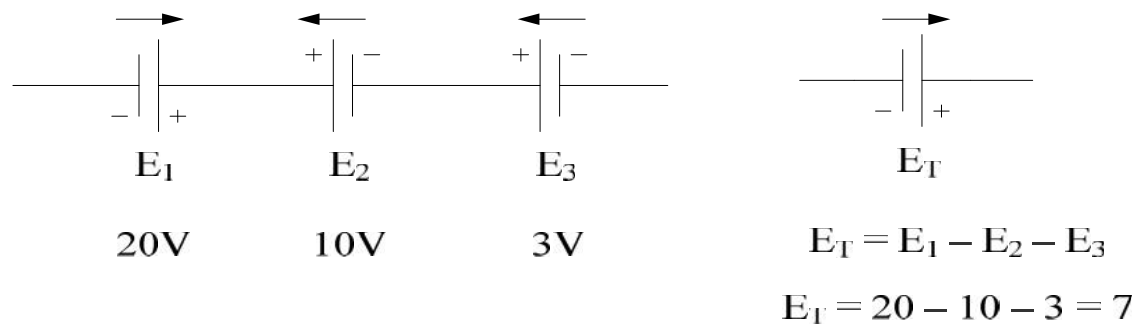

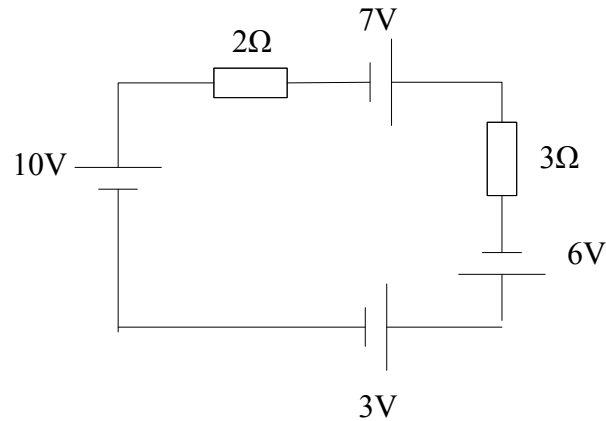Example: Find the current for the following circuit diagram?



Solution:

$$E_T = 10 + 7 + 6 - 3 = 20 \text{ V}$$

$$R_T = 2 + 3 = 5 \text{ } \Omega$$


$$I = I_T = \frac{E_T}{R_T} = \frac{20}{5} = 4 \text{ A}$$

Kirchoff's voltage law (K.V.L.):-

The algebraic sum of all voltages around any closed path is zero.

$$\sum_{m=1}^m V_m = 0$$

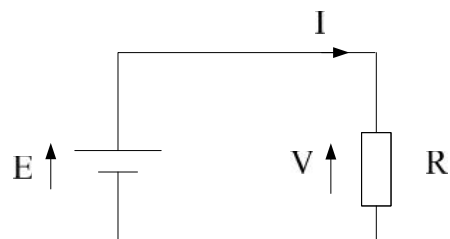
Where m is the number of voltages in the path (loop) , and V_m is the m^{th} voltage .



$$E - V = 0$$

$$E = V$$

$$I = \frac{V}{R} = \frac{E}{R}$$

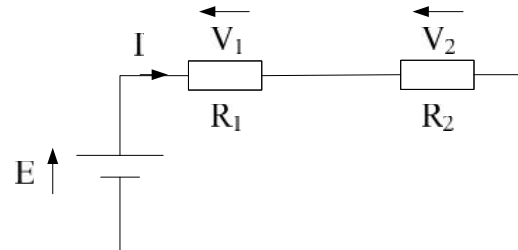


$$E - V_1 - V_2 = 0$$

$$E = V_1 + V_2 \quad ; \quad R_T = R_1 + R_2$$

$$I = \frac{E}{R_T} = \frac{V_1 + V_2}{R_T}$$

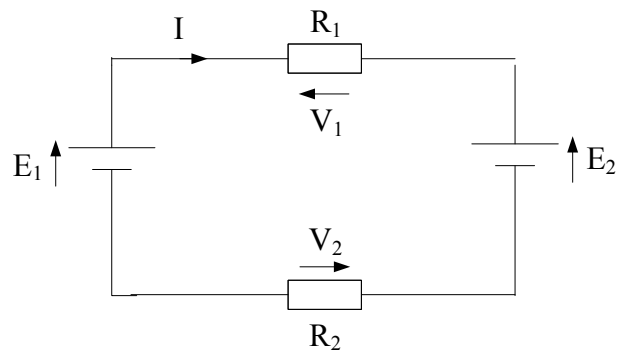Example: Use K.V.L. to find the current in the following circuit diagram?



Solution: From K.V.L. $\sum V = 0$

$$\therefore E_1 - V_1 - E_2 - V_2 = 0$$

$$E_1 - E_2 = V_1 + V_2$$


$$E_1 - E_2 = IR_1 + IR_2$$

$$E_1 - E_2 = I (R_1 + R_2)$$

$$\therefore I = \frac{E_1 - E_2}{R_1 + R_2}$$

Example: For the following circuit diagram, Find I using:-

- a) Ohm's law.
- b) K.V.L.

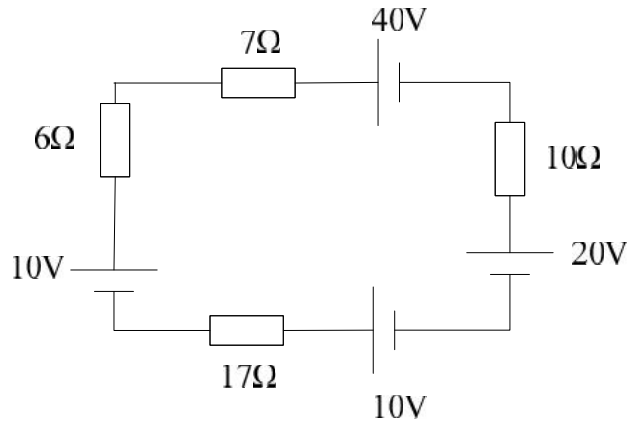

Solution:

a) By applying ohm's law :-

$$I = \frac{E_T}{R} = \frac{20 + 40 - 10 - 10}{10 + 7 + 6 + 17} = \frac{40}{40} = 1A$$

b) By applying K.V.L. :-

$$10 + 6I + 7I - 40 + 10I - 20 + 10 + 17I = 0$$

$$10 - 40 - 20 + 10 + I (6 + 7 + 10 + 17) = 0$$

$$-40 = -I (40) \Rightarrow I = \frac{40}{40} = 1A$$