

Voltage divider Rule :-

$$R_T = R_1 + R_2$$


$$I = \frac{E}{R_T}$$

$$V_1 = I.R_1 = \left(\frac{E}{R_T} \right) R_1 = \frac{E.R_1}{R_T}$$

$$V_2 = I.R_2 = \left(\frac{E}{R_T} \right) R_2 = \frac{E.R_2}{R_T}$$

$$V_n = \frac{ER_n}{R_T}$$

Voltage divider rule

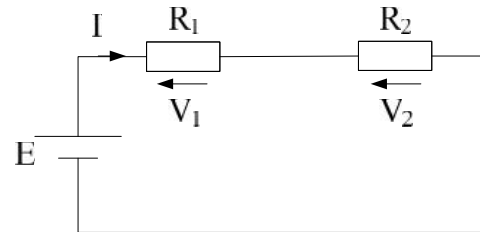


V_n = Voltage across R_n

E = The (emf) voltage across the series elements .

R_T = The total resistance of the series circuits .

Example :- Using voltage divider rule , determine the voltage V₁ , V₂ , V₃ and V₄ for the series circuit in figure below , given that ; R₁ = 2KΩ , R₂ = 5KΩ , R₃ = 8KΩ , E = 45 V ?

Solution :-

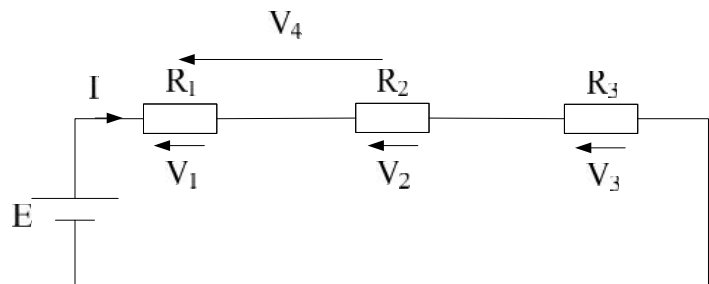

$$V_1 = \frac{R_1 E}{R_T} = \frac{2 * 10^3 * 45}{15 * 10^3} = 6V$$

$$V_2 = \frac{R_2 E}{R_T} = \frac{5 * 10^3 * 45}{15 * 10^3} = 15V$$

$$V_3 = \frac{R_3 E}{R_T} = \frac{8 * 10^3 * 45}{15 * 10^3} = 24V$$

$$V_4 = \frac{(R_1 + R_2)E}{R_T} = \frac{7 * 10^3 * 45}{15 * 10^3} = 21V \quad \text{or } V_4 = V_1 + V_2 = 21V$$

To check: $E - V_1 - V_2 - V_3 = 0$

$$E = V_1 + V_2 + V_3 \Rightarrow 45 = 6 + 15 + 24$$

$$45 = 45$$

Active Potential :-

رموز الارضي




V_{ab} is the voltage difference between the point a and point b


$$V_{ab} = V_a - V_b = 14 - 8 = 6V$$

$$V_{ba} = V_b - V_a = 8 - 14 = -6V$$


$$V_{ab} = - V_{ba}$$

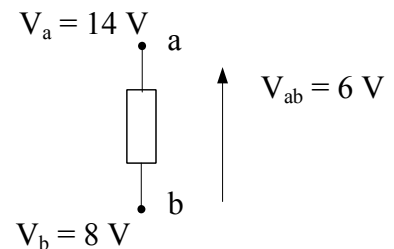

$$V_a = -7 \text{ V}$$

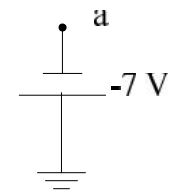


$$V_a = 10 \text{ V}$$

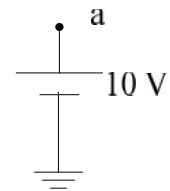


$$V_a = 0 \text{ V}$$





$$E = 20 \text{ V}$$

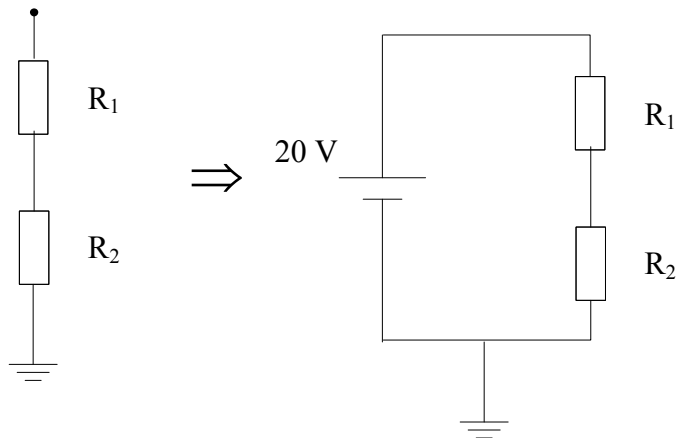


$$E = -12 \text{ V}$$

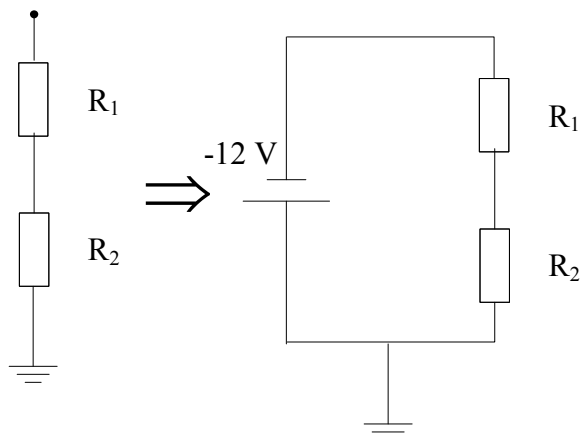

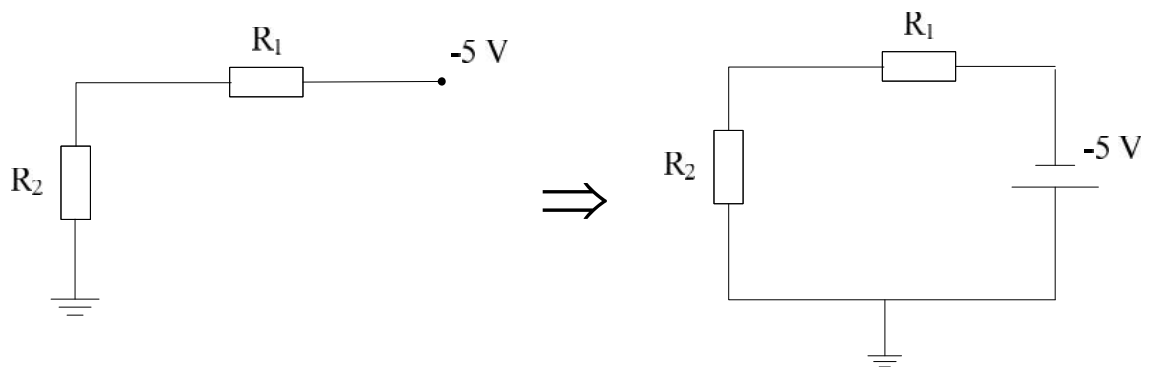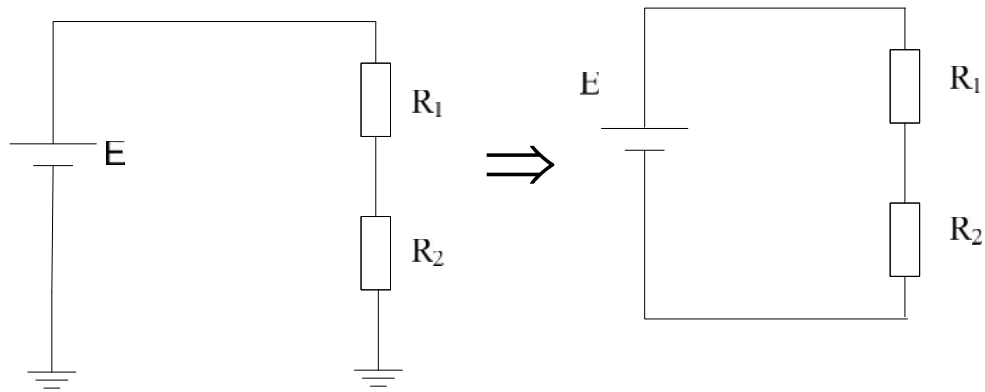

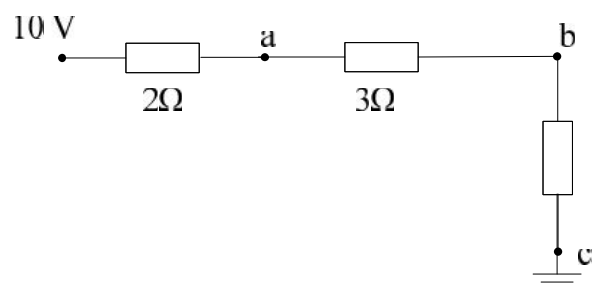Example :- Find V_a , V_b , V_c , V_{ab} , V_{ac} and V_{bc} for the following diagram .




Solution :-

$$R_T = R_1 + R_2 + R_3$$

$$= 2 + 5 + 3 = 10 \Omega$$
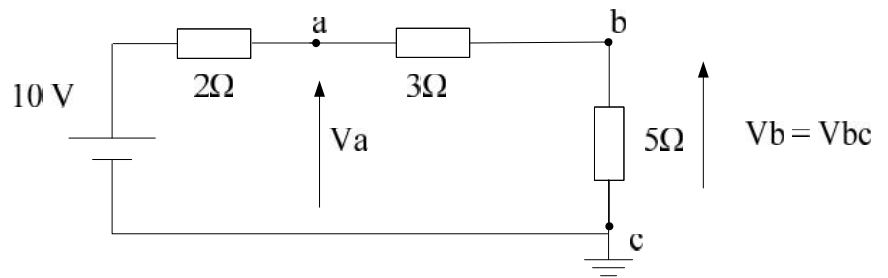
$$I = \frac{E}{R_T} = \frac{10}{10} = 1A$$



$$E - V_2 - V_a = 0$$

$$V_a = E - V_2 = 10 - (2 * 1) = 8 \text{ V}$$

$$V_b = V_5 = (1 * 5) = 5 \text{ V} = V_{bc} \quad ; \quad V_c = 0 \text{ V}$$

$$\text{or} \quad E - V_2 - V_3 - V_b = 0 \quad \Rightarrow \quad V_b = E - V_2 - V_3 = 10 - 2 - 3 = 5 \text{ V}$$

$$V_{ab} = V_a - V_b = 8 - 5 = 3 \text{ V}$$

$$V_{ac} = V_a - V_c = 8 - 0 = 8 \text{ V}$$

$$V_{bc} = V_b - V_c = 5 - 0 = 5 \text{ V}$$

Equivalence of actual sources :-

	Voltage Source	Current Source
Open Circuit	$V_{oc} = E$ $I = 0$	$V_{oc} = I_o \frac{1}{G_o}$
Short circuit	$I_{sc} = \frac{E}{R_o}$ $V = 0$	$I_{sc} = I_o$


Kirchoff's Current Law (K.C.L.) :-

The algebraic sum of ingoing currents is equal to the out going currents at any point .

$$\sum I_{in} = \sum I_{out}$$



Or , At any point , the algebraic sum of entering and leaving current is zero .

$$\sum I = 0$$

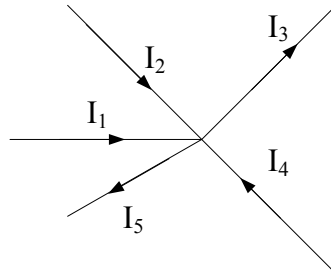

$$I_1 + I_2 + I_4 = I_3 + I_5$$

Or $I_1 + I_2 + I_4 - I_3 - I_5 = 0$

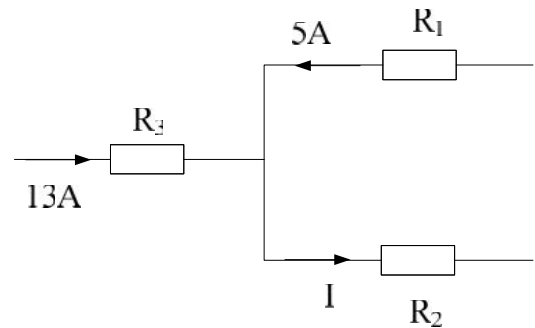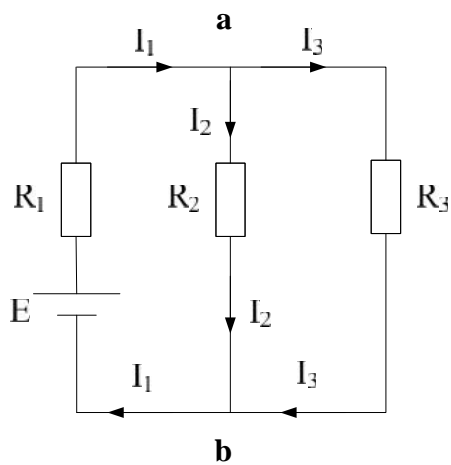

At a

$$I_1 = I_2 + I_3$$

Or $I_1 - I_2 - I_3 = 0$

At b


$$-I_1 + I_2 + I_3 = 0$$

$$13 + 5 - I = 0$$

$$18 - I = 0$$

$$\therefore I = 18 \text{ A}$$

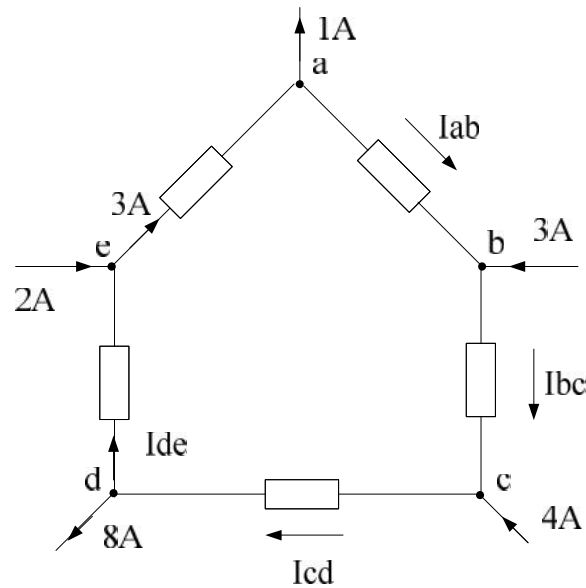Example :- Find the current in each section in the cct. Shown ?



Solution :-

At node a

$$3 - 1 - I_{ab} = 0$$

$$2 - I_{ab} = 0 \Rightarrow I_{ab} = 2 \text{ A}$$

At node b

$$I_{ab} + 3 - I_{bc} = 0$$

$$2 + 3 - I_{bc} = 0 \Rightarrow I_{bc} = 5 \text{ A}$$

At node c

$$I_{bc} + 4 - I_{cd} = 0$$

$$5 + 4 - I_{cd} = 0 \Rightarrow I_{cb} = 9 \text{ A}$$

At node d

$$I_{cd} - 8 - I_{de} = 0$$

$$9 - 8 - I_{de} = 0 \Rightarrow I_{de} = 1 \text{ A}$$


At node e

$$2 - 3 + I_{de} = 0$$

$$2 - 3 + 1 = 0$$

$$0 = 0 \text{ check .}$$

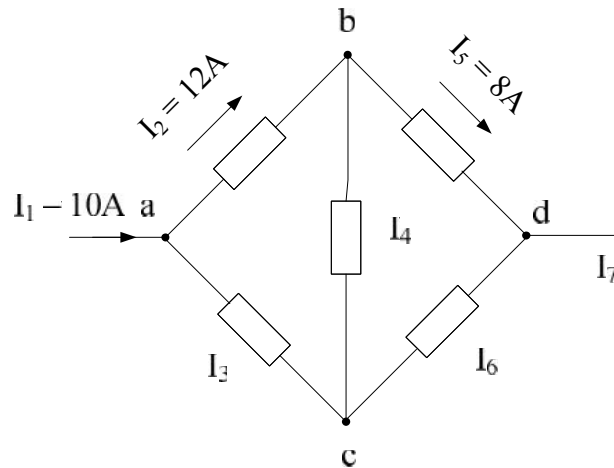Example :- Find the magnitude and direction of the currents I_3 , I_4 , I_6 , I_7 in the following cct. Diagram?



Solution :-

$$\sum I_{enter} = \sum I_{leave}$$

$$\therefore I_1 = I_7 = 10 \text{ A}$$

At node a ; suppose I_3 is entering

$$I_1 + I_3 - I_2 = 0$$

$$10 + I_3 - 12 = 0 \Rightarrow I_3 = 2 \text{ A}$$

At node b;

I_2 enter , I_5 leave , $\therefore I_4$ must be leaving

$$I_2 = I_5 + I_4$$

$$12 = 8 + I_4 \Rightarrow I_4 = 12 - 8 = 4 \text{ A}$$

At node c;

I_4 enter , I_3 leave , $\therefore I_6$ leave

$$I_4 = I_3 + I_6$$

$$4 = 2 + I_6 \Rightarrow I_6 = 2 \text{ A}$$

At node d;


I_5 and I_6 enter , I_7 leave

$$I_7 = I_5 + I_6$$

$$10 = 8 + 2$$

$$10 = 10 \quad \text{Ok.}$$

Resisters in Parallel :-

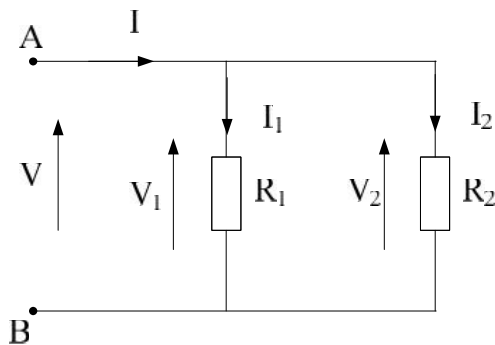

From K.V.L.

$$V = V_1 = V_2$$

From K.C.L.

$$I = I_1 + I_2$$

From Ω .L.

$$I = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$

$$= V_1 G_1 + V_2 G_2$$

$$= V_1 (G_1 + G_2)$$

or $I = V (G_1 + G_2)$

$$I = V G_T$$

Where $G_T = G_1 + G_2$


Hence
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 \cdot R_2}$$

or

$$R_T = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

In the same minner , if we have three resistors in parallel , then:
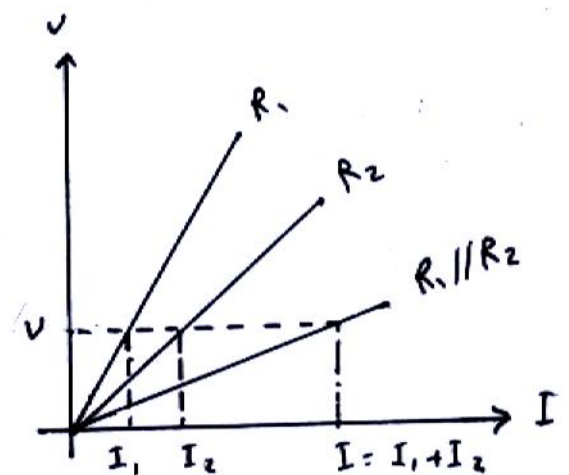
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



$$\frac{1}{R_T} = \frac{R_2 \cdot R_3 + R_1 \cdot R_3 + R_1 \cdot R_2}{R_1 \cdot R_2 \cdot R_3}$$

$$R_T = \frac{R_1 \cdot R_2 \cdot R_3}{R_2 \cdot R_3 + R_1 \cdot R_3 + R_1 \cdot R_2}$$

And , if we have N of parallel resistance , then

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$


Also

$$P_T = P_1 + P_2 + P_3$$

$$P_1 = V_1 I_1 = I_1^2 R_1 = \frac{V_1^2}{R_1}$$

$$\text{Source power } P_s = EI_T = I_T^2 R_T = \frac{E^2}{R_T}$$

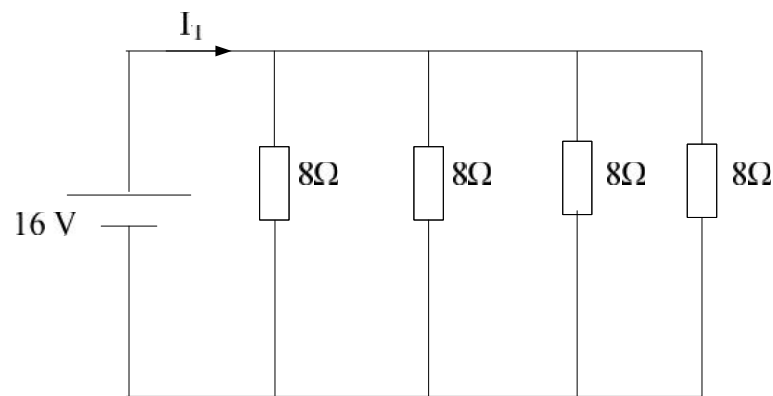Example :- For the following cct. Find R_T , P_T , I_T , I_b ?



Solution :-

$$R_T = \frac{R}{N} = \frac{8}{4} = 2\Omega$$

في حالة كون قيم المقاومات متساوية

$$I_T = \frac{E}{R_T} = \frac{16}{2} = 8A$$

$$I_{branch} = \frac{E}{R_1} = \frac{16}{8} = 2A$$

$$P_T = I_T^2 R_T = (8)^2 \cdot (2) = 128W$$


$$\text{or } P_T = E \cdot I_T = 16 * 8 = 128W$$

$$\begin{aligned} \text{or } P_T &= P_1 + P_2 + P_3 + P_4 \\ &= (2)^2 * 8 + (2)^2 * 8 + (2)^2 * 8 + (2)^2 * 8 \end{aligned}$$

$$= 32 + 32 + 32 + 32 = 128W$$

Example :- For the parallel network in fig. below , find :-

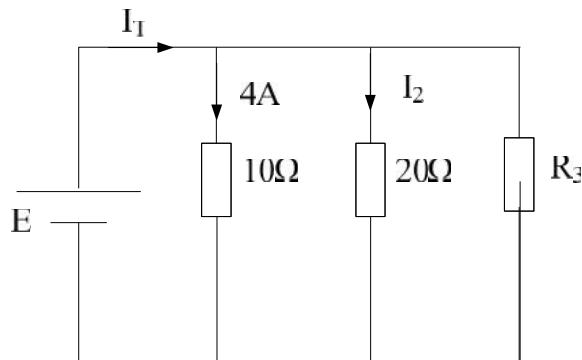a) R_3 , b) E , c) I_T , I_2 , d) P_2 ; given that $R_T = 4 \Omega$?



Solution :-

a)

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{4} = \frac{1}{10} + \frac{1}{20} + \frac{1}{R_3}$$

$$0.25 = 0.1 + 0.05 + \frac{1}{R_3}$$

$$0.25 - 0.1 - 0.05 = \frac{1}{R_3}$$

$$0.1 = \frac{1}{R_3} \Rightarrow R_3 = \frac{1}{0.1} = 10\Omega$$

b) $E = V_1 = I_1 R_1 = 4 * 10 = 40 V$

$$\text{c) } I_T = \frac{E}{R_T} = \frac{40}{4} = 10A$$

$$I_2 = \frac{V_2}{R_2} = \frac{E}{R_2} = \frac{40}{20} = 2A$$

$$\text{d) } P_2 = I_2^2 R_2 = (2)^2 \cdot (20) = 80W$$


$$\text{or } P_2 = \frac{V_2^2}{R_2}, \text{ or } P_2 = I_2 V_2$$

Current division Rule :-

$$V = I \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$I_1 = \frac{V}{R_1} = \frac{I \frac{R_1 \cdot R_2}{R_1 + R_2}}{R_1}$$
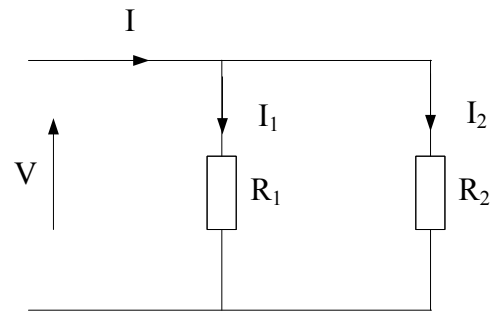
$$\therefore I_1 = I \frac{R_2}{R_1 + R_2}$$




In the same manner

$$I_2 = I \frac{R_1}{R_1 + R_2}$$

$$\text{Also } \frac{I_1}{I_2} = \frac{I \frac{R_2}{R_1 + R_2}}{I \frac{R_1}{R_1 + R_2}} = \frac{R_2}{R_1}$$

$$\therefore \frac{I_1}{I_2} = \frac{R_2}{R_1} = \frac{G_1}{G_2}$$

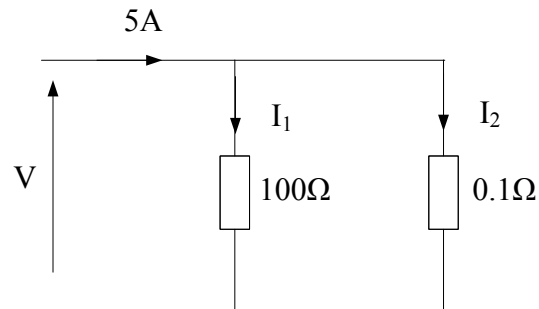Example :- For the following circuit. , find V , I₁ and I₂?



Solution :-

$$R_T = \frac{R_1 \cdot R_2}{R_1 + R_2} = \frac{100 \cdot 0.1}{100 + 0.1} = \frac{10}{100.1} = 0.0999\Omega$$

$$V = I \cdot R_T = 5 \cdot 0.0999 = 0.4995 \text{ V}$$

$$I_1 = \frac{V}{100} = 0.004995 \text{ A}$$


$$I_2 = \frac{V}{0.1} = 4.995 \text{ A}$$

To check $I = I_1 + I_2$

$$5 = 0.004995 + 4.995$$

$$5 = 5 \text{ Ok.}$$

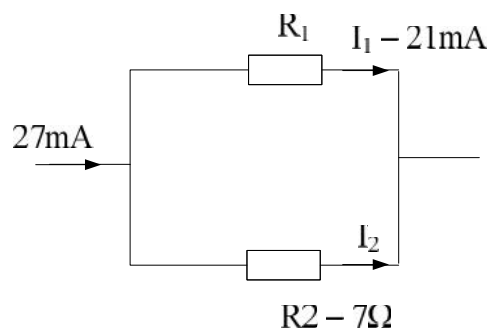Example :- Determine the resistance R1 in the figure below?



Solution :-

$$I = I_1 + I_2$$

or $I_2 = I - I_1 = 27 - 21 = 6 \text{ mA}$

$$V_2 = I_2 R_2 = 6 * 10^{-3} * 7 = 42 \text{ mV}$$

$$V_1 = V_2 = 42 \text{ mV}$$

$$R_1 = \frac{V_1}{I_1} = \frac{42 * 10^{-3}}{21 * 10^{-3}} = 2\Omega$$

or

$$I_1 = I \frac{R_2}{R_1 + R_2} \Rightarrow 21 * 10^{-3} = \frac{27 * 10^{-3} * 7}{R_1 + 7}$$

$$R_1 = 2\Omega$$