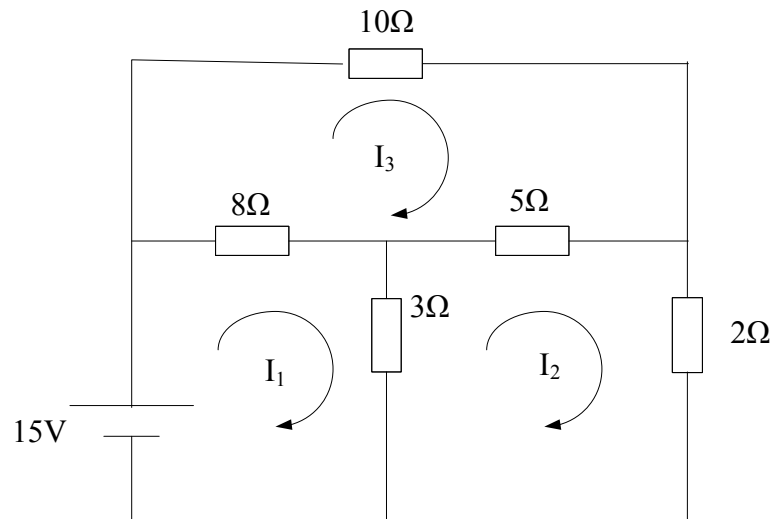


Network Solution :-

To solve a circuit is to find the current and voltage in all branches.

1) Loop (Mesh) current method :-

Example(1):- Find the current through the $10\ \Omega$ resistor of the network shown:



Solution :-

- مجموع المقاومات * تيار ال Loop + المقاومة المشتركة * تيار ال Loop المشترك \mp الفولتية
(حسب اتجاهها مع تيار ال Loop) = صفر .

The loop equations are :-

Loop 1 :-

$$-(8+3)I_1 + 3I_2 + 8I_3 + 15 = 0$$

Loop 2 :-

$$-(3+5+2)I_2 + 3I_1 + 5I_3 = 0$$

Loop 3 :-

$$-(10+8+5)I_3 + 8I_1 + 5I_2 = 0$$

Rearrange the equations , then :-

$$-11I_1 + 3I_2 + 8I_3 = -15$$


$$3I_1 - 10I_2 + 5I_3 = 0$$

$$8I_1 + 5I_2 - 23I_3 = 0$$

$$I_3 = \frac{D_3}{D} = \frac{\begin{bmatrix} -11 & 3 & -15 \\ 3 & -10 & 0 \\ 8 & 5 & 0 \end{bmatrix}}{\begin{bmatrix} -11 & 3 & 8 \\ 3 & -10 & 5 \\ 8 & 5 & -23 \end{bmatrix}} = 1.22A$$

$$\therefore I_3 = I_{10\Omega} = 1.22A$$

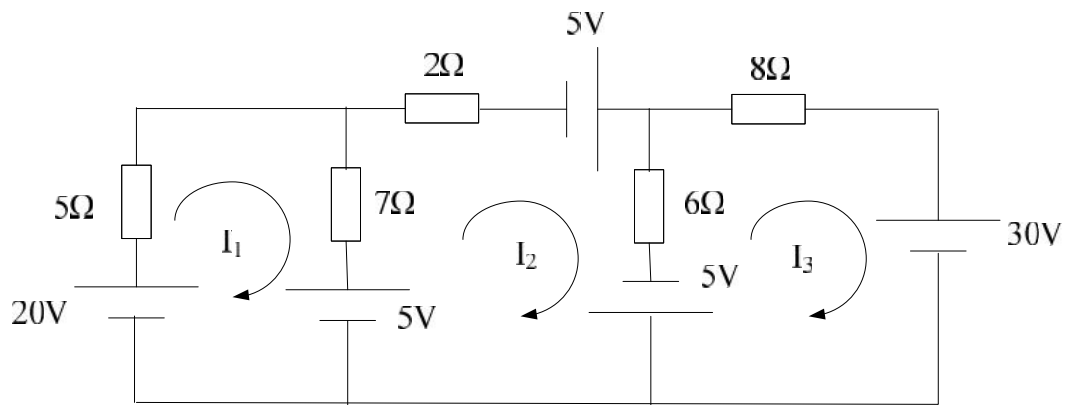Example(2):- Solve following circuit diagram;



Solution :-

$$-I_1 (5+7) + 7I_2 + 20 - 5 = 0$$

$$-I_2 (7+2+6) + 7I_1 + 6I_3 + 5 + 5 + 5 = 0$$

$$-I_3 (6+8) + 6I_2 - 5 - 30 = 0$$

Rearrange;

$$-12I_1 + 7I_2 + 0 = -15 \quad \text{-----} \quad (1)$$

$$7I_1 - 15I_2 + 6I_3 = -15 \quad \text{-----} \quad (2)$$


$$0 + 6I_2 - 14I_3 = 35 \quad \text{-----} \quad (3)$$

$$I_1 = \frac{D_1}{D} = \frac{\begin{bmatrix} -15 & 7 & 0 \\ -15 & -15 & 6 \\ 35 & 6 & -14 \end{bmatrix}}{\begin{bmatrix} -12 & 7 & 0 \\ 7 & -15 & 6 \\ 0 & 6 & -14 \end{bmatrix}} = \frac{2610}{1402} = 1.862A$$

$$I_2 = \frac{D_2}{D} = \frac{\begin{bmatrix} -12 & -15 & 0 \\ 7 & -15 & 6 \\ 0 & 35 & -14 \end{bmatrix}}{1402} = \frac{1470}{1402} = 1.049A$$

$$I_3 = \frac{D_3}{D} = \frac{\begin{bmatrix} -12 & 7 & -15 \\ 7 & -15 & -15 \\ 0 & 6 & 35 \end{bmatrix}}{1402} = \frac{-2875}{1402} = -2.05A$$

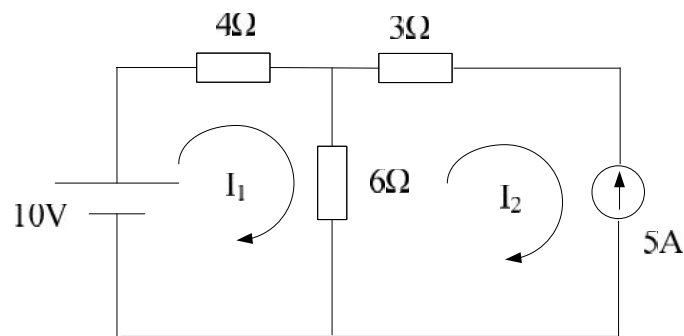Example(3):- Find the current in the 10V source , for the following network;



Solution :-

$$I_2 = -5 A$$


Hence , we need only one equation to solve this circuit

$$-I_1 (4+6) + 6 * (-5) + 10 = 0$$

$$-10I_1 - 20 = 0 \Rightarrow -10I_1 = 20$$

$$\therefore I_1 = \frac{20}{-10} = -2A$$

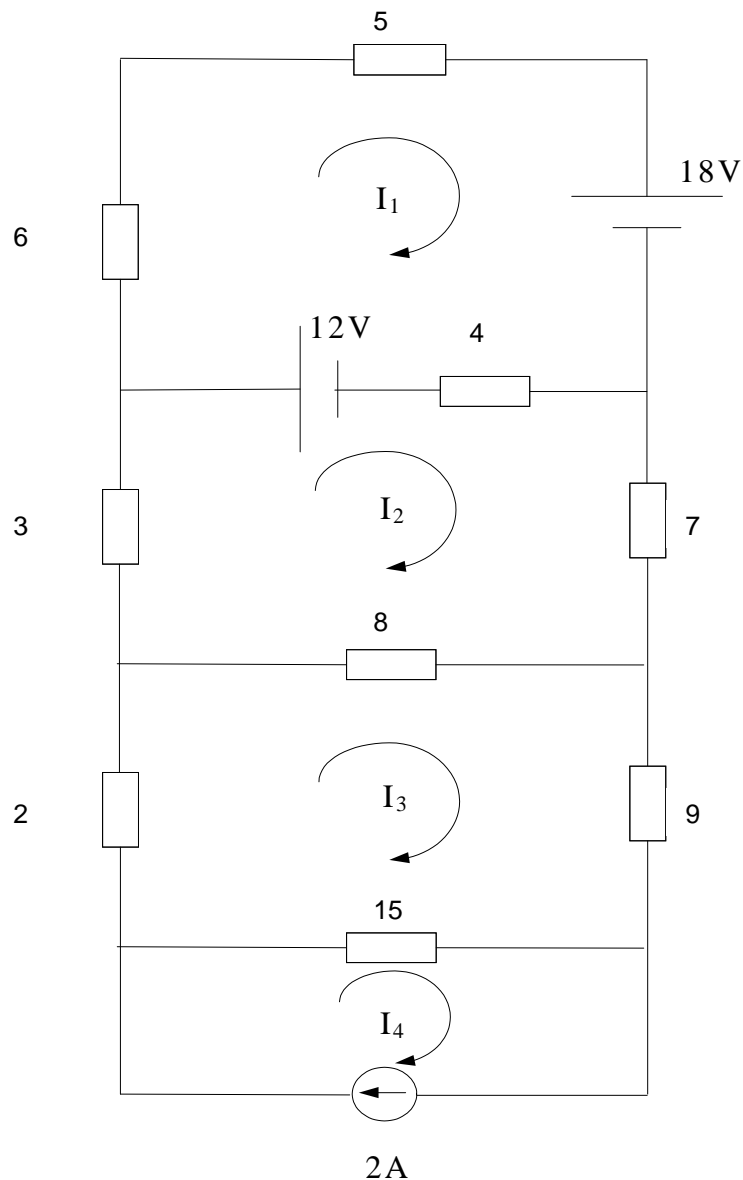Example(4):- Solve the following circuit diagram, also find the voltage across 15 Ω resistance?



Solution:-

$$I_4 = 2 \text{ A}$$

$$-I_1 (4+6+5) + 4I_2 + 12 - 18 = 0$$

$$-I_2 (8+3+4+7) + 4I_1 + 8I_3 - 12 = 0$$

$$-I_3 (15+2+8+9) + 8I_2 + 15 * 2 = 0$$

Rearrange:-

$$-15I_1 + 4I_2 + 0 = 6 \quad \text{-----} \quad (1)$$

$$4I_1 - 22I_2 + 8I_3 = 12 \quad \text{-----} \quad (2)$$

$$0 + 8I_2 - 34I_3 = -30 \quad \text{-----} \quad (3)$$

$$I_1 = \frac{D_1}{D}$$


$$I_2 = \frac{D_2}{D}$$

$$I_3 = \frac{D_3}{D}$$


أكمل الحل

$$\begin{aligned} V_{15} &= I_{15} * R_{15} \\ &= (I_3 - I_4) * 15 \\ &= (I_3 - 2) * 15 \end{aligned}$$

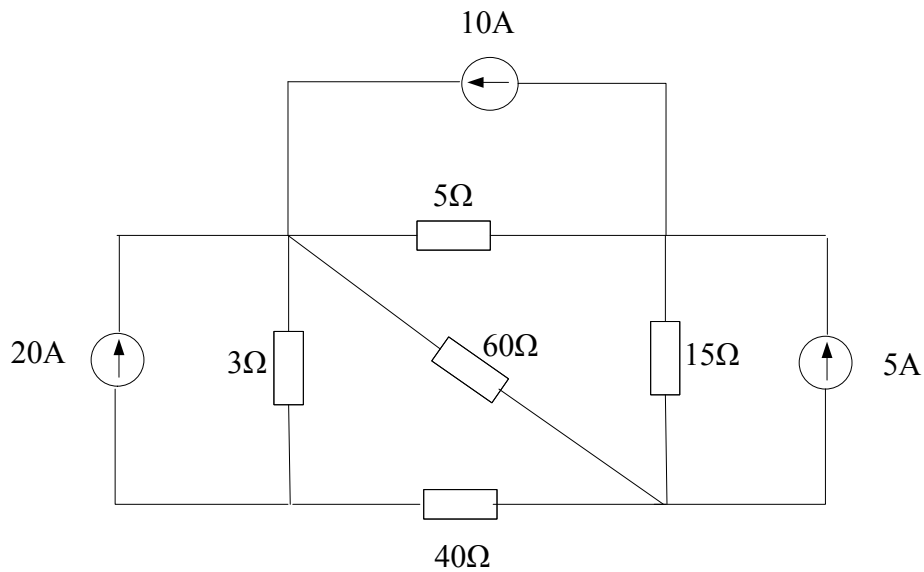Example(5):- Solve the following circuit diagram .



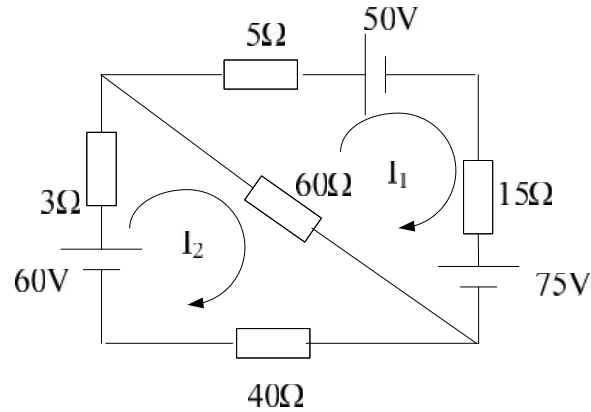Solution:- The above diagram can be reduced to the following diagram;



$$-I_1 (5+15+60) + 60I_2 - 50 - 75 = 0$$

$$-I_2 (3+60+40) + 60I_1 + 60 = 0$$

Rearrange:-

$$-80I_1 + 60I_2 = 125 \quad \text{-----} \quad (1)$$


$$60I_1 - 103I_2 = -60 \quad \text{-----} \quad (2)$$

$$I_1 = \frac{D_1}{D}$$

$$I_2 = \frac{D_2}{D}$$

أكمل الحل

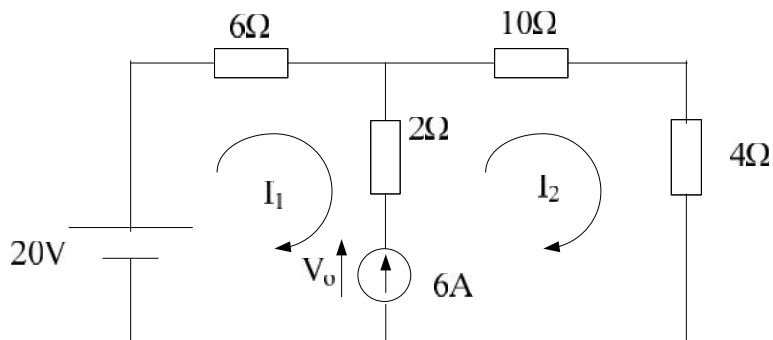Example(6):- Solve the following circuit diagram:



Solution:-

$$-(6+2)I_1 + 2I_2 + 20 - V_o = 0 \quad \text{-----} \quad (1)$$

$$-(10+2+4)I_2 + 2I_1 + V_o = 0 \quad \text{-----} \quad (2)$$

$$I_2 - I_1 = 6 \quad \text{-----} \quad (3)$$

Add eq. 1 & eq. 2

$$-8I_1 + 2I_2 + 20 - 16I_2 + 2I_1 = 0 \quad \text{-----} \quad (1)$$

$$-6I_1 - 14I_2 = -20 \quad \text{-----} \quad (2)$$

From eq. 3

$$I_1 - I_2 = -6$$

$$I_1 = \frac{D_1}{D} = \frac{\begin{bmatrix} -20 & -14 \\ -6 & -1 \end{bmatrix}}{\begin{bmatrix} -6 & -14 \\ 1 & -1 \end{bmatrix}} = \frac{20 - 84}{6 + 14} = -3.2A$$

$$I_2 = \frac{D_2}{D} = \frac{\begin{bmatrix} -6 & -20 \\ 1 & -6 \end{bmatrix}}{20} = \frac{36 + 20}{20} = 2.8A$$