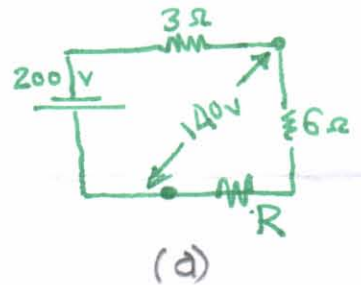


## Answers to the Exam. Questions.


Q<sub>1</sub> :: Find the unknown for ::

$$\begin{aligned} \text{(a)} \quad 140 &= \frac{200(R+6)}{3+6+R} \\ 60R &= 1260 - 1200 \\ \therefore R &= \frac{60}{60} = 1\Omega \end{aligned}$$




(b)
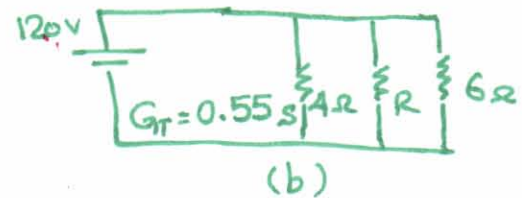
$$\begin{aligned} G_T &= \frac{1}{4} + \frac{1}{R} + \frac{1}{6} \\ 0.55 &= 0.25 + \frac{1}{R} + 0.166 \\ \therefore 0.134R &= 1 \\ \therefore R &= 1/0.134 \Omega \end{aligned}$$





(c)
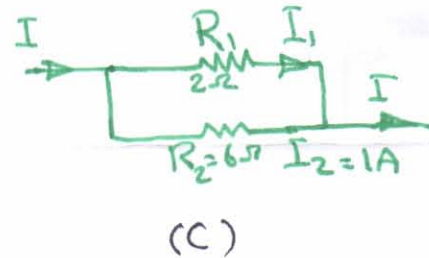
$$\begin{aligned} \text{Using C.D.R} \\ I_2 &= \frac{I \cdot R_1}{R_1 + R_2} = \frac{2I}{2+6} = 1 \\ \therefore I &= \frac{8}{2} = 4A \\ I_1 &= I - I_2 = 4 - 1 = 3A \end{aligned}$$




Q<sub>2</sub> - a - Determine the Current - - -
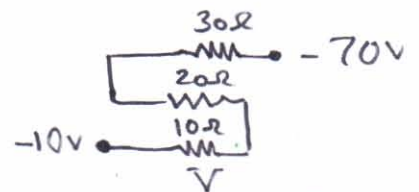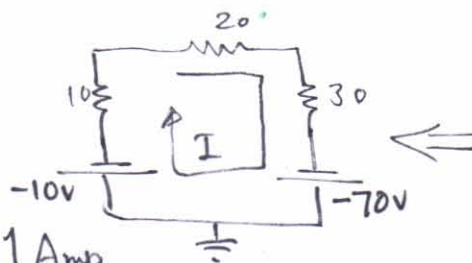
$$\begin{aligned} E &= R_T I \\ \therefore I &= \frac{70 - 10}{10 + 20 + 30} = 1 \text{ Amp} \\ V &= IR = 1 \times 10 = 10V \end{aligned}$$



(a)

b-

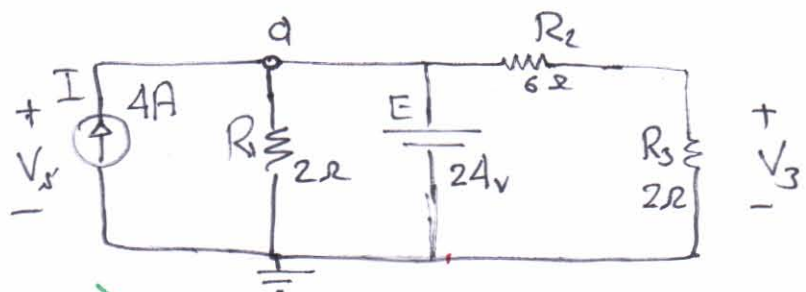

(1-5)

The figure is redrawn as shown

Since the cks have 4. branches in Parallel, all Voltages equal

$$\therefore I_1 = E/R_1 = \frac{24V}{2\Omega} = 12 \text{ Amp}$$

$$I_s = I_2 + I_3$$

$$I_3 = E/R_2 + R_3 = 24/2+6 = 3A$$


K.C.L at Point (a)

$$\therefore I + I_2 = I_1 \quad \therefore I_2 = 12 - 4 = 8A$$

$$\therefore I_s = 8 + 3 = 11 \text{ Amps.}$$

$$V_s = E = 24V.$$
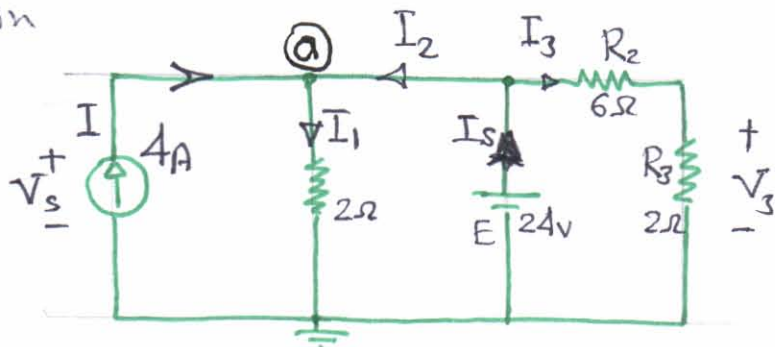
$$V_3 = I_3 \cdot R_3 = 3 \times 2 = 6V.$$



Q3: Using mesh format ....

Assign the Loop Currents CW.

$I_1$  :

$$(2+3)I_1 - 3I_2 = 60 - 25$$

$$5I_1 - 3I_2 = 35$$


$I_2$  :

$$(5+3)I_2 - 3I_1 = 6 - 60 - 20$$

$$8I_2 - 3I_1 = -74$$

$$\therefore 5I_1 - 3I_2 = 35 \dots \textcircled{1}$$
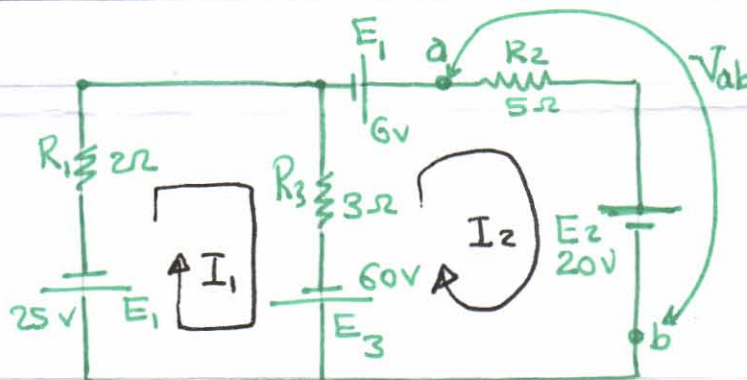
$$-3I_1 + 8I_2 = -74 \dots \textcircled{2}$$



$$\therefore I_1 = \frac{\begin{vmatrix} 35 & -3 \\ -74 & 8 \end{vmatrix}}{\begin{vmatrix} 5 & -3 \\ -3 & 8 \end{vmatrix}} = 1.8 \text{ Amps}$$

$$I_2 = \frac{\begin{vmatrix} 5 & 35 \\ -3 & -74 \end{vmatrix}}{\begin{vmatrix} 5 & -3 \\ -3 & 8 \end{vmatrix}} = -8.5 \text{ Amps.}$$

(2-5)





Q4 - a) Determine the Current I ....

$\Delta$  circuit of 6K-4K-4K to be converted into Y:

$$R_1 = \frac{6 \times 4}{4+4+6} = \frac{12}{7} \text{ K}\Omega$$


$$R_2 = \frac{4 \times 4}{4+4+6} = \frac{8}{7} \text{ K}\Omega$$
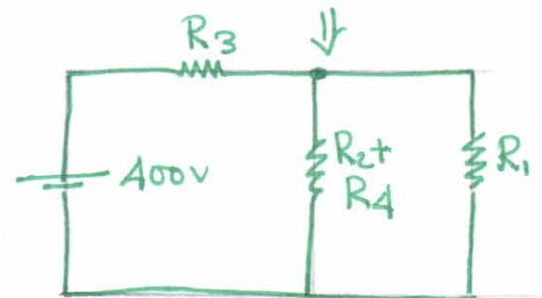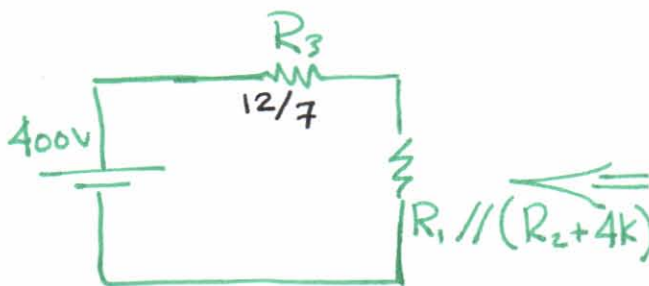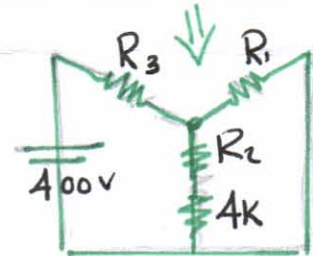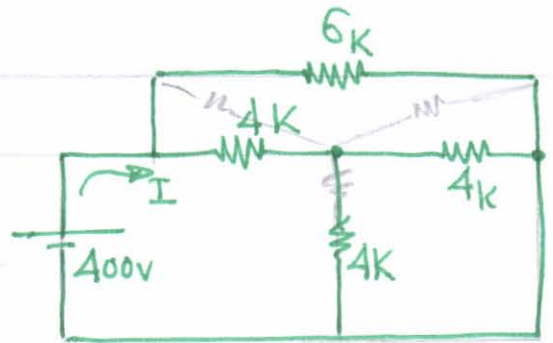
$$R_3 = \frac{6 \times 4}{4+4+6} = \frac{12}{7} \text{ K}\Omega$$



$$R_1 // (R_2 + 4K) = \frac{12 \times 36}{7 \times 7} \times \frac{7}{48} = \frac{9}{7} \text{ K}\Omega$$
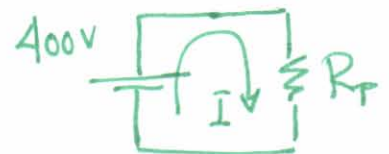
$$\begin{aligned} R_T &= R_3 + R_1 // (R_2 + 4K) \\ &= \frac{12}{7} + \frac{9}{7} \\ &= 3 \text{ K}\Omega \end{aligned}$$





$$\therefore I = \frac{400 \text{ V}}{3 \text{ K}\Omega} = 133.3 \text{ mA}$$

b) Find the Norton ...

$$\begin{aligned} R_N &= 5 // 5 + 5 \\ &= 7.5 \Omega \end{aligned}$$

$$I_N = \frac{30}{5 + \frac{5}{2}} = \frac{60}{15} \text{ A}$$

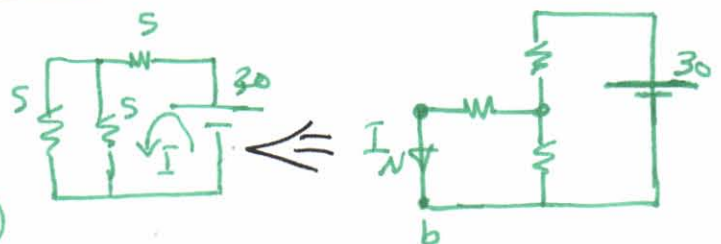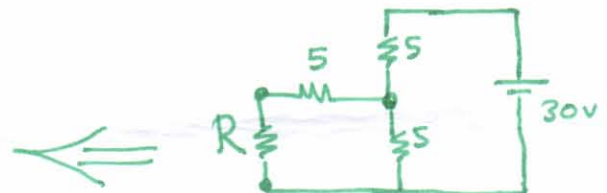
$$I_N = \frac{5 \times \frac{60}{15}}{10} = 1.33 \text{ A}$$





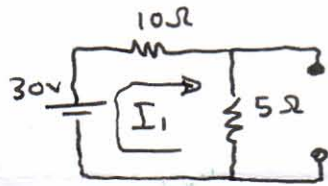Q5/Using Superposition....


Consider the effect of the 30v source as shown



$$I_1 = \frac{E}{R_T} = \frac{30}{10+5} = 2A$$

The effect of the 15A source ∴ Using C.D.R
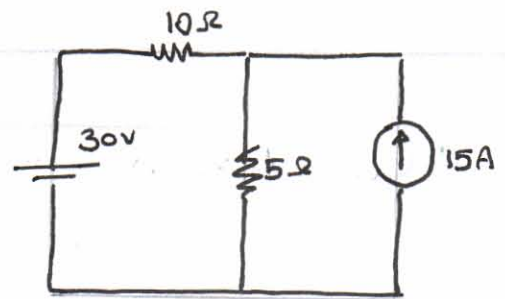
$$I_2 = \frac{10 \times 15}{10+5} = \frac{150}{15} = 10A$$



∴ Total current through 5Ω is  $I_{5\Omega} = 10 + 2 = 12A$




The actual Power to the 5Ω is  $I^2 R = (12)^2 \times 5 = 720W$

The calculated Power to the 5Ω due to each source

$$P_1 = I_1^2 \cdot R = (2)^2 \times 5 = 20W$$


$$P_2 = I_2^2 \cdot R = (10)^2 \times 5 = 150W$$

$$P_1 + P_2 = 20 + 150 = 170 \neq 720$$

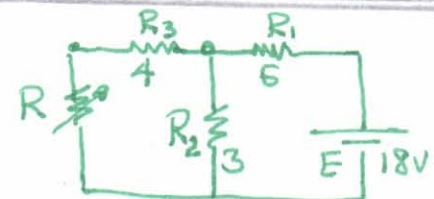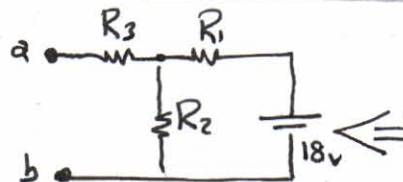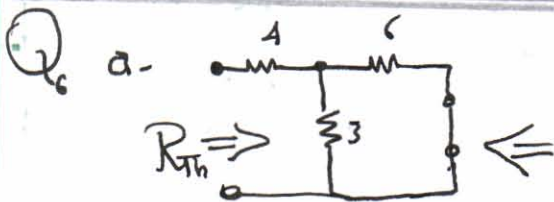

$$R_{Th} = 4 + (6 \parallel 3)$$
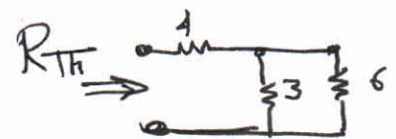
$$= 4 + \frac{6 \times 3}{6+3} = 6\Omega$$



$$I = \frac{18}{6+3} = \frac{18}{9} = 2A$$



$$V_{3\Omega} = I \cdot R_2 = 2 \times 3 = 6V$$

$$E_{TH} = 6V$$


$$I_{R_{22}} = \frac{6}{6+2} = \frac{6}{8} = 0.75A$$

$$I_{R_{30}} = \frac{6}{6+30} = \frac{6}{36} = 0.166A$$

(4-5)

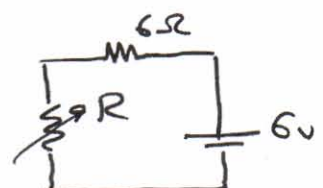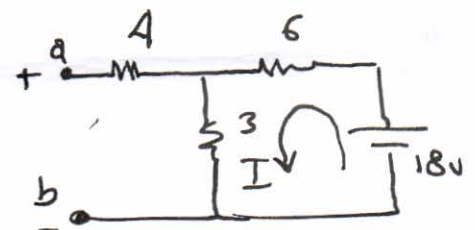

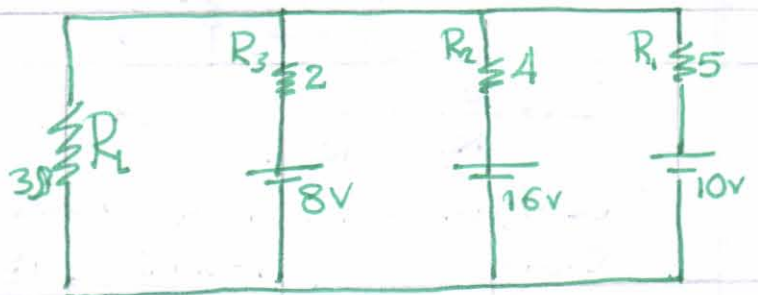Q6 - b. Find the Current through & Voltage - -  
Using Millman




$$E_{eq} = \frac{+\frac{E_1}{R_1} - \frac{E_2}{R_2} + \frac{E_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{\frac{10}{5} - \frac{16}{4} + \frac{8}{2}}{\frac{1}{5} + \frac{1}{4} + \frac{1}{2}}$$

$$= \frac{2}{0.95} = 2.105 \text{ V.}$$

$$R_{eq} = \frac{1}{\frac{1}{5} + \frac{1}{4} + \frac{1}{2}} = \frac{1}{0.95} = 1.053 \Omega.$$

The resultant source is shown

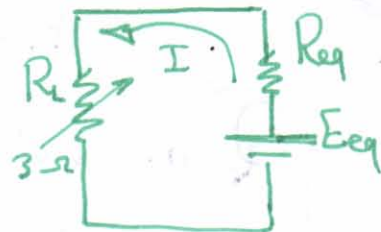

$$I_L = \frac{2.105}{1.053 + R_L} = \frac{2.105}{1.053 + 3}$$

$$= 0.519 \text{ A}$$

$$\therefore V_L = I_L R_L = (0.519)(3)$$

$$= 1.557 \text{ V.}$$

(5.5)