



Attempt five questions only

Q1: choose (a) or (b)

a) For the network in Fig. (1-a), Calculate V_{ab} , V_b , V_c .

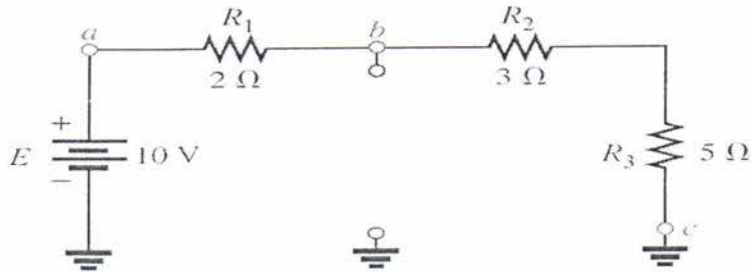


Fig.1-a

b) Find the unknown quantities for the networks in Fig. (1-b)

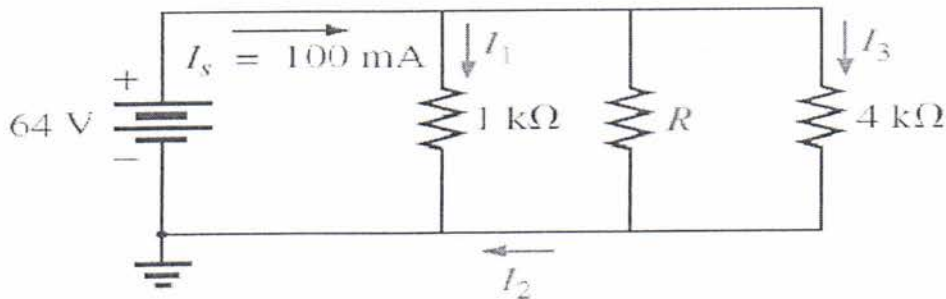


Fig.1-b

10 marks

Q2) Write the nodal equations for the networks in Fig. (2). Using determinants, solve for the nodal voltages.

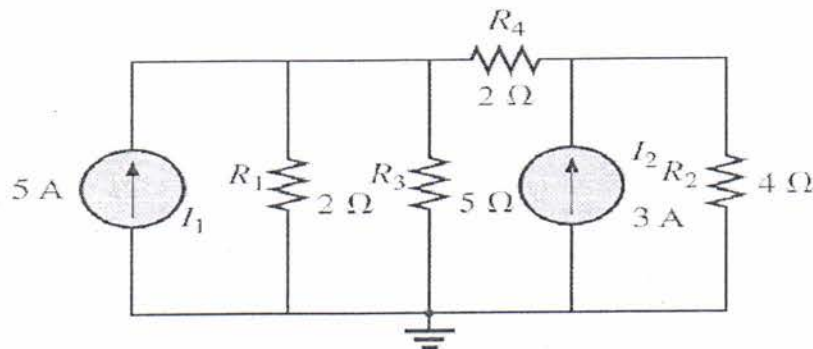


Fig.2

10 marks

Q3) a) if the flux density is (1.2 T) and the area is ($1.613 \times 10^{-4} \text{ m}^2$), determine the flux through the core.

b) For the magnetic circuit, if $NI=40 \text{ At}$, and $l=0.2 \text{ m}$, find magnetizing force.

10 marks

2

- Q4) a. For the network in Fig. (3-a) determine the current(I).
 b. Repeat part (a) for the network in Fig. (3-b)
 c. Is the reciprocity theorem satisfied?

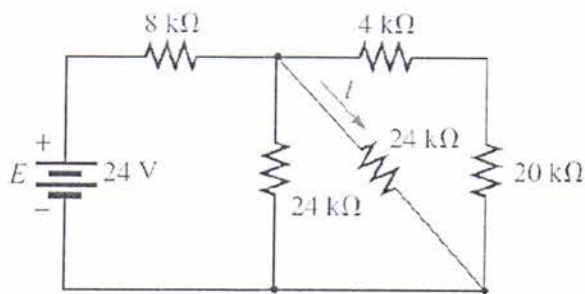


Fig.3-a

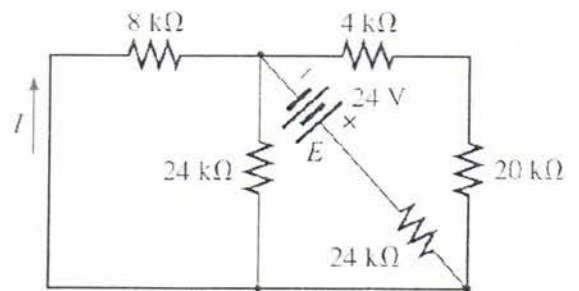


Fig 3-b

10 marks

- Q5) Using a Δ -Y or Y- Δ conversion, find the current(I) in the networks in Fig.(4)

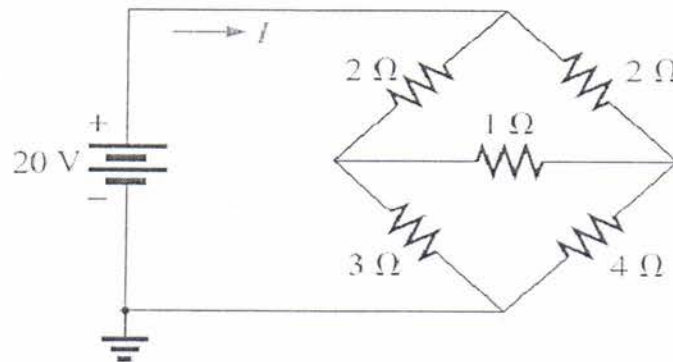


Fig. (4)

10 marks

- Q6) Find the indicated currents and voltages(I_s, I_2, I_4, V_1, V_5) for the network in Fig(5):

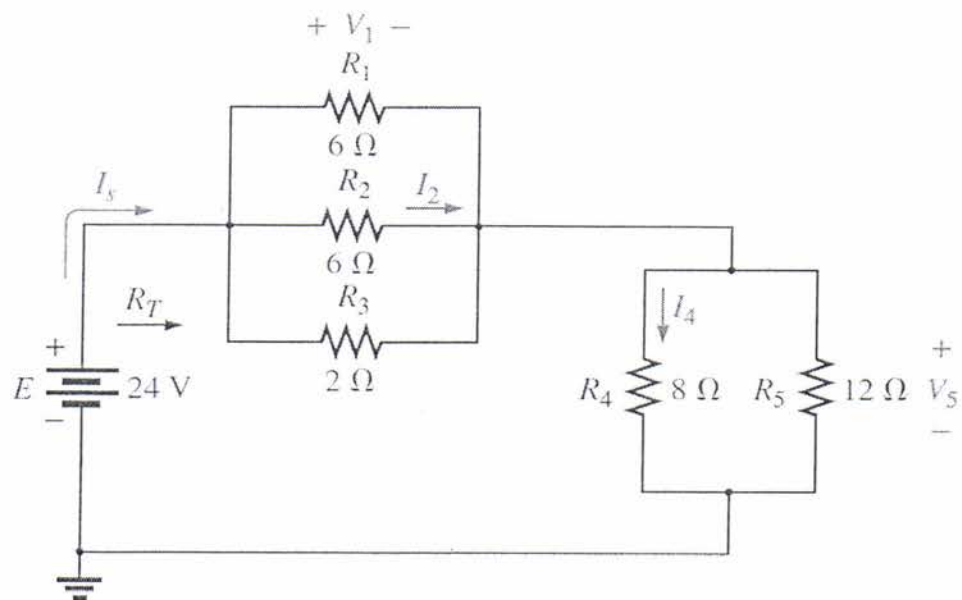


Fig. (5)

10 marks

الموجة حادة أساسيات الهندسة الكهربائية
 مرحلة ادخل / لينر + الكترينيات
 ١.٣ اعمارها طقة

Q1 a)

- Calculate V_{ab} .
- Determine V_b .
- Calculate V_c .

Solutions:

- Voltage divider rule:

$$V_{ab} = \frac{R_1 E}{R_T} = \frac{(2 \Omega)(10 \text{ V})}{2 \Omega + 3 \Omega + 5 \Omega} = +2 \text{ V}$$

- Voltage divider rule:

$$V_b = V_{R_2} + V_{R_3} = \frac{(R_2 + R_3)E}{R_T} = \frac{(3 \Omega + 5 \Omega)(10 \text{ V})}{10 \Omega} = 8 \text{ V}$$

$$\text{or } V_b = V_a - V_{ab} = E - V_{ab} = 10 \text{ V} - 2 \text{ V} = 8 \text{ V}$$

- $V_c = \text{ground potential} = 0 \text{ V}$

Q1 b)

$$I_1 = \frac{64 \text{ V}}{1 \text{ k}\Omega} = 64 \text{ mA}$$

$$I_3 = \frac{64 \text{ V}}{4 \text{ k}\Omega} = 16 \text{ mA}$$

$$I_5 = I_1 + I_2 + I_3$$

$$I_2 = I_5 - I_1 - I_3 = 100 \text{ mA} - 64 \text{ mA} - 16 \text{ mA} = 20 \text{ mA}$$

$$R = \frac{E}{I_2} = \frac{64 \text{ V}}{20 \text{ mA}} = 3.2 \text{ k}\Omega$$

$$I = I_2 + I_3 = 20 \text{ mA} + 16 \text{ mA} = 36 \text{ mA}$$

Q2)

a. V_1 V_2 **Tow Nodes**

$$V_1 \left[\frac{1}{2} + \frac{1}{5} + \frac{1}{2} \right] - \frac{1}{2} V_2 = 5$$

$$V_2 \left[\frac{1}{2} + \frac{1}{4} \right] - \frac{1}{2} V_1 = 3$$

$$1.2 V_1 - 0.5 V_2 = 5$$

$$0.75 V_2 - 0.5 V_1 = 3$$

$$\begin{aligned} 1.2 V_1 - 0.5 V_2 &= 5 \\ -0.5 V_1 + 0.75 V_2 &= 3 \end{aligned}$$

$$V_1 = \frac{\begin{vmatrix} 5 & -0.5 \\ 3 & +0.75 \end{vmatrix}}{\begin{vmatrix} 1.2 & -0.5 \\ -0.5 & 0.75 \end{vmatrix}} = \frac{(5 \times 0.75) - (3 \times -0.5)}{(1.2 \times 0.75) - (-0.5 \times -0.5)}$$

$$V_1 = 8.08 \text{ V}$$

$$V_2 = \frac{\begin{vmatrix} 1.2 & 5 \\ -0.5 & 3 \end{vmatrix}}{\begin{vmatrix} 1.2 & -0.5 \\ -0.5 & 0.75 \end{vmatrix}} = \frac{(1.2 \times 3) - (-0.5 \times 5)}{(1.2 \times 0.75) - (-0.5 \times -0.5)}$$

$$V_2 = 9.39 \text{ V}$$

Q3) a)


$$\Phi = BA = 1.2 \times 1.613 \times 10^{-4} = 1.93 \times 10^{-4} \text{ Wb}$$

Q3) b)


$$H = \frac{NI}{l} = \frac{40 \text{ At}}{0.2 \text{ m}} = 200 \text{ At/m}$$

Q4)

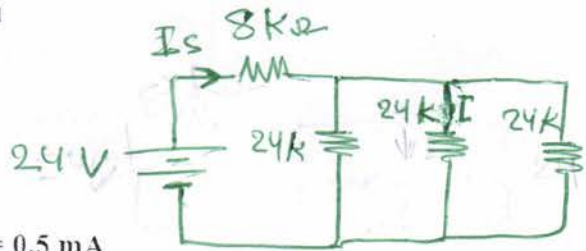a. $I_s = \frac{24 \text{ V}}{8 \text{ k}\Omega + \frac{24 \text{ k}\Omega}{3}} = 1.5 \text{ mA}, I = \frac{I_s}{3} = 0.5 \text{ mA}$



b.

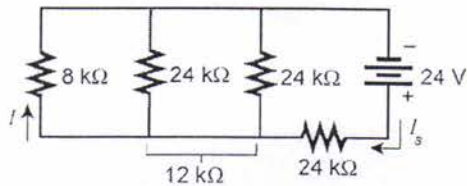


$$I_s = \frac{24 \text{ V}}{24 \text{ k}\Omega + 8 \text{ k}\Omega \parallel 12 \text{ k}\Omega} = 0.83 \text{ mA}$$

$$I = \frac{12 \text{ k}\Omega(I_s)}{12 \text{ k}\Omega + 8 \text{ k}\Omega} = 0.5 \text{ mA}$$

c. yes

Q5)

$\Delta \rightarrow Y$

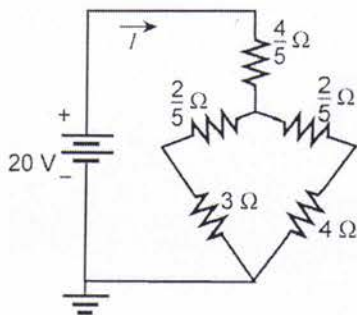

$$I = \frac{20 \text{ V}}{\frac{4}{5} \Omega + \left[\frac{2}{5} \Omega + 3 \Omega \right] \parallel \left[\frac{2}{5} \Omega + 4 \Omega \right]}$$

$$= \frac{20 \text{ V}}{\frac{4}{5} \Omega + (3.14 \Omega) \parallel (4.4 \Omega)}$$

$$= 7.36 \text{ A}$$

- Q4) a. For the network in Fig. (3-a) determine the current(I).
 b. Repeat part (a) for the network in Fig. (3-b)
 c. Is the reciprocity theorem satisfied?

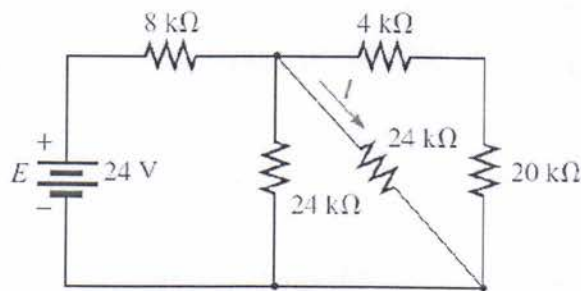


Fig.3-a

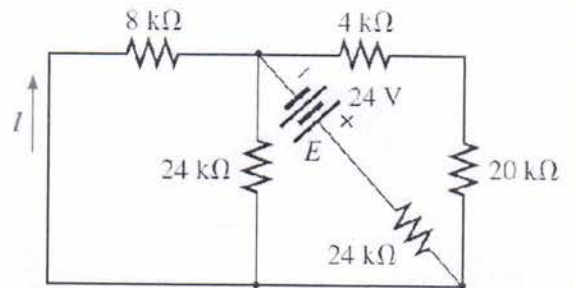


Fig 3-b

10 marks

- Q5) Using a Δ -Y or Y- Δ conversion, find the current(I) in the networks in Fig.(4)

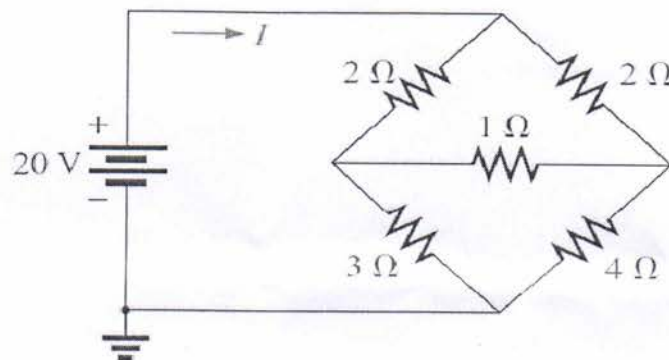


Fig. (4)

10 marks

- Q6) Find the indicated currents and voltages(I_s, I_2, I_4, V_1, V_5) for the network in Fig(5):


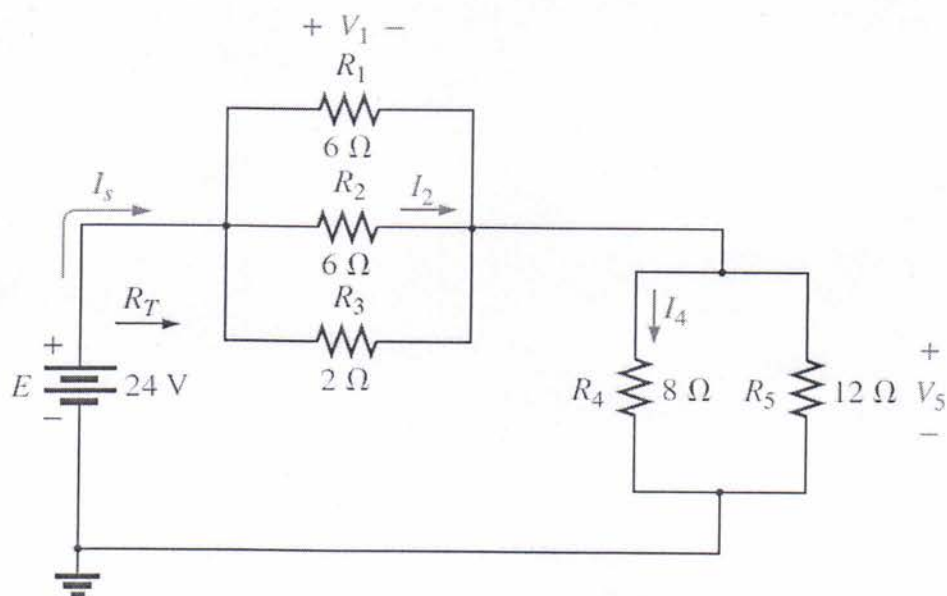


Fig. (5)

10 marks


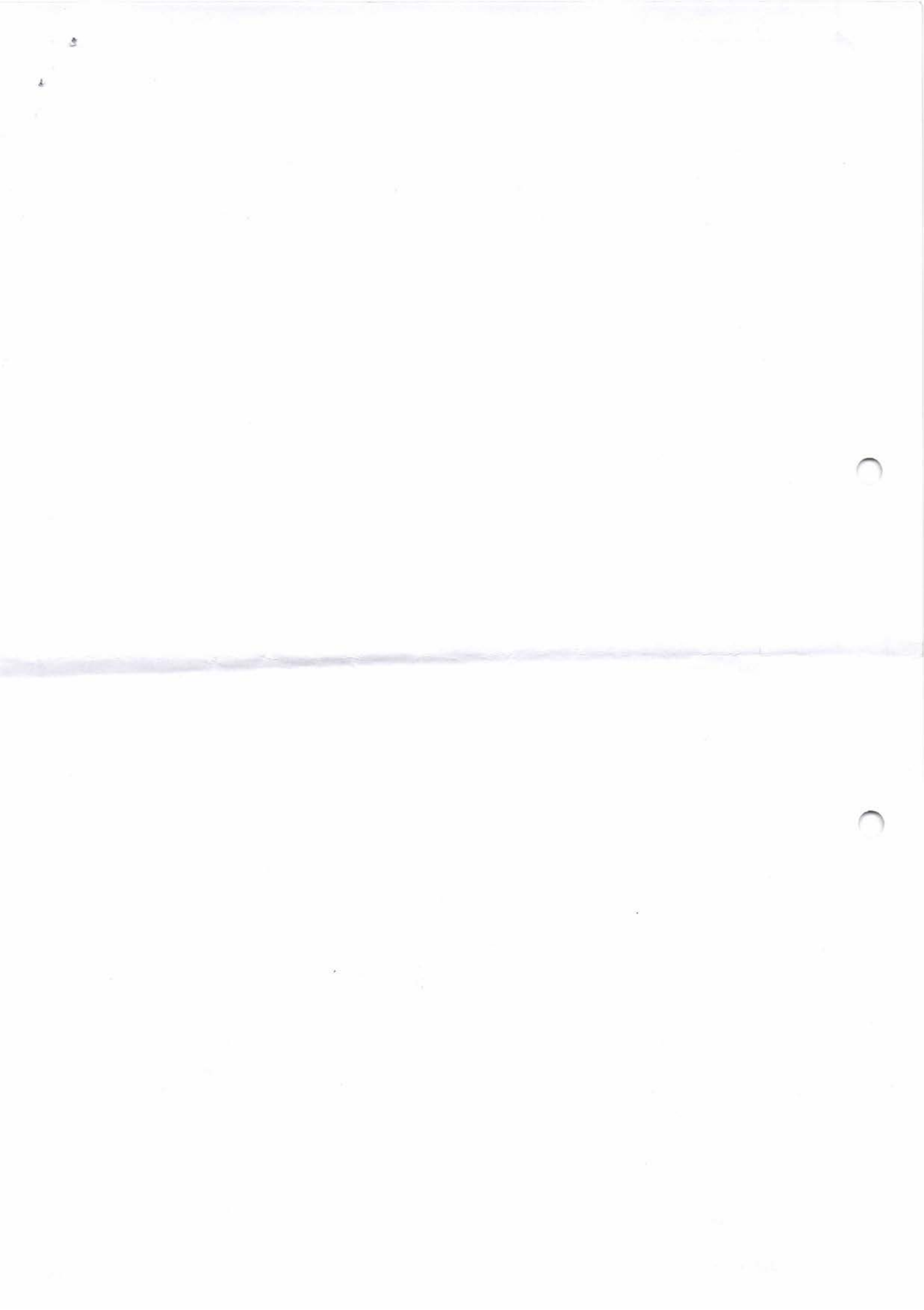


Q6)

$$R_{1||2} = \frac{R}{N} = \frac{6\ \Omega}{2} = 3\ \Omega$$

$$R_A = R_{1||2||3} = \frac{(3\ \Omega)(2\ \Omega)}{3\ \Omega + 2\ \Omega} = \frac{6\ \Omega}{5} = 1.2\ \Omega$$

$$R_B = R_{4||5} = \frac{(8\ \Omega)(12\ \Omega)}{8\ \Omega + 12\ \Omega} = \frac{96\ \Omega}{20} = 4.8\ \Omega$$

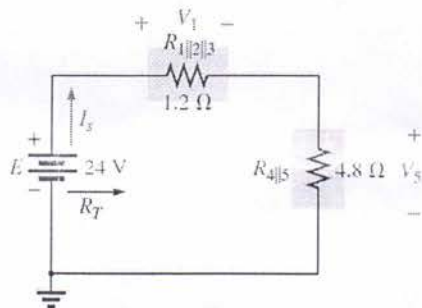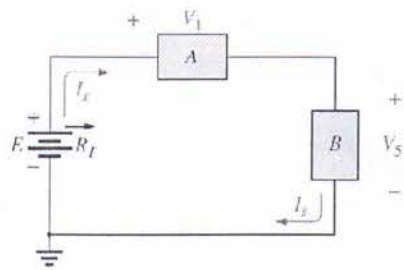

$$R_T = R_{1||2||3} + R_{4||5} = 1.2\ \Omega + 4.8\ \Omega = 6\ \Omega$$

$$I_s = \frac{E}{R_T} = \frac{24\text{ V}}{6\ \Omega} = 4\text{ A}$$

$$V_1 = I_s R_{1||2||3} = (4\text{ A})(1.2\ \Omega) = 4.8\text{ V}$$

$$V_5 = I_s R_{4||5} = (4\text{ A})(4.8\ \Omega) = 19.2\text{ V}$$

Applying Ohm's law,

$$I_4 = \frac{V_5}{R_4} = \frac{19.2\text{ V}}{8\ \Omega} = 2.4\text{ A}$$

$$I_2 = \frac{V_2}{R_2} = \frac{V_1}{R_2} = \frac{4.8\text{ V}}{6\ \Omega} = 0.8\text{ A}$$

