



Attempt five questions only

Q1) a: Find the rms values and ω and θ of the following sinusoidal waveforms:

1. $v = 140 \sin(377t + 60^\circ)$ 2. $i = 6 \times 10^{-3} \sin(2\pi 1000t)$

b: Determine the frequency at which a $1 \mu\text{F}$ capacitor and a 10 mH inductor will have the same reactance.

10 marks

Q2) For the network in Fig. (1):

- Find the total impedance Z_T and the total admittance Y_T .
- Find the current I_s .
- Calculate I_2 using the current divider rule.
- Calculate V_C .
- Calculate the average power delivered to the network

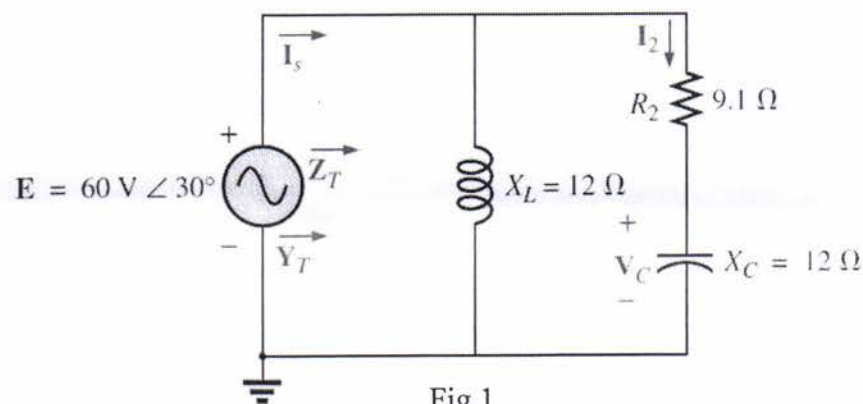


Fig.1

10 marks

Q3) Using the Δ -Y or Y- Δ conversion, determine the current (I) for the network in Fig. (2).

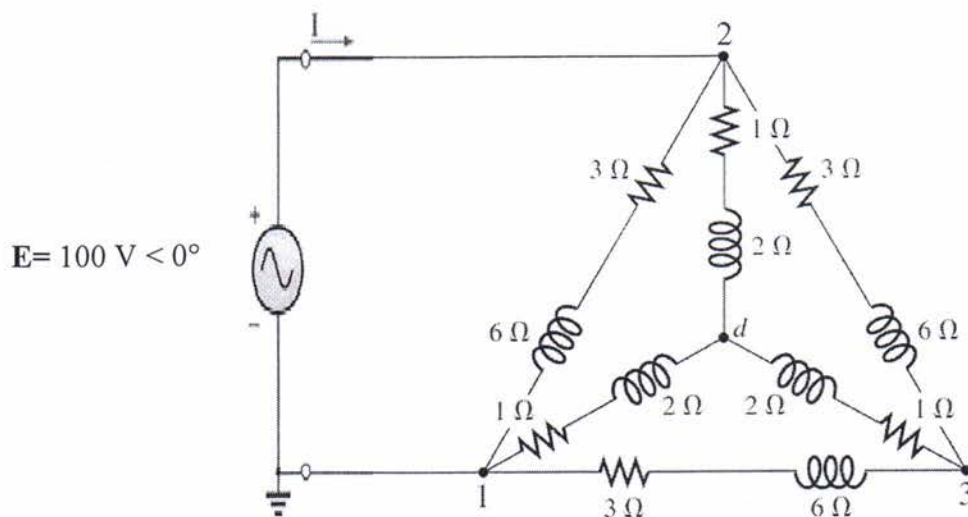


Fig.2

10 marks

Q4) Find the Thévenin equivalent circuit for the network external to branch $a-a'$ in Fig.(3)

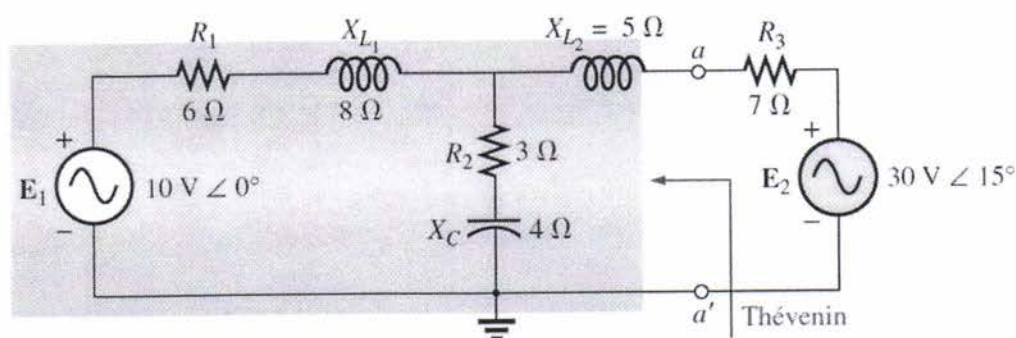


Fig.3

10 marks

Q5) Given $R = 20 \text{ k}\Omega$ and $C = 1200 \text{ pF}$

- Sketch the normalized plot if the filter is used as a high-pass filter.
- Sketch the phase plot for high-pass filter.
- Determine the magnitude and phase of $A_v = V_o / V_i$ at $(f = 1/2 f_c)$ for the high-pass filter.

10 marks

Q6) choose(a)or (b)

a) The bandwidth of a series resonant circuit is 400 Hz.

- If the resonant frequency is 4000 Hz, what is the value of Q_s ?
- If $R = 10 \Omega$, what is the value of XL at resonance?
- Find the inductance L and capacitance C of the circuit.

b) For the network in Fig. (4) with f_p provided:

- Determine Q_l .
- Determine R_p
- Calculate Z_{Tp}
- Find C at resonance.
- Find Q_p .

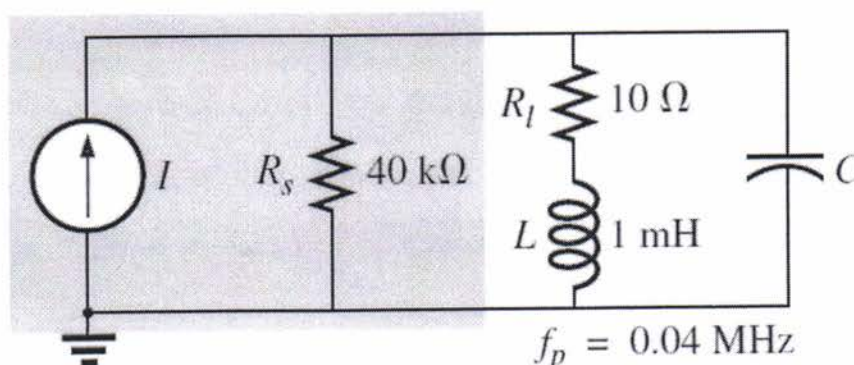


Fig.4

10 marks

Q1)a) $V_{rms} = 0.7071(140 \text{ V}) = 98.99 \text{ V}$, $\omega = 377$, $\theta = 60^\circ$
 $I_{rms} = 0.7071(6 \text{ mA}) = 4.24 \text{ mA}$, $\omega = 2\pi \times 1000 = 2000\pi$, $\theta = 0^\circ$

b)

$$X_C = X_L$$

$$\frac{1}{2\pi fC} = 2\pi fL$$

$$f^2 = \frac{1}{4\pi^2 LC}$$

$$\text{and } f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(10 \times 10^{-3} \text{ H})(1 \times 10^{-6} \text{ F})}} = 1.59 \text{ kHz}$$

Q2)

a. $Z_T = 12 \Omega \angle 90^\circ \parallel (9.1 \Omega - j12 \Omega) = 12 \Omega \angle 90^\circ \parallel 15.06 \Omega \angle -52.826^\circ$
 $= \frac{180.72 \Omega \angle 37.17^\circ}{9.10 \angle 0^\circ}$
 $= 19.86 \Omega \angle 37.17^\circ$
 $Y_T = \frac{1}{Z_T} = \frac{1}{19.86 \Omega \angle 37.17^\circ} = 50.35 \text{ mS} \angle -37.17^\circ$

b. $I_s = \frac{E}{Z_T} = \frac{60 \text{ V} \angle 30^\circ}{19.86 \Omega \angle 37.17^\circ} = 3.02 \text{ A} \angle -7.17^\circ$



c. $(\text{CDR}) I_2 = \frac{(12 \Omega \angle 90^\circ)(3.02 \text{ A} \angle -7.17^\circ)}{j12 \Omega + 9.1 \Omega - j12 \Omega} = \frac{36.24 \text{ A} \angle 82.83^\circ}{9.1 \angle 0^\circ}$
 $= 3.98 \text{ A} \angle 82.83^\circ$

d. $(\text{VDR}) V_C = \frac{(12 \Omega \angle -90^\circ)(60 \text{ V} \angle 30^\circ)}{9.1 \Omega - j12 \Omega} = \frac{720 \text{ V} \angle -60^\circ}{15.06 \angle -52.826^\circ}$
 $= 47.81 \text{ V} \angle -7.17^\circ$


e. $P = EI \cos \theta = (60 \text{ V})(3.02 \text{ A})\cos(30^\circ - 7.17^\circ)$
 $= 181.20(0.922) = 167.07 \text{ W}$

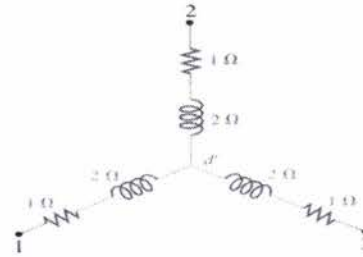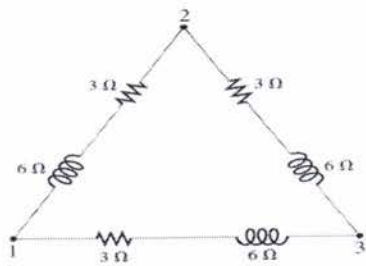Q3)

$$Z_Y = \frac{Z_\Delta}{3} = \frac{3 \Omega + j6 \Omega}{3} = 1 \Omega + j2 \Omega$$




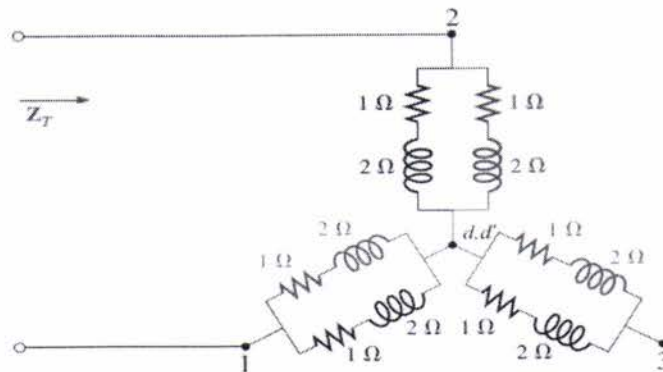
$$Z_T = 2 \left(\frac{1 \Omega + j 2 \Omega}{2} \right) = 1 \Omega + j 2 \Omega$$



Or

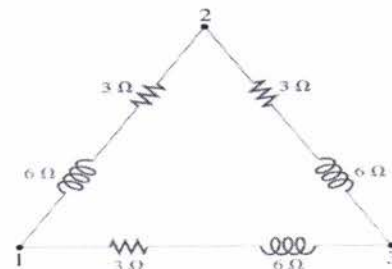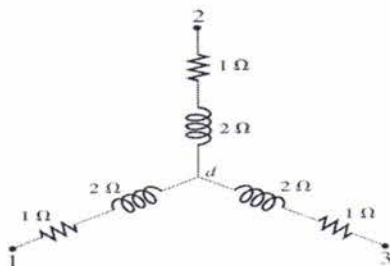
$$Z_{\Delta} = 3Z_Y = 3(1 \Omega + j 2 \Omega) = 3 \Omega + j 6 \Omega$$



$$Z' = \frac{3 \Omega + j 6 \Omega}{2} = 1.5 \Omega + j 3 \Omega$$

$$Z_T = \frac{Z' (2Z')}{Z' + 2Z'} = \frac{2(Z')^2}{3Z'} = \frac{2Z'}{3}$$
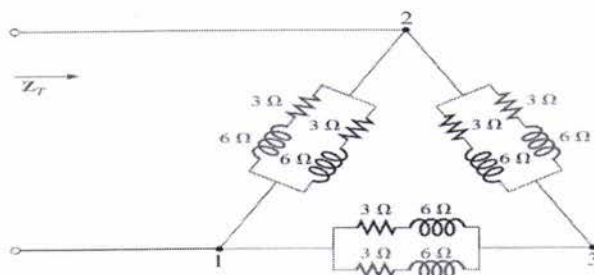
$$= \frac{2(1.5 \Omega + j 3 \Omega)}{3} = 1 \Omega + j 2 \Omega$$



$$Z_T = 1 + j2 \quad Z_T = 2.236 \angle 63.43^\circ$$

$$I = E/Z$$


$$I = \frac{100 \angle 0^\circ}{2.236 \angle 63.43^\circ} = 44.722 \angle -63.43^\circ \text{ A}$$

Q4)


$$Z_1 = R_1 + jX_{L_1} = 6 \Omega + j8 \Omega$$

$$Z_2 = R_2 - jX_C = 3 \Omega - j4 \Omega$$

$$Z_3 = +jX_{L_2} = j5 \Omega$$

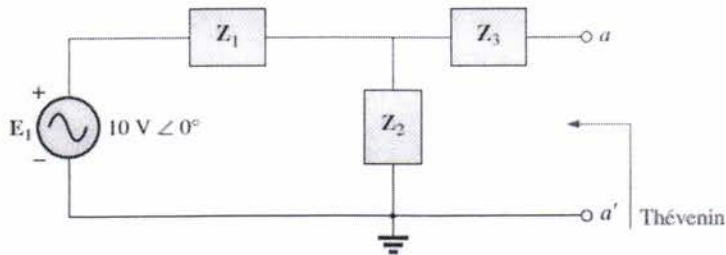


$$\begin{aligned} Z_{Th} &= Z_3 + \frac{Z_1 Z_2}{Z_1 + Z_2} = j5 \Omega + \frac{(10 \Omega \angle 53.13^\circ)(5 \Omega \angle -53.13^\circ)}{(6 \Omega + j8 \Omega) + (3 \Omega - j4 \Omega)} \\ &= j5 + \frac{50 \angle 0^\circ}{9 + j4} = j5 + \frac{50 \angle 0^\circ}{9.85 \angle 23.96^\circ} \\ &= j5 + 5.08 \angle -23.96^\circ = j5 + 4.64 - j2.06 \\ Z_{Th} &= 4.64 \Omega + j2.94 \Omega = 5.49 \Omega \angle 32.36^\circ \end{aligned}$$

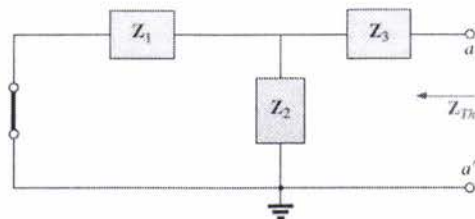


$$E_{Th} = \frac{Z_3 E}{Z_2 + Z_3} \quad (\text{voltage divider rule})$$

$$= \frac{(5 \Omega \angle -53.13^\circ)(10 \text{ V} \angle 0^\circ)}{9.85 \Omega \angle 23.96^\circ}$$
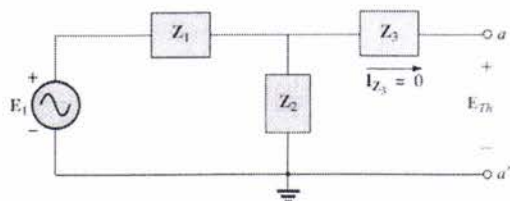
$$E_{Th} = \frac{50 \text{ V} \angle -53.13^\circ}{9.85 \angle 23.96^\circ} = 5.08 \text{ V} \angle -77.09^\circ$$




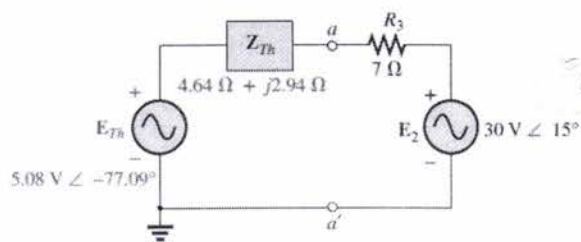


Q5)

$$\begin{aligned} \text{a. } f_c &= \frac{1}{2\pi RC} = \frac{1}{(2\pi)(20 \text{ k}\Omega)(1200 \text{ pF})} \\ &= 6631.46 \text{ Hz} \end{aligned}$$

a-

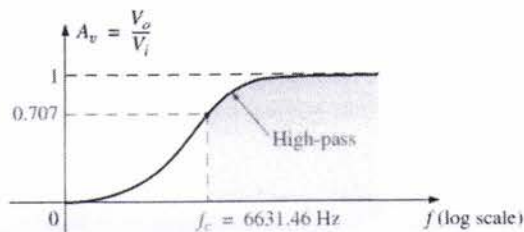

b-

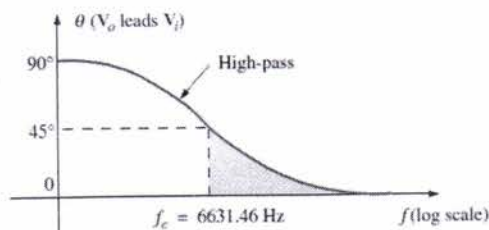

$$\text{c. } f = \frac{1}{2} f_c = \frac{1}{2} (6631.46 \text{ Hz}) = 3315.73 \text{ Hz}$$

$$\begin{aligned} X_C &= \frac{1}{2\pi f C} = \frac{1}{(2\pi)(3315.73 \text{ Hz})(1200 \text{ pF})} \\ &\cong 40 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} A_v = \frac{V_o}{V_i} &= \frac{1}{\sqrt{1 + \left(\frac{X_C}{R}\right)^2}} = \frac{1}{\sqrt{1 + \left(\frac{40 \text{ k}\Omega}{20 \text{ k}\Omega}\right)^2}} = \frac{1}{\sqrt{1 + (2)^2}} \\ &= \frac{1}{\sqrt{5}} = 0.4472 \end{aligned}$$

$$\theta = \tan^{-1} \frac{X_C}{R} = \tan^{-1} \frac{40 \text{ k}\Omega}{20 \text{ k}\Omega} = \tan^{-1} 2 = 63.43^\circ$$

$$\text{and } A_v = \frac{V_o}{V_i} = 0.447 \angle 63.43^\circ$$

Q6)

a)

$$1- BW = \frac{f_s}{Q_s} \quad \text{or} \quad Q_s = \frac{f_s}{BW} = \frac{4000 \text{ Hz}}{400 \text{ Hz}} = 10$$

$$2- Q_s = \frac{X_L}{R} \quad \text{or} \quad X_L = Q_s R = (10)(10 \Omega) = 100 \Omega$$

$$3- X_L = 2\pi f_s L \quad \text{or} \quad L = \frac{X_L}{2\pi f_s} = \frac{100 \Omega}{2\pi(4000 \text{ Hz})} = 3.98 \text{ mH}$$

$$3- X_C = \frac{1}{2\pi f_s C} \quad \text{or} \quad C = \frac{1}{2\pi f_s X_C} = \frac{1}{2\pi(4000 \text{ Hz})(100 \Omega)} \\ = 397.89 \text{ nF}$$

b)

$$1- Q_l = \frac{X_L}{R_l} = \frac{2\pi f_p L}{R_l} = \frac{2\pi(0.04 \text{ MHz})(1 \text{ mH})}{10 \Omega} = 25.12$$

$$2- Q_l \geq 10. \text{ Therefore,}$$

$$R_p \cong Q_l^2 R_l = (25.12)^2 (10 \Omega) = 6.31 \text{ k}\Omega$$

$$3- Z_{T_p} = R_s \parallel R_p = 40 \text{ k}\Omega \parallel 6.31 \text{ k}\Omega = 5.45 \text{ k}\Omega$$

$$4- Q_l \geq 10. \text{ Therefore,}$$

$$f_p \cong \frac{1}{2\pi\sqrt{LC}}$$

$$\text{and} \quad C = \frac{1}{4\pi^2 f^2 L} = \frac{1}{4\pi^2 (0.04 \text{ MHz})^2 (1 \text{ mH})} = 15.83 \text{ nF}$$

$$5- Q_l \geq 10. \text{ Therefore,}$$

$$Q_p = \frac{Z_{T_p}}{X_L} = \frac{R_s \parallel R_p \parallel Q_l^2 R_l}{2\pi f_p L} = \frac{5.45 \text{ k}\Omega}{2\pi(0.04 \text{ MHz})(1 \text{ mH})} = 21.68$$

1
2
3

1
2
3

1