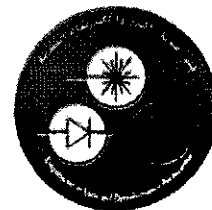


University of Technology
Department of Laser & Optoelectronics Engineering
Final Examination 2011-2012

Subject: Electrical A.C Circuits
Division: Laser & optoelectronics Eng.
Examiner: Dr. Salah Aldeen Adnan

Class: 2nd year
Time: 3 hours
Date: 28 / 5 / 2012



Answer only five questions

Q.1:For the series parallel circuit of Fig.(1), the parallel elements is at resonance .

- a. Calculate I , V_R , V_L , and V_C in Phasor form.
- b. Calculate the total power factor.
- c. Calculate the average power delivered to the circuit.
- d. Draw the Phasor diagram.
- e. Obtain the Phasor sum of V_R , V_L , and V_C , and show that it equals the input voltage E .
- f. Find V_R and V_C using the voltage divider rule.


Q.2:Redesign a parallel resonance cct. to have the response curve of fig. (2) , using 2mH,100 Ω inductor .

Q.3:Calculate the magnetic flux (Φ) for the magnetic circuit of figure (3) where the flux density of cast iron is 0.39T .

Q.4:Find the voltage V_{AB} of Fig.(4) by nodal theorem .

Q.5:Sketch the output voltage V_0 versus frequency for the R-L filter of Fig.(5) , and Determine the voltage V_0 at $F = 100\text{kHz}$ and 1MHz ,where $R=10\Omega$ and $L = 1\text{mH}$.

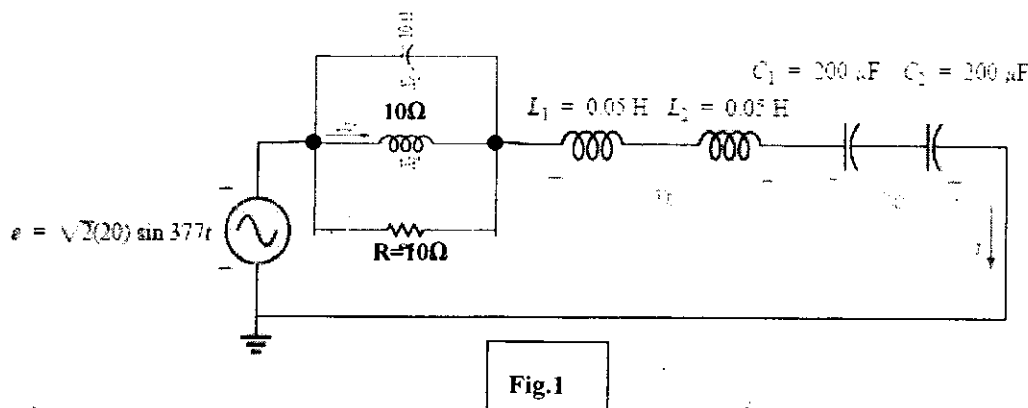Q.6:Find the equivalent circuit for each current locus diagram shown in Fig.(6).



أقلب الصفحة ←

good Luck V.1

S
R...

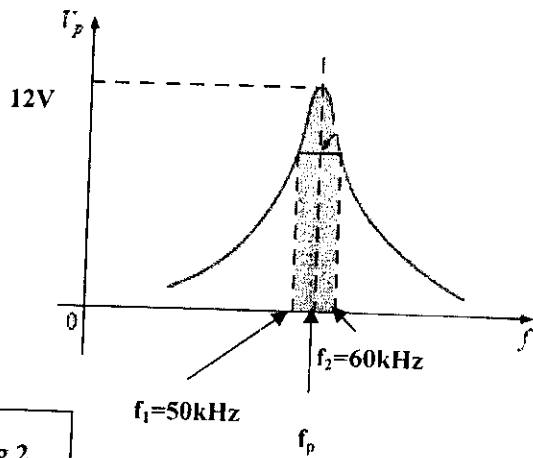


Fig.2

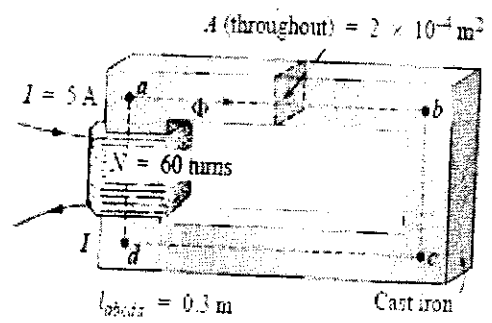


Fig.3

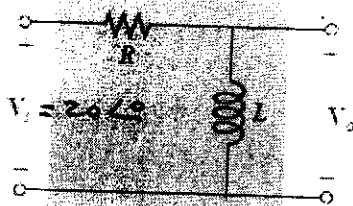


Fig.5

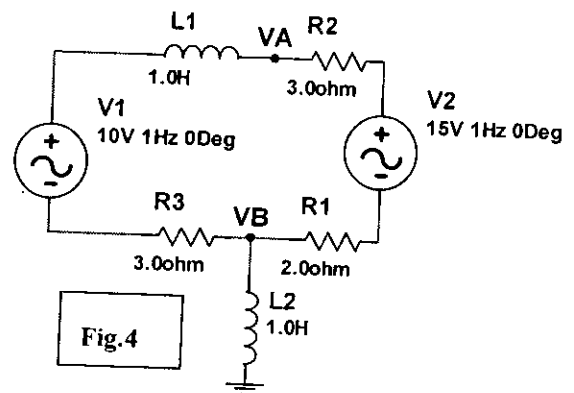


Fig.4

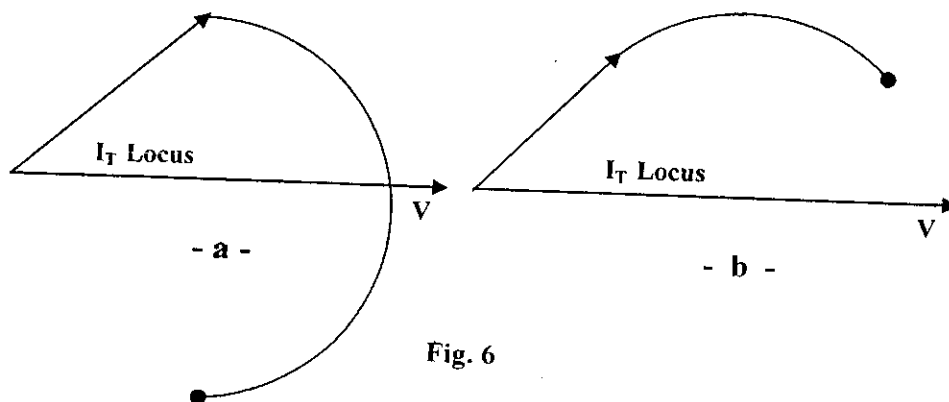


Fig. 6

Acc. cct. (v-1)

Q.1

for (Laser + optoelectronic)

Q.1

$$R_T = 6 \Omega + 4 \Omega = 10 \Omega$$

$$L_T = 0.05 \text{ H} + 0.05 \text{ H} = 0.1 \text{ H}$$

$$C_T = \frac{200 \mu\text{F}}{2} = 100 \mu\text{F}$$

$$X_L = \omega L = (377 \text{ rad/s})(0.1 \text{ H}) = 37.70 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(377 \text{ rad/s})(100 \times 10^{-6} \text{ F})} = \frac{10^6 \Omega}{37,700} = 26.53 \Omega$$

Redrawing the circuit using phasor notation results in Fig. 15.43.

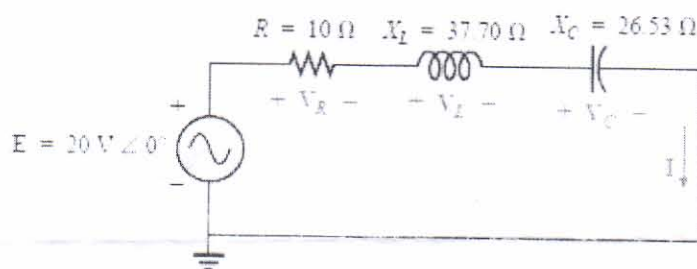


FIG. 15.43

Applying phasor notation to the circuit of Fig. 15.42.

For the circuit of Fig. 15.43.

$$\begin{aligned} Z_T &= R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ \\ &= 10 \Omega + j 37.70 \Omega - j 26.53 \Omega \\ &= 10 \Omega + j 11.17 \Omega = 15 \Omega \angle 48.16^\circ \end{aligned}$$

The current I is

$$I = \frac{E}{Z_T} = \frac{20 \text{ V} \angle 0^\circ}{15 \Omega \angle 48.16^\circ} = 1.33 \text{ A} \angle -48.16^\circ$$

The voltage across the resistor, inductor, and capacitor can be found using Ohm's law:

$$\begin{aligned} V_R &= I Z_R = (I \angle \theta)(R \angle 0^\circ) = (1.33 \text{ A} \angle -48.16^\circ)(10 \Omega \angle 0^\circ) \\ &= 13.30 \text{ V} \angle -48.16^\circ \end{aligned}$$

$$\begin{aligned} V_L &= I Z_L = (I \angle \theta)(X_L \angle 90^\circ) = (1.33 \text{ A} \angle -48.16^\circ)(37.70 \Omega \angle 90^\circ) \\ &= 50.14 \text{ V} \angle 41.84^\circ \end{aligned}$$

$$\begin{aligned} V_C &= I Z_C = (I \angle \theta)(X_C \angle -90^\circ) = (1.33 \text{ A} \angle -48.16^\circ)(26.53 \Omega \angle -90^\circ) \\ &= 35.28 \text{ V} \angle -138.16^\circ \end{aligned}$$

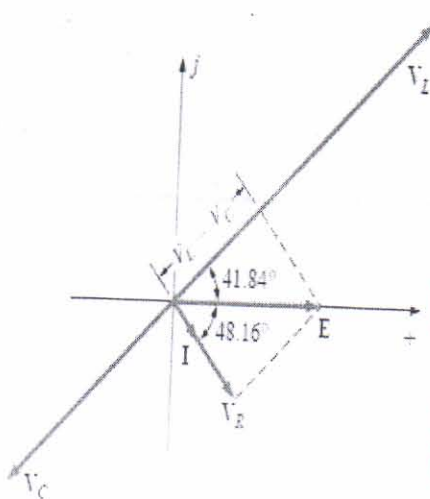


FIG. 15.44
Phasor diagram for the circuit of Fig. 15.42.

- b. The total power factor, determined by the angle between the applied voltage E and the resulting current I , is 48.16° :

$$F_p = \cos \theta = \cos 48.16^\circ = 0.667 \text{ lagging}$$

or
$$F_p = \cos \theta = \frac{R}{Z_T} = \frac{10 \Omega}{15 \Omega} = 0.667 \text{ lagging}$$

- c. The total power in watts delivered to the circuit is

$$P_T = EI \cos \theta = (20 \text{ V})(1.33 \text{ A})(0.667) = 17.74 \text{ W}$$

- d. The phasor diagram appears in Fig. 15.44.

- e. The phasor sum of V_R , V_L , and V_C is

$$\begin{aligned} E &= V_R + V_L + V_C \\ &= 13.30 \text{ V} \angle -48.16^\circ + 50.14 \text{ V} \angle 41.84^\circ + 35.28 \text{ V} \angle -138.16^\circ \\ E &= 13.30 \text{ V} \angle -48.16^\circ + 14.86 \text{ V} \angle 41.84^\circ \end{aligned}$$

Therefore,

$$E = \sqrt{(13.30 \text{ V})^2 + (14.86 \text{ V})^2} = 20 \text{ V}$$

and $\theta_E = 0^\circ$ (from phasor diagram)

and $E = 20 \angle 0^\circ$

f.
$$V_R = \frac{Z_R E}{Z_T} = \frac{(10 \Omega \angle 0^\circ)(20 \text{ V} \angle 0^\circ)}{15 \Omega \angle 48.16^\circ} = \frac{200 \text{ V} \angle 0^\circ}{15 \angle 48.16^\circ}$$

$$= 13.3 \text{ V} \angle -48.16^\circ$$

$$\begin{aligned} V_C &= \frac{Z_C E}{Z_T} = \frac{(26.5 \Omega \angle -90^\circ)(20 \text{ V} \angle 0^\circ)}{15 \Omega \angle 48.16^\circ} = \frac{530.6 \text{ V} \angle -90^\circ}{15 \angle 48.16^\circ} \\ &= 35.37 \text{ V} \angle -138.16^\circ \end{aligned}$$

Q.2


① AC-coupled

Q.1: Redesign a parallel resonance circuit to have the response curve of fig. (), using $2\mu\text{H}$, 100Ω inductor?

$$f_1 = 50\text{kHz}, f_2 = 60\text{kHz}$$

$$\text{BW} = 60\text{K} - 50\text{K} = 10\text{kHz}$$

$$\frac{\text{BW}}{2} = 5\text{kHz}$$

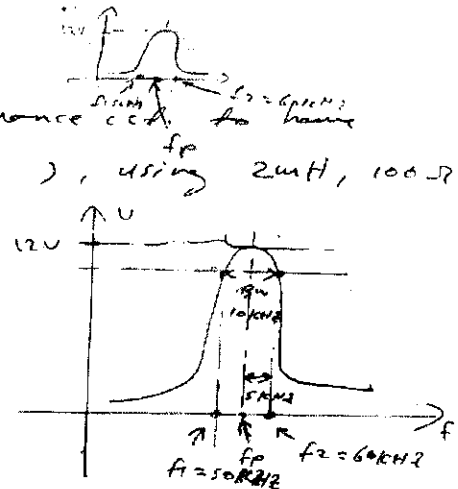

① $f_p = 60\text{K} - 5\text{K} = 55\text{kHz}$

② $Q_p = \frac{f_p}{\text{BW}} = \frac{55\text{kHz}}{10\text{K}} = 5.5$

③ $X_L = 2\pi f_p L = 2\pi \times 55 \times 10^3 \times 2 \times 10^{-6} = 691\Omega$

④ $Q_1 = \frac{X_L}{R_1} = \frac{691}{100} = 6.91 < 10$


Q_1 must be ≥ 10 , because max. current or impedance at resonant frequency (f_p) and because $f_p = f_m = f_s$

~~if $Q_1 < 10$~~ $Q_1 = 10$ $\therefore R_1 = \frac{X_L}{Q_1} = \frac{691}{10} = 69.1\Omega$

\therefore we must add another resistance (\bar{R}_1) in parallel with (R_1) to reduce R_1 to (69.1Ω).

$$69.1 = \frac{100 \times \bar{R}_1}{100 + \bar{R}_1} \rightarrow 6910 + 69.1 \bar{R}_1 = 100 \bar{R}_1$$
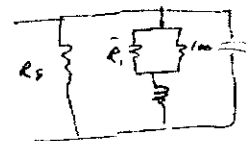
$$6910 = 30.9 \bar{R}_1 \quad \therefore \bar{R}_1 = 223.6\Omega$$



(5) $Q_1 = 10$

$\therefore X_{LP} = X_L = X_C = 691$

$f_s = f_p = f_m = 55 \text{ kHz}$

$R_p = Q_1^2 \cdot R_1$
 $= (10)^2 \cdot X_{LP} = 6910 \Omega$


(6) $Q_p = \frac{R}{X_{LP}} = \frac{R}{X_C} = \frac{R_s // R_p}{X_C}$

$Q_p = \frac{\frac{R_s \cdot R_p}{R_s + R_p}}{X_C}$

$5.5 = \frac{\frac{6910 R_s}{R_s + 6910}}{691}$

$3.8 \times 10^3 = \frac{6910 R_s}{R_s + 6910}$

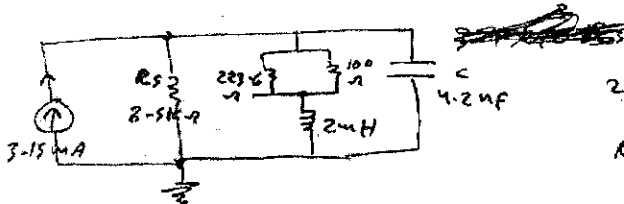$3.8 \times 10^3 R_s + 26.3 \times 10^6 = 6910 R_s$



$26.3 \times 10^6 = 3110 R_s$
 $R_s = \frac{26.3 \times 10^6}{3110}$

(7) $R_s = 8.5 \text{ k}\Omega$
 $X_C = \frac{1}{2\pi f C} = X_L = 691 \Omega$

(8) $C = \frac{1}{2\pi \times 55 \times 10^3 \times 691} = 4.2 \text{ nF}$ or $C = \frac{L}{R_s \cdot R_p} = 4.2 \text{ nF}$

(9) $I = V_p / Z_{TP} \rightarrow Z_{TP} = R_s // R_p = \frac{R_s \cdot R_p}{R_s + R_p}$

$Z_{TP} = \frac{8.5 \times 10^3 \times 6.91 \text{ k}}{8.5 \text{ k} + 6.91 \text{ k}} = 3.81 \text{ k}\Omega$

$I = 12 / 3.81 \text{ k}\Omega = 3.15 \text{ mA}$

Q.3

Solution: By Ampère's circuital law,

$$NI = H_{abcd} l_{abcd}$$

or

$$H_{abcd} = \frac{NI}{l_{abcd}} = \frac{(60)(5 \text{ A})}{0.3 \text{ m}} \\ = \frac{300 \text{ At}}{0.3 \text{ m}} = 1000 \text{ At/m}$$

and

$$B_{abcd} \text{ (from Fig. 11.23)} = 0.39 \text{ T}$$

Since $B = \Phi/\mathcal{A}$, we have

$$\Phi = B\mathcal{A} = (0.39 \text{ T})(2 \times 10^{-4} \text{ m}^2) = 0.78 \times 10^{-4} \text{ Wb}$$

Q.4


$$\underline{Q.4} = \frac{\text{BY NODAL}}{V_A - 10 - V_B = \frac{V_B + 15 - V_A}{5} = I \rightarrow (1)}$$

$$\frac{V_B}{j24\pi} = \frac{I}{1} \rightarrow (2)$$

$$V_A = ? \quad V_B = ?$$

$$V_{AB} = V_A - V_B$$

طریقه انجری
غیر ال
(NODAL)

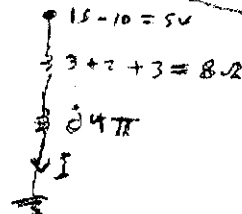


$$I = \frac{5}{8 + j4}$$

APF

$$\underline{Q.5} :- f_c = \frac{R}{2\pi L}$$

$$V_0 = ? \text{ at } f = 100 \text{ kHz}$$
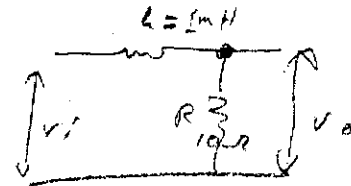
$$\text{anal } 1 \text{ MHz} \quad \text{or } 20 \text{ L}$$



$$V_0 = V_i \frac{X_C}{R + jX_C} = \frac{V_i X_C}{\sqrt{R^2 + X_C^2}} = \frac{V_i}{\sqrt{\left(\frac{R}{X_C}\right)^2 + 1}}$$

$$X_C = 2\pi f L \quad f_c = \frac{10}{2\pi \times 10^{-3}} = 1.6 \text{ kHz}$$



$$1) f = 100 \times 10^3 \quad X_C = 2\pi \times 100 \times 10^3 \times 10^{-3} = 628.3 \Omega$$

$$V_0 = \frac{20}{\sqrt{\left(\frac{10}{628.3}\right)^2 + 1}} = 20 \angle 0.2^\circ$$

$$2) f = 10^6 \text{ Hz}$$


$$X_C = 6283.1 \Omega$$

$$V_0 = 19.9 \angle -0.2^\circ$$

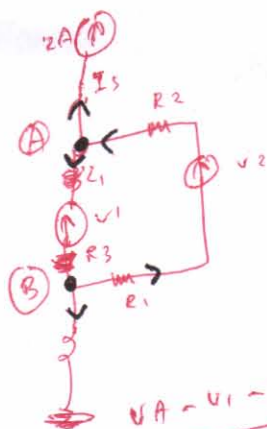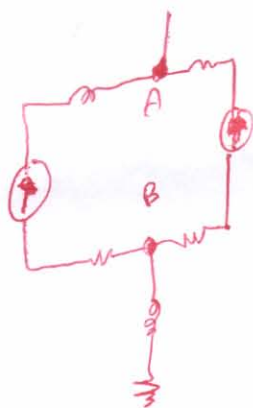


$$\frac{V_A - V_1 - V_B}{L_1 + R_3} + I_S = \frac{V_B + V_2 - V_A}{R_1 + R_2}$$

Q.6

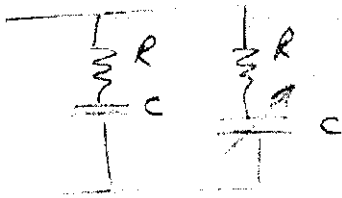

(a)

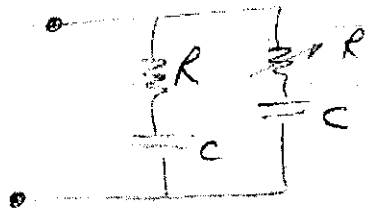

(b)