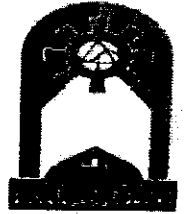


University of Technology
Department of Laser & Optoelectronics Engineering
Final Examination 2011/2012



Subject: Electronic I
Division: Laser & Optoelectronics
Examiner: Assist. Lec. Ahmed Chyad

Class: Second year
Time: 3 hours
Date: 3/6/2012

Answer only Five Questions

Q1:(A) Determine I_D , V_{D2} , and V_o for the circuit of Fig. 1.

(B) (a) For the Zener diode network of Fig. 2, determine V_L , V_R , I_Z , and P_Z .

(b) Repeat part (a) with $R_L = 3 \text{ k}\Omega$.

Q2: A full-wave bridge rectifier with a 120V rms sinusoidal input has a load resistor of 1 k Ω .

(a) If silicon diodes are employed, what is the dc voltage available at the load?

(b) Determine the required PIV rating of each diode.

(c) Find the maximum current through each diode during conduction.

(d) What is the required power rating of each diode?

Q3:(A) Sketch v_o for each network of Fig. 3. for the input shown.

(B) Determine v_o and the required PIV rating of each diode for the configuration of Fig. 4.

Q4: For the emitter bias network of Fig. 5, determine: I_B , I_C , V_{CE} , V_C , V_E , and V_B .

Q5: For the network of Fig. 6. determine: V_{GSQ} , I_{DQ} , V_{DS} , V_S , V_G and V_D .

Q6: For the network of Fig. 7, determine: r_e , Z_i , Z_o , A_i , and A_v .

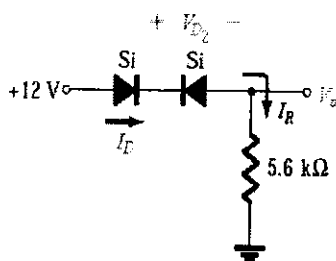


Fig. 1.

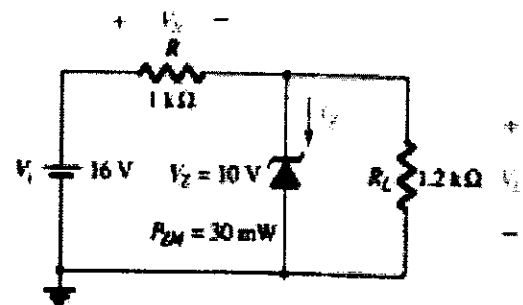


Fig. 2.

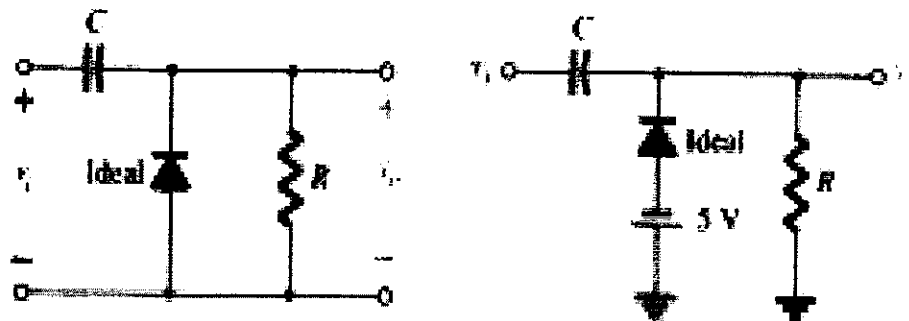
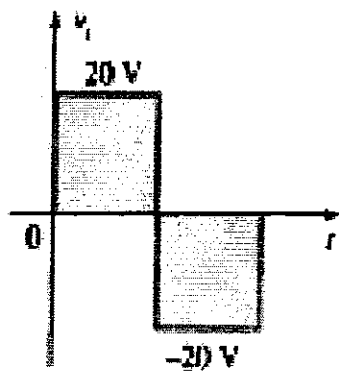


Fig. 3.

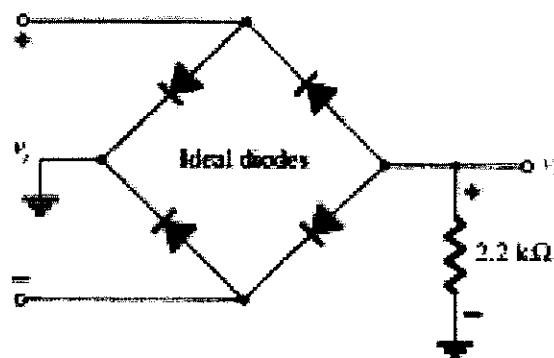
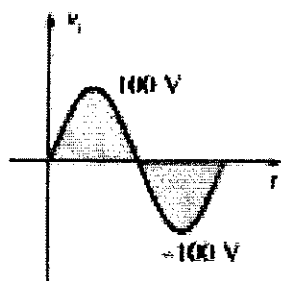


Fig. 4.

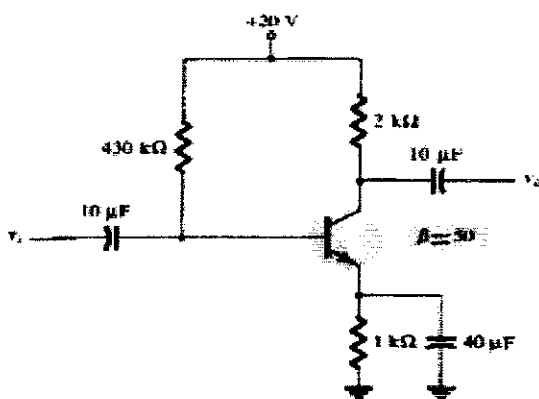


Fig. 5

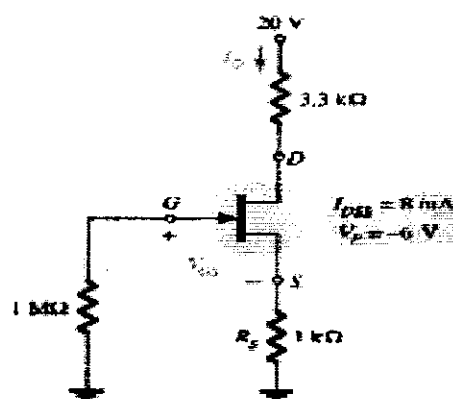


Fig. 6

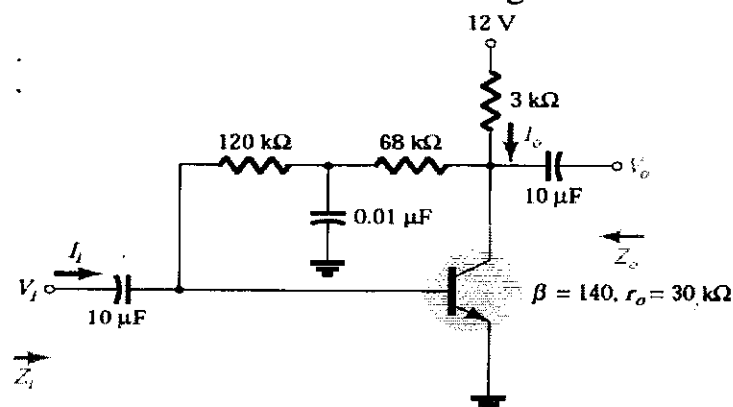


Fig. 7.

Handwritten signature and date: 20.1

حل المسألة الأولى



$$I_D = 0, V_{D2} = 12 - 0.7 = 11.3 \text{ V}$$

$$V_D = 0$$

$$(B) \quad V_L = 16 \times \frac{1.2}{2.2} = 8.73 \text{ Volt.}$$

$$P_Z = 30 \text{ mW}$$

$\therefore V_L < V_Z$ \therefore appear as ~~short~~ ^{open} circuit.

$$\therefore V_L = 8.73 \text{ Volt.}, V_R = V_L = 8.73 \text{ Volt.}$$

$$I_Z = 0, P_Z = I_Z \cdot V_Z = 0.$$

$$(b) \quad V_L = 16 \cdot \frac{3}{4} = 12 \text{ Volt.}$$

$\therefore V_L > V_Z$ The Zener diode appears as voltage source.

$$\therefore V_L = V_R = V_Z = 10 \text{ V}$$

$$I_R = \frac{10}{1.2} = 8.33 \text{ mA}, I_i = \frac{16 - 10}{1} = 6 \text{ mA}$$

$$\therefore I_Z = I_i - I_R \approx 5 \text{ mA}$$

$$\therefore P_Z = V_Z I_Z = 10 \times 5 = 50 \text{ mW}$$

Q₂

$V_{rms} = 120 \text{ V Sin wave}$

$$R_L = 1 \text{ k}\Omega$$

$$\textcircled{a} V_{dc} = 0.328 V_m \rightarrow V_m = \frac{120}{\sqrt{2}} = \frac{100.7}{\sqrt{2}} \text{ Volt.}$$

or








$$V_{dc} = 0.328 (V_m - 2(0.7)) = 0.328 (100.7 - 2(0.7))$$

$$\therefore V_{dc} = 5.4 \text{ Volt.}$$

$$\textcircled{b} P_{IV} = V_m = 100.7.$$


$$\textcircled{c} I_m = \frac{V_m - 1.4}{1 \text{ k}\Omega} = \frac{100.7 - 1.4}{1 \text{ k}\Omega} = 99.7 \text{ mA}$$
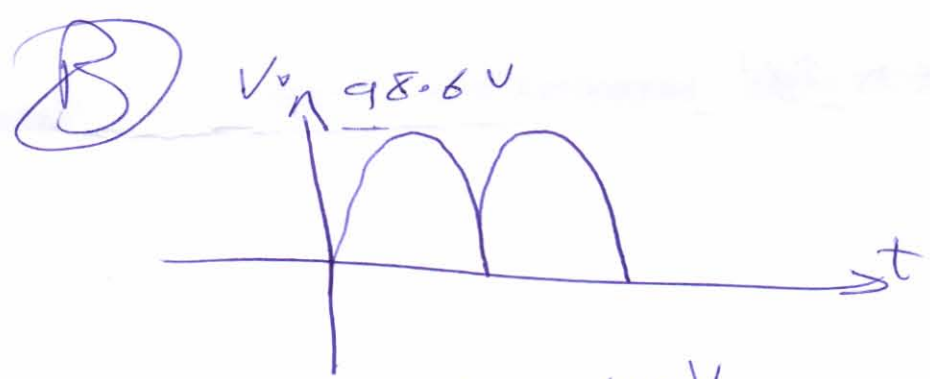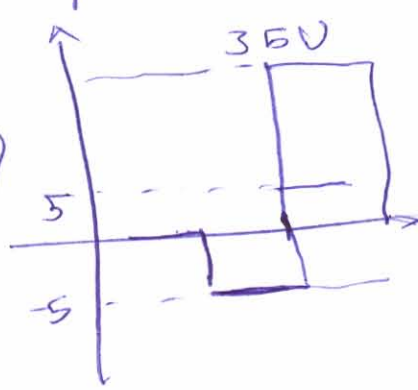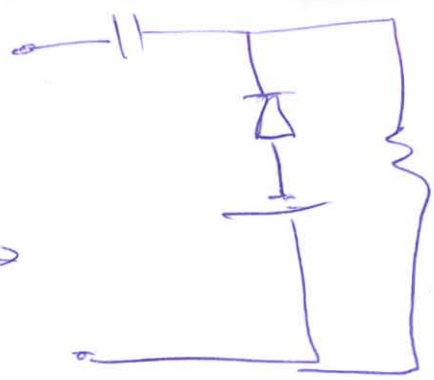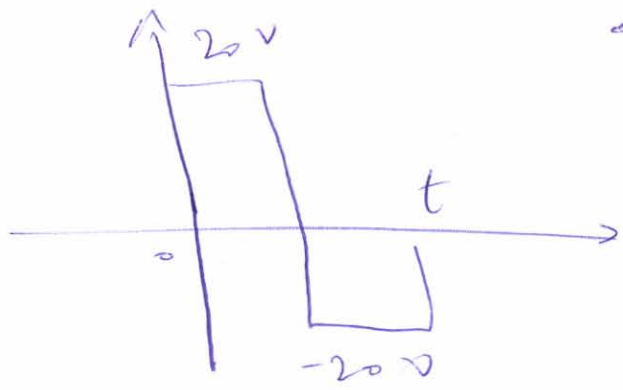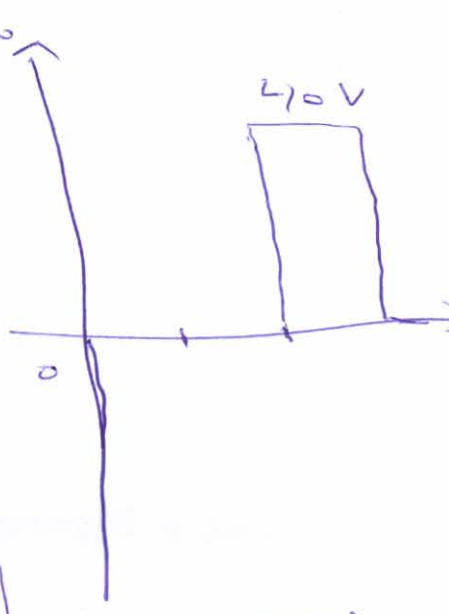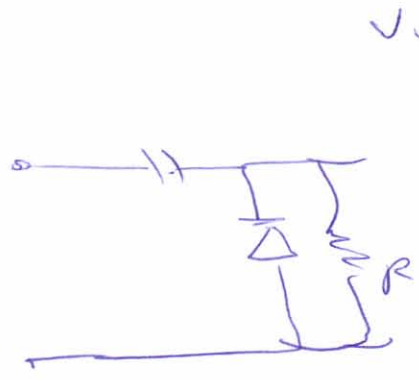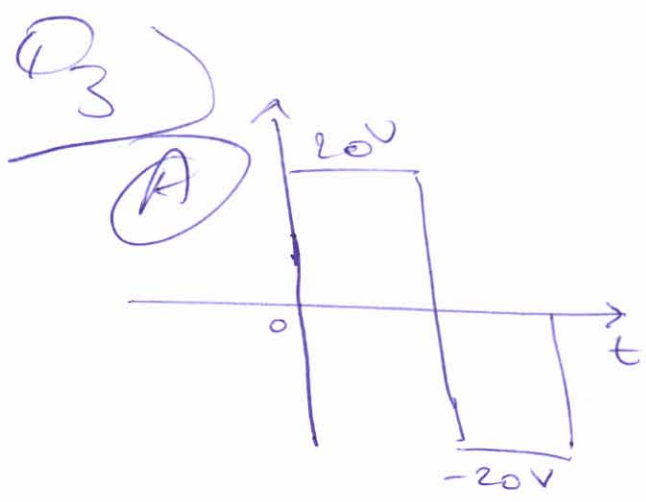
$$\textcircled{d} P_D = V_D I_D = 0.7 * I_m = \underline{88.7 \text{ mW}}$$



$P_{IV} = V_m = 100V$

Q4) $I_B, I_C, V_{CE}, V_C, V_E, V_B$

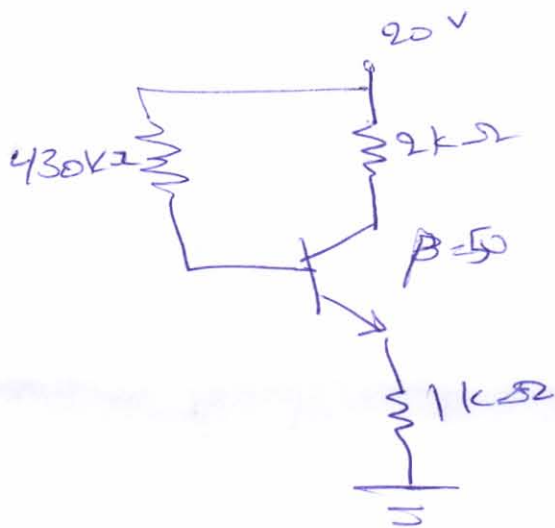

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_E = (1 + \beta) I_B$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta) R_E}$$

$$I_B = \frac{19.3}{430k + (51)1k} = \frac{19.3}{481k}$$

$$\therefore I_B = 40 \mu A \Rightarrow I_E = (1 + \beta) I_B$$

$$\therefore I_E = 51 \times 40 \mu A = 2 \text{ mA}$$

$$I_C \approx I_E = 2 \text{ mA}$$

$$V_E = I_E R_E = 2 \times 1 = 2 \text{ Volt}$$

$$V_B = V_{BE} + V_E = 0.7 + 2 = 2.7 \text{ Volt}$$

$$V_C = V_{CC} - I_C R_C = 20 - 4 = 16 \text{ Volt}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$= 20 - 4 - 2 = 14 \text{ Volt}$$


Q5 $V_{GSQ}, I_{DQ}, V_{DS}, V_S, V_G, V_D$

$$I_G \approx 0$$

$$V_G = I_G R_G = 0$$

$$V_{GS} = V_G - V_S$$

$$= 0 - I_D R_S$$

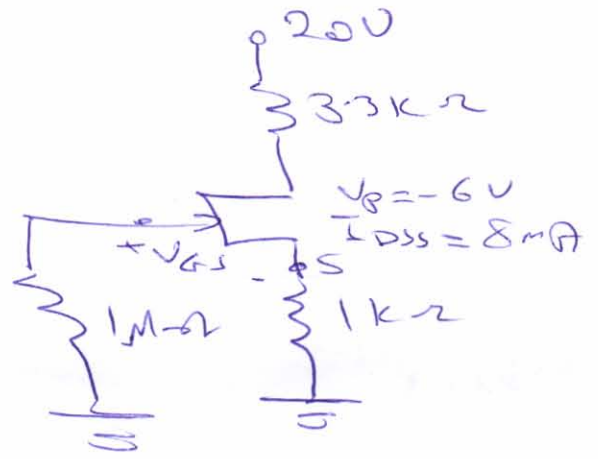


$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

if $I_D = 0$ $V_{GS} = 0$

if $V_{GS} = V_P$

$$I_D = \frac{6}{1k\Omega} = 6mA$$

V_{GS}	$I_D (mA)$
0	$I_{DSS} = 8$
-1.8	4
-3	2
-6	0

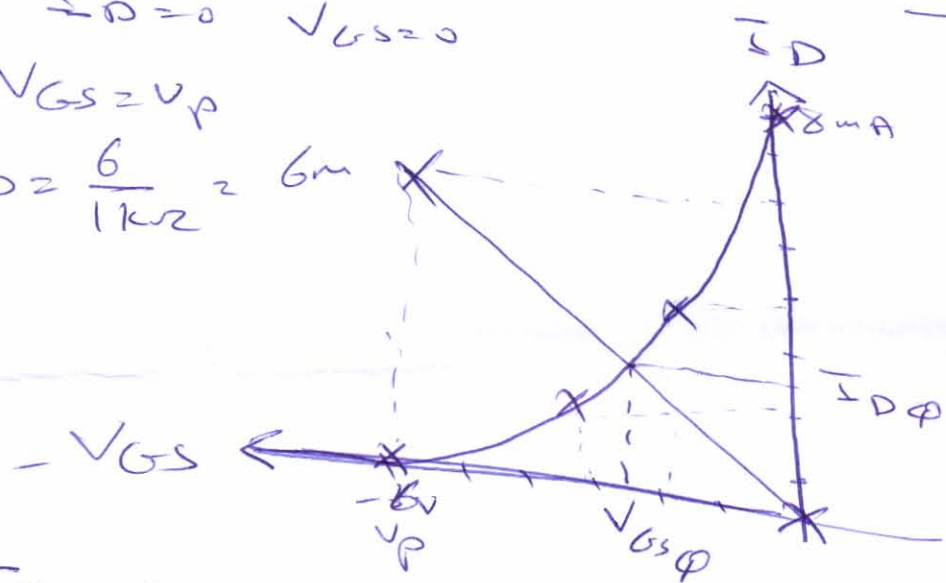

$$I_{DQ} = 2.5mA$$

$$V_{GSQ} = -2.5V$$

$$V_{DS} = V_D - V_S$$

$$V_D = I_D R_D = 2.5 \times 3.3 = 8.25V$$


$$V_S = 2.5 \times 1 = 2.5V$$

$$V_{DS} = 20 - 8.25 - 2.5 = 9.25V$$

$$V_{DS} = 9.25V$$

(Q6)

$$\beta = h_{fe} = 140$$

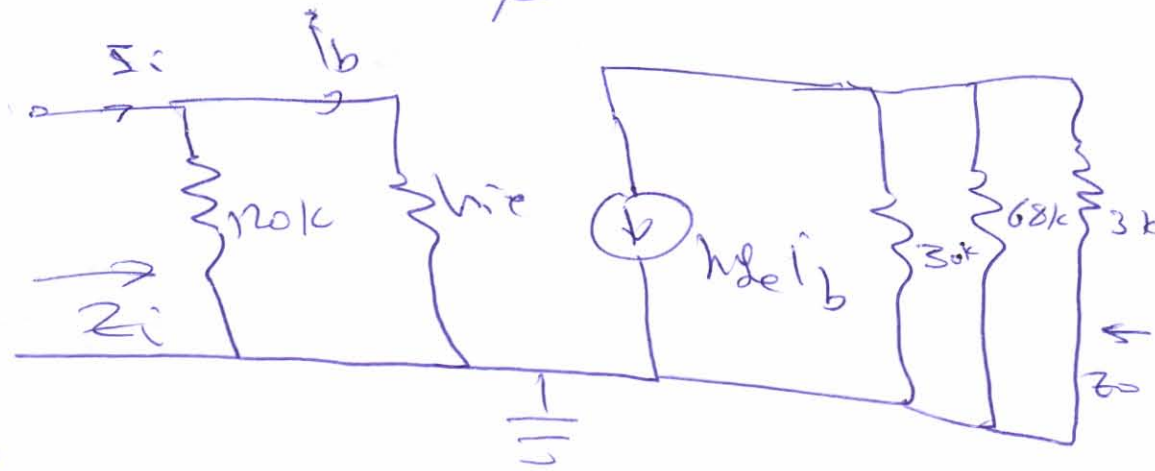

$$r_e = \frac{26mV}{I_E} \Rightarrow I_E = (1 + \beta) I_B$$

$$I_B = \frac{12 - 0.7}{188k + (141) \times 3} = \frac{11.3}{611k} = 10.4 \mu A$$

$$I_E = 141 \times 10.4 = 1mA$$

$$\therefore r_e = \frac{26mV}{1mA} = 26\Omega$$

$$h_{ie} \approx \beta r_e = (141) 26 = 9.7k\Omega$$

$$\therefore Z_i = h_{ie} \parallel 120k = 0.974k\Omega$$

$$Z_o = 30k \parallel 68k \parallel 3k = 2.02k\Omega$$

$$A_v = -h_{fe} \frac{Z_o}{h_{ie}} = -140 \cdot \frac{2.02}{9.7} = -29.15$$

$$A_i = \frac{I_o}{I_c} \cdot \frac{I_e}{I_b} \cdot \frac{I_b}{I_i}$$