

Q1: The single-phase half-wave rectifier has an R-L load with $R = 5\Omega$ and $L = 100 \text{ mH}$. The rectifier is supplied from a voltage source has rms value of 120V and at 50Hz . Calculate:

- a) Average and rms value of output voltage, (4 marks)
- b) Rectification efficiency, (3 marks)
- c) Ripple factor and form factor, (2 marks)
- d) Peak inverse voltage. (1 Mark)

$$a) \quad V_{dc} = \frac{\sqrt{2} V_i}{\pi} \left(\frac{1 - \cos \beta}{2} \right)$$

$$\beta = \phi + \pi$$

$$\phi = \tan^{-1} \frac{\omega L}{R} = \tan^{-1} \frac{2\pi \times 50 \times 100 \times 10^{-3}}{5}$$

$$= \tan^{-1} \left(\frac{6.38}{1} \right) = 1.41$$

$$\beta = \pi + 1.41 = 4.55 \text{ rad}$$

$$V_{dc} = \frac{\sqrt{2} \times 120}{\pi} \left(\frac{1 - \cos(4.55)}{2} \right) = 53.84 \text{ V}$$

$$V_L = \frac{V_i}{\sqrt{2}} \sqrt{\frac{2\beta - \sin 2\beta}{2\pi}} = \frac{120}{\sqrt{2}} \cdot \sqrt{\frac{2 \times 3.265 - \sin 2(4.55)}{2\pi}}$$

$$= 84.89 \text{ V}$$

$$b) \quad \eta = \frac{P_{dc}}{P_L} = \frac{V_{dc} I_{dc}}{V_L I_L}$$

$$P_{dc} = V_{dc} \times \frac{V_{dc}}{R} = 53.84 \times \frac{53.84}{5} = 579.75 \text{ W}$$

$$P_L = V_L \times \frac{V_L}{R} = (84.89)^2 \cdot \frac{1}{5} = 1441.26$$

$$\eta = \frac{579.75}{1441.26} = 40.22\%$$

$$c) F.F = \frac{V_L}{V_{dc}} = \frac{24.89}{53.84} = 1.577$$

$$R.F = \sqrt{F.F^2 - 1} = \sqrt{(1.577)^2 - 1} = 1.219$$

d) Peak inverse voltage "PIV" = V_m

$$PIV = \sqrt{2} \times V_s = \sqrt{2} \times 120 = 169.7 \text{ V}$$

Q2: Two diodes are connected in series to share a total voltage of 12 kV.

The reverse leakage currents of the two diodes are $I_{s1} = 1 \text{ mA}$, $I_{s2} = 1.5 \text{ mA}$ and the total leakage current $I_s = 2 \text{ mA}$. Find the voltage sharing resistance R_1 and R_2 when diodes voltages are equal.

(10 marks)

b) The diodes voltages (V_{D1}, V_{D2}) if $R_1 = 8 \text{ M}\Omega$, $R_2 = 10 \text{ M}\Omega$

a) $V_{D1} = V_{D2} = \frac{1}{2} V_s$

$$V_{D1} = V_{D2} = \frac{1}{2} \times 12 \text{ kV} = 6 \text{ kV}$$

$$I_s = I_{s1} + I_{R1}$$

$$2 \times 10^{-3} = 1 \times 10^{-3} + I_{R1}$$

$$I_s = I_{s2} + I_{R2}$$

$$2 \times 10^{-3} = 1.5 \times 10^{-3} + I_{R2}$$

$$I_{R1} = \frac{V_{D1}}{R_1}, \quad I_{R2} = \frac{V_{D2}}{R_2}$$

$$2 \times 10^{-3} = 1 \times 10^{-3} + \frac{6 \times 10^3}{R_1} \Rightarrow R_1 = \frac{6 \times 10^3}{1 \times 10^{-3}} = 6 \times 10^6 = 6 \text{ M}\Omega$$

$$2 \times 10^{-3} = 1.5 \times 10^{-3} + \frac{6 \times 10^3}{R_2}$$


$$R_2 = \frac{6 \times 10^3}{0.5 \times 10^{-3}} = 12 \times 10^6 = 12 \text{ M}\Omega$$

b) $I_{s1} + I_{R1} = I_{s2} + I_{R2}$

$$1 \times 10^{-3} + \frac{V_{D1}}{8 \times 10^6} = 1.5 \times 10^{-3} + \frac{V_{D2}}{10 \times 10^6}$$

$$V_{D1} = 12 \times 10^3 - V_{D2}$$

$$8 \times 10^6$$

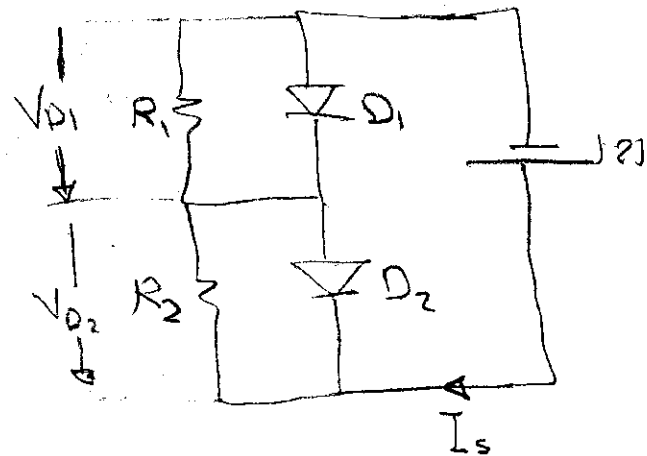

$$1 \times 10^{-3} + \frac{12 \times 10^{-3} - V_{D2}}{8 \times 10^{-6}} = 1.5 \times 10^{-3} + \frac{V_{D2}}{10 \times 10^{-6}}$$

$$1 \times 10^3 + 1.5 \times 10^3 - \frac{V_{D2}}{8} = 1.5 \times 10^3 + \frac{V_{D2}}{10}$$

$$1 \times 10^3 = \frac{V_{D2}}{10} + \frac{V_{D2}}{8}$$

$$1 \times 10^3 = \frac{4V_{D2} + 5V_{D2}}{40}$$

$$\therefore V_{D2} = \frac{40 \times 10^3}{9} = 4.44 \text{ kV}$$

$$\therefore V_{D1} = 12 - 4.44 = 7.56 \text{ kV}$$

Q₃: Three-stage voltage multiplier supplied from the transformer with secondary voltage equal to 500V at 5 kHz. The capacitors used in voltage doubler are identical and equal to 3.3 nF. Find the average output voltage when the output current equal to 1 mA.

(10 marks)

Sol

$$V_o = V_{no-load} - \Delta V - \Sigma V$$

$$V_{no-load} = 2n V_{max}$$

$$V_{max} = \sqrt{2} V_s$$

$$= \sqrt{2} \times 500 = 707 \text{ V}$$

$$V_{no-load} = 707 \times 2 \times 3 = 4242 \text{ V}$$

$$\Delta V = \frac{I}{fC} \left(\frac{2n^3}{3} + \frac{n^2}{2} - \frac{n}{6} \right)$$


$$= \frac{1 \times 10^{-3}}{5 \times 10^3 \times 3.3 \text{ nF}} \left(\frac{2 \times 27}{3} + \frac{9}{2} - \frac{3}{6} \right)$$

$$= 1333.3 \text{ V}$$

$$\Sigma V = \frac{I}{f \cdot C} \times \frac{n(n+1)}{4}$$


$$= \frac{1 \times 10^{-3}}{5 \times 10^3 \times 3.3 \times 10^{-9}} \times \frac{3 \times 4}{4} = 182 \text{ V}$$
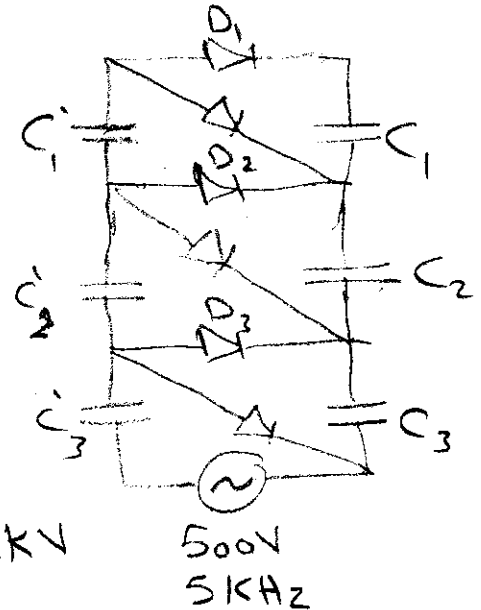
$$\therefore V_o = 4242 - 1333.3 - 182 = 2726.7 \text{ V}$$



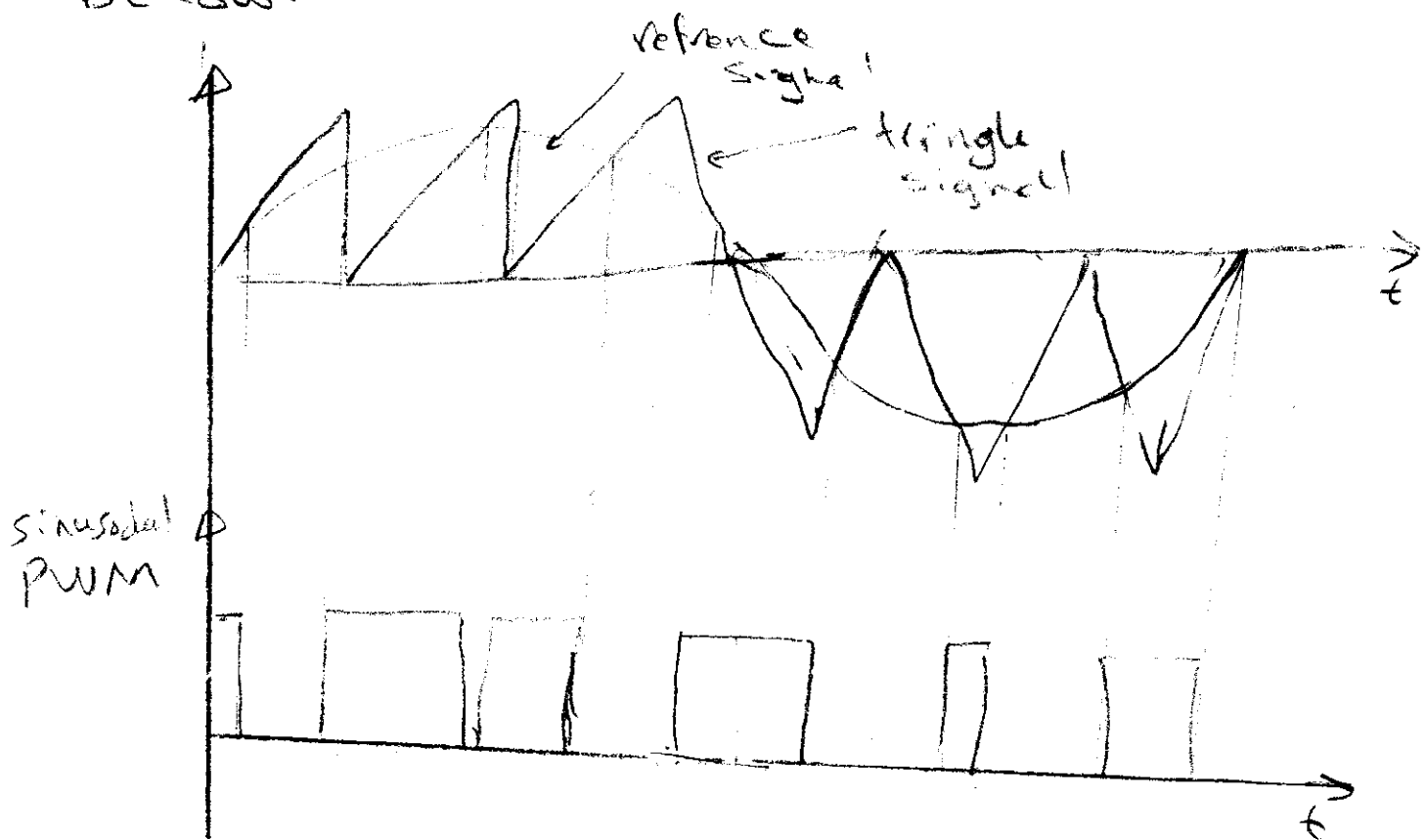
b) Sinusoidal Pulse width modulation

Instead of maintaining the width of all pulses the same as in the case of uniform pulse width modulation, the width of each pulse is vary in proportion to the amplitude of sine wave evaluated at the center of the same pulse. The Sinusoidal signal is generated by Comparing an sine wave reference signal with a triangular carrier signal of frequency f_c as shown in figure below.



- Q4: a) Explain the operation of the voltage-mode control loop in the DC-DC converters. (5 marks)
b) Explain the sinusoidal pulse width modulation technique. (5 marks)

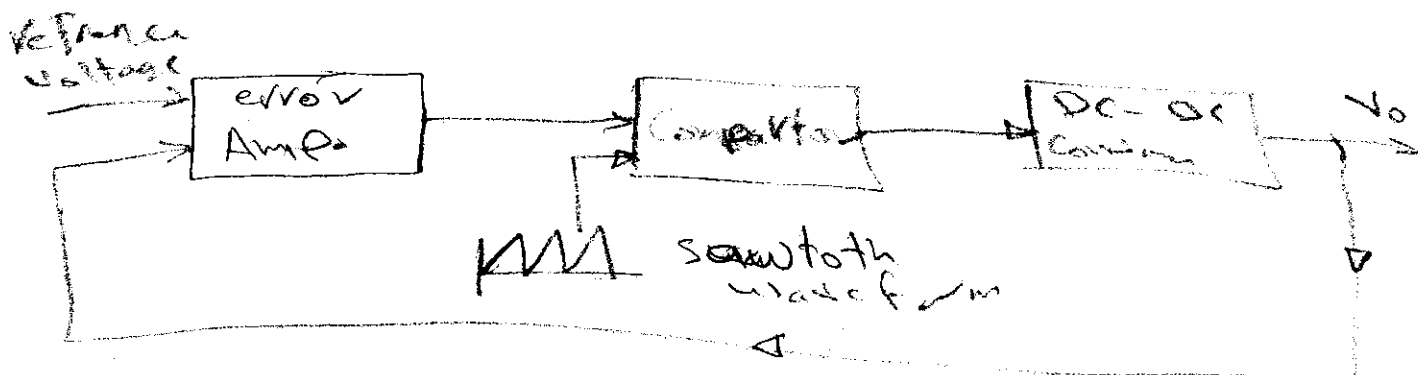a) The Voltage mod control loop is shown in Figure below. It consist from the error amplifier which amplify the difference between the output voltage and reference voltage. The output of error amplifier is applied to the comparator as d.c level. The comparator is compar the Sawtoth waveform with output of error amplifier. The output of comparator become pulse width modulation waveform. It is applied to the switching transistor of dc-dc converter.



Voltage-mode Control

$$I_1 = I_s - \frac{1}{2} \Delta I$$

$$I_2 = I_s + \frac{1}{2} \Delta I$$

$$I_s = \frac{I_o}{1-D} = \frac{3.6}{\frac{2}{3}} = 5.4 \text{ A}$$


$$I_1 = 5.4 - \frac{1}{2} \times 1.2 = 4.8 \text{ A}$$

$$I_2 = 5.4 + \frac{1.2}{2} = 6 \text{ A}$$

$$P_s = V_s I_s = 24 \times 5.4 = 129.6 \text{ W}$$

Q₅: Design a Step-up DC-DC converter has the following parameters: $V_s = 24V$, $V_o = 36V$, $R = 10\Omega$, $f = 25 \text{ kHz}$. The inductor current ripple is $1.2A$ and ripple of output voltage is 60 mV . **(10 marks)**

Sol

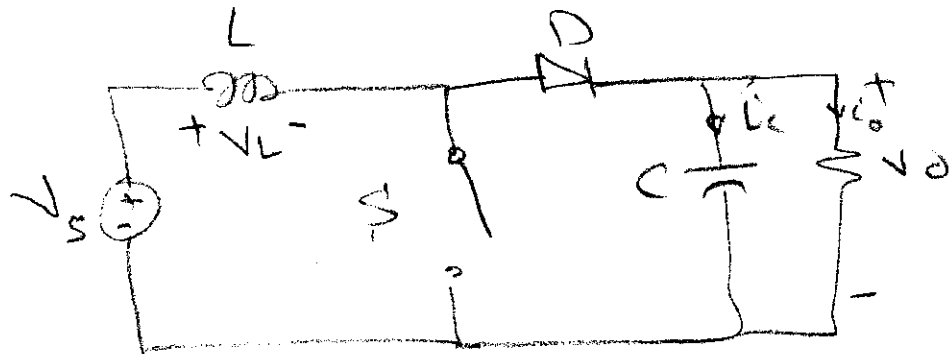

$$V_o = \frac{V_s}{1-D}$$

$$36 = \frac{24}{1-D}$$

$$1-D = \frac{24}{36} \Rightarrow D = 1 - \frac{24}{36} = 1 - \frac{2}{3} = \frac{1}{3}$$

$$L = \frac{V_s (V_o - V_s)}{D I_o f}$$

$$= \frac{24 (36 - 24)}{1.2 \times 36 \times 25 \times 10^3} = 266.7 \mu H$$

$$C = \frac{D I_o}{\Delta V_C \times f}$$

$$I_o = \frac{V_o}{R} = \frac{36}{10} = 3.6 A$$

$$\therefore C = \frac{\frac{1}{3} \times 3.6}{60 \times 10^{-3} \times 25 \times 10^3} = 800 \mu F$$

$$\% DF_3 = \frac{36}{7 \times 10^8} = 3.7\%$$

Q6: The single-phase half-bridge has a resistive load of $R = 5\Omega$ supplied from dc input voltage $V_{dc} = 240V$ with switching frequency of 60Hz. Determine the following:

- a) The rms value of fundamental component, (2 marks)
- b) The output power, (2 marks)
- c) The average and peak current of each transistor, (2 marks)
- d) The total harmonic distortion, (2 marks)
- e) The distortion factor of lowest harmonic. (2 marks)

$$a) \quad V_1 = \frac{2 V_{dc}}{\pi \sqrt{2}} = \frac{2 \times 240}{\pi \sqrt{2}} \\ = 108 \text{ V}$$

$$b) \quad V_o = V_{dc}/2 = \frac{240}{2} = 120 \\ P_o = \frac{V_o^2}{R} = \frac{(120)^2}{5} = 2.88 \text{ kW}$$

$$c) \quad I_{peak} = \frac{V_{dc}}{2R} = \frac{240}{2 \times 5} = 24 \text{ A}$$

$$I_{average} = 0.5 I_{peak} \\ = 0.5 \times 24 = 12 \text{ A}$$

$$d) \quad THD = \frac{(\sqrt{V_o^2 - V_1^2})^{1/2}}{V_1} \\ = \frac{((120)^2 - (108)^2)^{1/2}}{108} = 48.4\%$$

e) lowest harmonic is Third harmonic

$$DF_3 = \frac{V_3}{(3)^2 V_1}$$

$$V_3 = \frac{2 V_{dc}}{3 \pi \sqrt{2}} = \frac{2 \times 240}{3 \pi \sqrt{2}} = 36$$