

Electrical Engineering Fundamentals

EE1

① Basic Concepts & Basic Laws

1.1 Basic Concepts

1.1.1 System of Units

The basic SI units

Quantity	Basic unit	Symbol
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	kelvin	K
Luminous intensity	candela	cd

The SI prefixes

Multiplier	Prefix	Symbol
10^{18}	exa	E
10^{15}	peta	P
10^{12}	tera	T
10^9	giga	G
10^6	mega	M
10^3	kilo	k
10	deca	da
10^{-1}	deci	d
10^{-2}	centi	c
10^{-3}	milli	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p
10^{-15}	femto	f
10^{-18}	atto	a

Examples

$$10 \text{ MHz} \Rightarrow 10 \times 10^6 \text{ Hz}$$

$$2 \text{ mA} = 2 \times 10^{-3} = 0.002 \text{ A}$$

$$5 \mu\text{s} = 5 \times 10^{-6} \text{ s}$$

1.1.2 Charge and Current


EE1

The electric charge is an electrical property of the atomic particles of which matter consists, measured in coulombs (C). The charge of an electron is $(-1.602 \times 10^{-19} \text{ C})$.

Electric Current


is the rate of change of charge, measured in amperes (A). The current (I) is defined mathematically as:

$$i = \frac{dq}{dt}$$

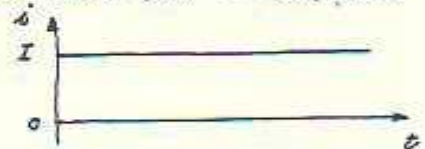

d.c. current
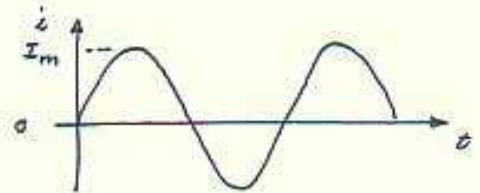
$$\therefore q = \int_{t_1}^{t_2} i \, dt$$



a.c. current

- * A direct current (dc) is current that remains constant with time. The symbol (I) is usually used to represent such a constant current.
- * An alternating current (ac) is a current that is varying sinusoidally with time. A time varying current is represented by the symbol (i).

Example

Determine the total charge entering a terminal between $t = 1 \text{ s}$ and $t = 2 \text{ s}$, if the current passing the terminal is $i = (3t^2 - t) \text{ A}$.


Solution

$$\begin{aligned} q &= \int_{t_1}^{t_2} i \, dt \\ &= \int_1^2 (3t^2 - t) \, dt = \left(t^3 - \frac{t^2}{2} \right) \Big|_1^2 \\ &= (8 - 2) - \left(1 - \frac{1}{2} \right) = \underline{\underline{5.5 \text{ C}}} \end{aligned}$$

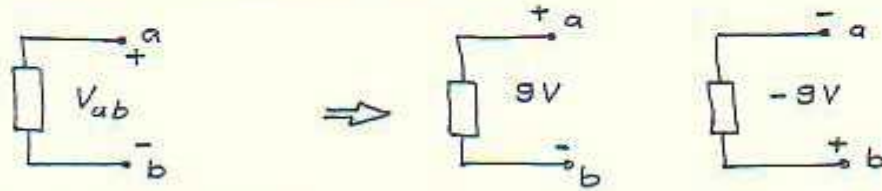1.1.3 Voltage

EE1

Voltage: The voltage (or potential difference) is the energy required to move a unit charge through an element, measured in volts (V).



Polarity of Voltage
 V_{ab}

* For the voltage $V_{ab} \Rightarrow$ This means that the potential of point a is higher than that of point b

$$V_{ab} = V_a - V_b$$

1.1.4 Power and Energy

* Power: is the time rate of expending or absorbing energy, measured in watts (W)

$$\Rightarrow p = \frac{dw}{dt}$$

where p is the power in watts (W), w is the energy in joules (J), and t is the time in seconds (s)

$$\text{We have; } p = \frac{dw}{dt} \Rightarrow p = \frac{dw}{dt} \cdot \frac{dq}{dq}$$

$$\Rightarrow p = \frac{dw}{dq} \cdot \frac{dq}{dt} = v \cdot i$$

$$\therefore p = vi$$

* The energy absorbed or supplied by an element

from time t_0 to time t is :

ESI

$$w = \int_{t_0}^t p dt = \int_{t_0}^t v i dt$$

Energy is the capacity to do work, measured in joules (J)

* The electric power utility companies measure energy in watt-hour (Wh), where

$$1 \text{ Wh} = 3,600 \text{ J}$$

Example

: How much energy does a 100 W electric bulb consume in 2 hours?

Solution

$$w = pt = 100 \times 2 = 200 \text{ Wh}$$

or


$$\begin{aligned} w &= pt = (100 \text{ W})(2 \times 60 \times 60) \\ &= 720000 \text{ J} \\ &= 720 \text{ kJ} \end{aligned}$$

which is the same result (if you convert from joules to watts or vice-versa).

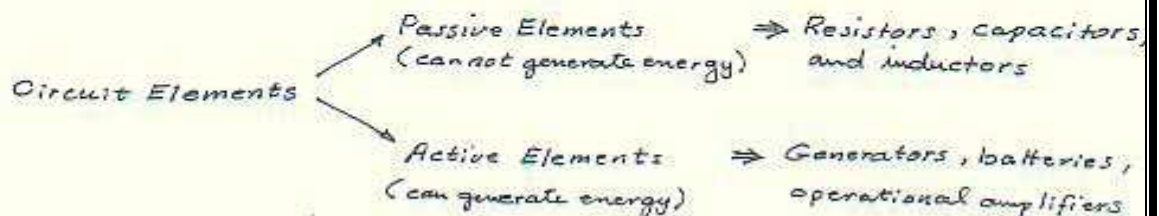1.1.5 Circuit Elements

: An electric circuit is an interconnection of electrical elements.

* Circuit analysis is the process of determining voltages across (or the currents through) the elements of the circuit.



- * The most important active elements are voltage or current sources that generally deliver power to the circuit connected to them. 551

Voltage (or current) sources $\left\{ \begin{array}{l} \text{Independent sources} \\ \text{Dependent sources} \end{array} \right.$

- * An ideal independent source is an active element that provides a specified voltage or current that is completely independent of other circuit variables.
- * Dependent sources (or controlled sources) are active elements in which the source quantity is controlled by another voltage or current. (It will be discussed later.)

1.2 Basic Laws


1.2.1 Ohm's Law

(1826): Ohm's Law states that the voltage V across a resistor is directly proportional to the current I flowing through the resistor.

$$V \propto I$$

$$\Rightarrow V = IR$$

كانوا

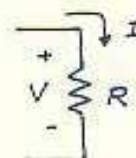


where R is the resistance. The resistance R denotes the ability of an element to resist the flow of electric current, it is measured in ohms (Ω).

For any material, the resistance R depends on its physical dimensions as follows:

$$R = \rho \frac{\ell}{A}$$

where ρ is the resistivity of the material.

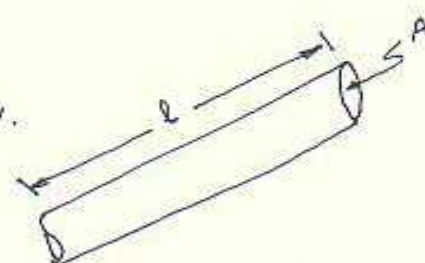
- \Rightarrow Good conductors have low resistivities (such as copper, aluminum, etc...)
- \Rightarrow Insulators have high resistivities (such as mica, paper, etc...)




المواد Material	Resistivities of Common Materials Resistivity ($\Omega \cdot m$)	Usage
Silver	1.54×10^{-8}	Conductor
Copper	1.72×10^{-8}	"
Aluminum	2.80×10^{-8}	"
Gold	2.45×10^{-8}	"
Carbon	4.00×10^{-5}	Semiconductor
Germanium	47.0×10^{-2}	"
Silicon	6.40×10^{-2}	"
Paper	10^{10}	Insulator
Mica	5×10^{11}	"
Glass	10^{12}	"
Teflon	3×10^{12}	"

* The resistance of a short circuit element is approaching zero

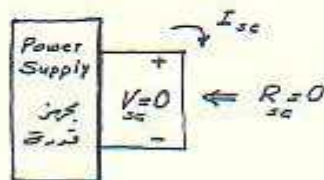* The resistance of an open circuit is approaching infinity.



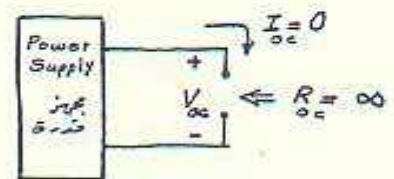Short circuit with $R_{sc} = 0$
 $V_{sc} = 0$



Open circuit with $R_{oc} = \infty$
 $I_{oc} = 0$

* Conductance (G)

A useful quantity in circuit analysis is the reciprocal of resistance (R), is called the conductance (G);

$$G = \frac{1}{R} = \frac{i}{v}$$

The conductance can be explained as the ability of an element to conduct electric current, it is measured in mhos (\mathcal{U}) or in siemens (S).

$$\therefore i = Gv$$

and:


$$p = vi = i^2 R = \frac{v^2}{R} \quad \text{watts (W)}$$

OR

$$p = vi = v^2 G = \frac{i^2}{G}$$

Example

: In the circuit shown, calculate the current I , the conductance G , and the power P

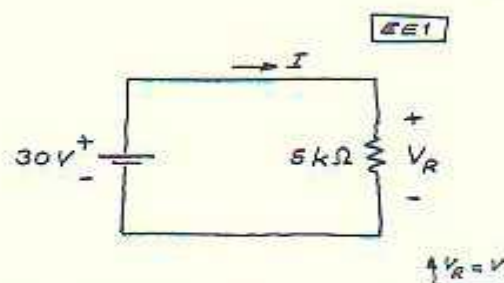Solution

- the current

$$I = \frac{V_R}{R} = \frac{30}{5 \times 10^3} = 6 \times 10^{-3} = \underline{6 \text{ mA}}$$

- the conductance

$$G = \frac{1}{R} = \frac{1}{5 \times 10^3} = 0.2 \times 10^{-3} = \underline{0.2 \text{ mS}}$$

- the power

$$P = V_R I = 30 (6 \times 10^{-3}) = \underline{180 \text{ mW}}$$

or

$$P = I^2 R = (6 \times 10^{-3})^2 (5 \times 10^3) = \underline{180 \text{ mW}}$$

or

$$P = V_R^2 G = (30)^2 (0.2 \times 10^{-3}) = \underline{180 \text{ mW}}$$

1.2.2 Nodes, branches and loops


* A branch represents a single element in the electric circuit, such as a voltage source or a resistor etc...

* A node represents the point of connection between two or more branches.

* A loop is any closed path in a circuit.

Example

: For the circuit shown, determine the number of branches, nodes and the independent loops.

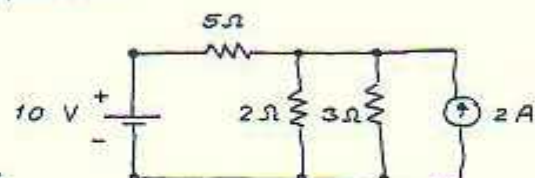Solution

Since there are 5 elements

$$\Rightarrow \text{Number of branches} = \underline{5}$$

10V, 5Ω, 2Ω, 3Ω, and 2A

$$\text{Number of nodes} = \underline{3} \quad (\text{as shown in the figure}).$$

3 loops

تمتة حل المثال



⇒ There are 3 nodes :
a, b and c

* The number of the independent loops = 3

⇒ loop 1 or loop abc :
contains (10V, 5Ω, 2Ω)

⇒ loop 2 or loop bcb :
contains (2Ω, 3Ω)

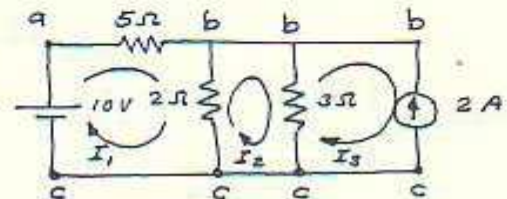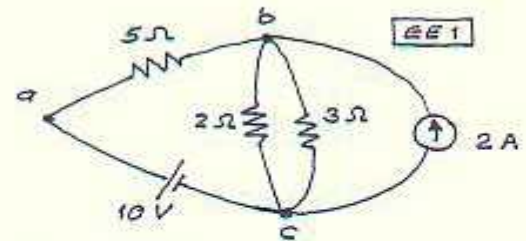& ⇒ loop 3 or loop bcb :
contains (3Ω, 2A)



Notes

— : There are more than 3 (dependent) loops in this example, we had only calculated the INDEPENDENT loops which are only 3.

IN GENERAL; Any circuit with b branches, n nodes and l independent loops, the following fundamental theorem of network topology:

$$b = l + n - 1$$

* Two or more elements are in SERIES if they are cascaded sequentially and consequently carry the SAME current.

* Two or more elements are in PARALLEL if they are connected to the same two nodes and have consequently the same VOLTAGE across them.

1.2.3 Kirchhoff's Laws (1847)

* Kirchhoff's current law (KCL); states that the algebraic sum of all current entering a node is zero or: The sum of currents entering a node is equal to the sum of currents leaving that node.

$$\sum_{n=1}^N I_n = 0$$


or

$$\sum_{m=1}^M I_{mi} = \sum_{n=1}^N I_{no}$$

where I_{mi} are the currents entering the node and I_{no} are the currents leaving the node.

Example

For the network shown, calculate the total current I_T

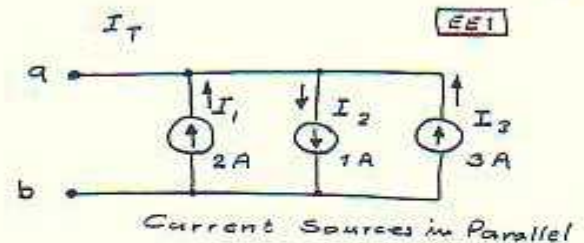
Solution

According to KCL;

$$I_T = I_1 - I_2 + I_3$$

$$= 2 - 1 + 3 = \underline{5A}$$

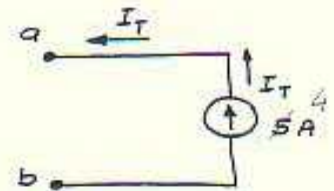∴ The equivalent circuit for the network can be as shown ⇒



* Kirchhoff's Voltage Law (KVL); states that the algebraic sum of all voltages around a closed path (or loop) is zero.
توازن كيرشوف للجهد


∴ Mathematically KVL states that:

$$\sum_{m=1}^M V_m = 0$$

where M is the number of voltages in the loop (or the number of branches in the loop), and V_m is the m th voltage.

Example

For the circuit shown, find the voltages V_1 and V_2

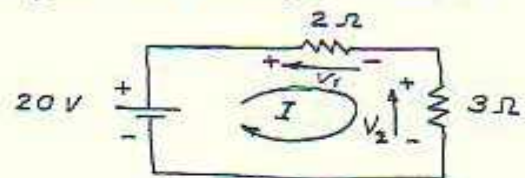Solution

$$V_1 = 2I$$

$$V_2 = 3I$$

From KVL:

$$\sum V = 0 \Rightarrow 20 - V_1 - V_2 = 0 \Rightarrow 20 = 3I + 2I$$

$$\Rightarrow 5I = 20 \Rightarrow I = 4A$$


$$\therefore V_1 = 2I = \underline{8V} \quad \text{and} \quad V_2 = 3I = \underline{12V}$$

Tutorial Sheet No 1

Basic Concepts & Basic Laws

T31

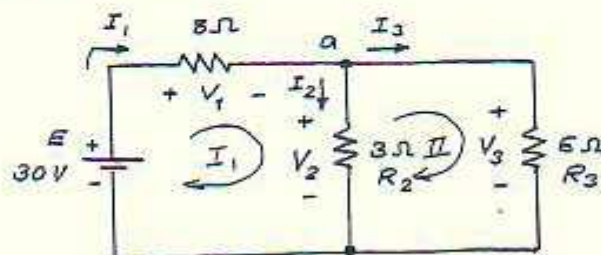Example Using Kirchhoff's laws, find the currents and voltages in the circuit shown.



Solution:

ملاحظة: المطلوب في المثال إيجاد كل من I_1 , I_2 , I_3 , V_1 , V_2 و V_3
باستخدام قوانين كيرشوف

* Using Ohm's law:

$$\begin{aligned} V_1 &= I_1 R_1 = 8 I_1 \\ V_2 &= I_2 R_2 = 3 I_2 \\ V_3 &= I_3 R_3 = 6 I_3 \end{aligned}$$

* Applying KCL at node a:

$$I_1 = I_2 + I_3 \Rightarrow I_1 - I_2 - I_3 = 0 \quad \text{Eq(1)}$$

* Applying KVL to loop 1:

$$\begin{aligned} E - V_1 - V_2 &= 0 \Rightarrow 30 - V_1 - V_2 = 0 \\ \Rightarrow 30 - 8 I_1 - 3 I_2 &= 0 \end{aligned}$$

$$\therefore I_1 = \frac{30 - 3 I_2}{8} \quad \text{Eq(2)}$$

* Applying KVL to loop 2:

$$\begin{aligned} V_2 - V_3 &= 0 \Rightarrow V_2 = V_3 \\ \therefore 3 I_2 &= 6 I_3 \end{aligned} \quad \begin{array}{l} \text{هنا واضح أنه} \\ \text{متساوية لأن } R_2 \neq R_3 \end{array}$$

$$\therefore I_3 = \frac{I_2}{2} \quad \text{Eq(3)}$$

\Rightarrow From Eq(1), Eq(2) & Eq(3)

$$\frac{30 - 3 I_2}{8} - I_2 - \frac{I_2}{2} = 0 \Rightarrow I_2 = \underline{\underline{2 \text{ A}}}$$

$$\text{and } I_1 = \frac{30 - 3 I_2}{8} = \frac{30 - 3(2)}{8} = \underline{\underline{3 \text{ A}}}$$

$$I_3 = \frac{I_2}{2} = \frac{2}{2} = 1 \text{ A}$$

$$\Rightarrow \therefore V_1 = 8I_1 \Rightarrow \therefore V_1 = 8(3) = 24V$$

T51

$$\text{Similarly } V_2 = 3I_2 = 3(2) = 6V$$

$$\text{and } V_3 = 6I_3 = 6(1) = 6V$$

للتأكد منه صعدنا الخلية :

$$I_1 = I_2 + I_3$$

$$3 = 2 + 1 \Rightarrow 3 = 3$$

كذلك فان تطبيقه قانون كيرشوف للشحونة على المالحه رقم 1 ينم ما يأتي :


$$E = V_1 + V_2$$

$$\therefore 30 = 24 + 6$$

$$\therefore 30 = 30 \quad \leftarrow \text{كل شيء صحيح}$$

Example

Determine the number of branches, nodes and independent loops in the circuit shown.

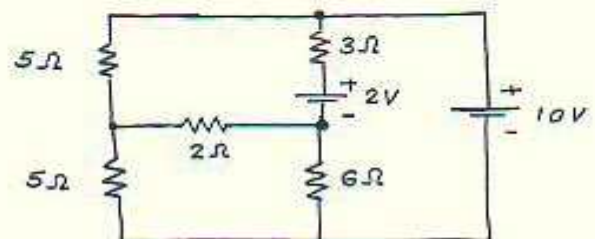Solution

* There are 7 element \Rightarrow no. of branches = 7
 $\Rightarrow \underline{b = 7}$

a, b, c, d, e \leftarrow * There are 5 nodes as shown in the figure :
 $\Rightarrow n = 5$


I, II, III \leftarrow * There are 3 independent loops :

$$\Rightarrow l = 3$$

$\therefore b = l + n - 1$ is satisfied

$$\text{Since } 7 = 3 + 5 - 1$$


$$\Rightarrow 7 = 7$$

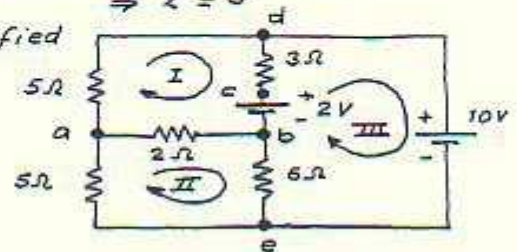

Practice Problem

T51

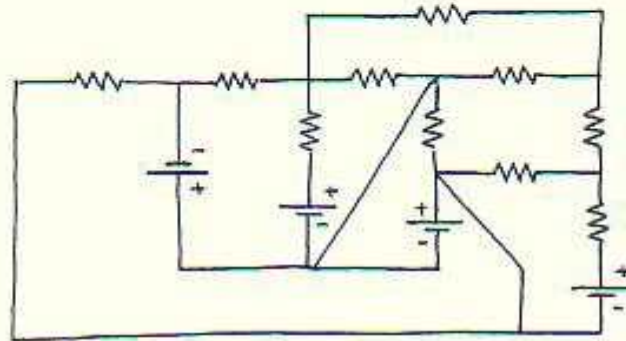Identify all nodes, branches and independent loops in the circuit shown in the figure.



Answer


no. of nodes = 8 $n = 8$
 no. of branches = 14 $b = 14$
 no. of independent loops = 7 $l = 7$

Check. Does this satisfy the fundamental theorem of network topology?

$$b = l + n - 1 = 7 + 8 - 1 = 14 \quad \text{YES}$$

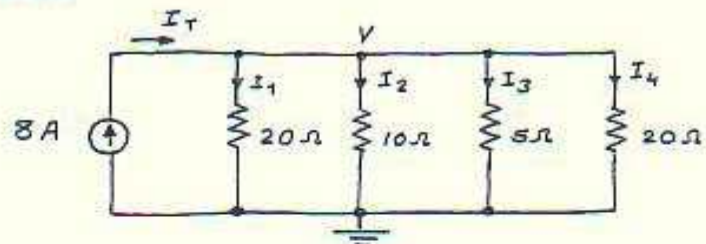Example

Determine all currents and voltages in the circuit of the figure shown.



Solution

KCL \Rightarrow
 $I_T = I_1 + I_2 + I_3 + I_4 \Rightarrow 8 = I_1 + I_2 + I_3 + I_4$

Ohm's law

$$\begin{aligned} V &= 20 I_1 & \Rightarrow I_1 &= V/20 \\ &= 10 I_2 & I_2 &= V/10 \\ &= 5 I_3 & I_3 &= V/5 \\ &= 20 I_4 & I_4 &= V/20 \end{aligned}$$

Substituting in the current equation;

$$\Rightarrow 8 = \frac{V}{20} + \frac{V}{10} + \frac{V}{5} + \frac{V}{20}$$

$$\therefore 160 = V + 2V + 4V + V$$

$$160 = 8V$$

$$\therefore V = \underline{20 \text{ Volts}}$$

$$\therefore I_1 = \frac{V}{20} = \frac{20}{20} = 1 \text{ A}$$

$$I_2 = \frac{V}{10} = \frac{20}{10} = 2 \text{ A}$$

$$I_3 = \frac{V}{5} = \frac{20}{5} = 4 \text{ A}$$

$$I_4 = \frac{V}{20} = \frac{20}{20} = 1 \text{ A}$$

Check

$$I_T = I_1 + I_2 + I_3 + I_4$$

$$8 = 1 + 2 + 4 + 1$$

$$8 = 8 \quad \checkmark$$