

2. Circuit Transformations


2.1 Series Circuits

Two elements are in series if they have only one point in common that is not connected to other current carrying elements of the network.

For the series ckt. shown, using KVL we have:

$$\begin{aligned} E &= V_1 + V_2 + V_3 \\ &= IR_1 + IR_2 + IR_3 \\ &= I(R_1 + R_2 + R_3) \\ &= IR_T \end{aligned}$$

$$\therefore I = \frac{E}{R_T}$$

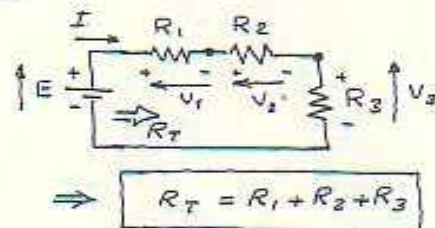


In general, for a series ckt. consisting N resistors, then the total resistance of such a ckt. R_T is given as

$$R_T = R_1 + R_2 + R_3 + \dots + R_N$$

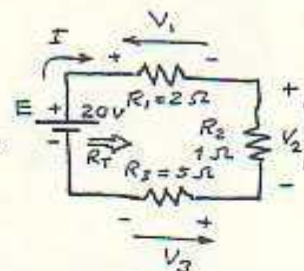Example

For the ckt. shown;

- Find the total resistance
- Calculate the current I
- Determine the voltages V_1 , V_2 and V_3



Solution

a. $R_T = R_1 + R_2 + R_3$
 $= 2 + 1 + 5 = 8 \Omega$

b. $I = \frac{E}{R_T} = \frac{20}{8} = 2.5 \text{ A}$


c. $V_1 = IR_1 = (2.5)(2) = 5 \text{ V}$
 $V_2 = IR_2 = (2.5)(1) = 2.5 \text{ V}$
 $V_3 = IR_3 = (2.5)(5) = 12.5 \text{ V}$

ملاحظة
 $V_1 + V_2 + V_3 = E$
 $5 + 2.5 + 12.5 = 20 \text{ V}$
 $\therefore 20 \text{ V} = 20 \text{ V}$

2.1.1 Voltage Sources in Series

The net voltage will be the algebraic sum of all sources that are connected in series.

Example

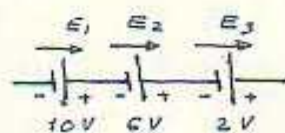

$$E_T = 18 \text{ V}$$

$$\begin{aligned} E_T &= E_1 + E_2 + E_3 \\ &= 10 + 6 + 2 = 18 \text{ V} \end{aligned}$$

ملاحظة
 لا يمكن ربط مصادر الجهد
 في التوازي حيث ذلك مخالف لقانون كيرشوف للجهد

(2)

2.1.2 Voltage Divider Rule

EE2

: Consider the series ckt. shown.

we have:

$$R_T = R_1 + R_2$$

and

$$I = \frac{E}{R_T}$$

$$V_1 = IR_1 = \left(\frac{E}{R_T} \right) \cdot R_1$$

$$= \frac{E \cdot R_1}{R_T}$$

Similarly;

$$V_2 = IR_2 = \left(\frac{E}{R_T} \right) \cdot R_2$$

$$= \frac{E \cdot R_2}{R_T}$$

Hence, we can write:

$$V_x = \frac{E \cdot R_x}{R_T}$$

← Voltage divider rule

This means that "the voltage divider rule" can be understood to state that:

The voltage across a resistor in a series circuit is equal to the value of that resistor times the the total applied voltage across the series elements divided by the total resistance of the series elements.

Example

: Determine the voltages V_1 , V_3 , and V' for the ckt. shown.

Solution

:

Using the voltage divider rule:


$$V_1 = \frac{E \cdot R_1}{R_T}$$

$$= \frac{(45) \cdot (2 \times 10^3)}{(2+5+8) \times 10^3}$$

$$= 6V$$

$$V_3 = \frac{E \cdot R_3}{R_T} = \frac{(45)(8 \times 10^3)}{(2+5+8) \times 10^3}$$

$$= 24V$$

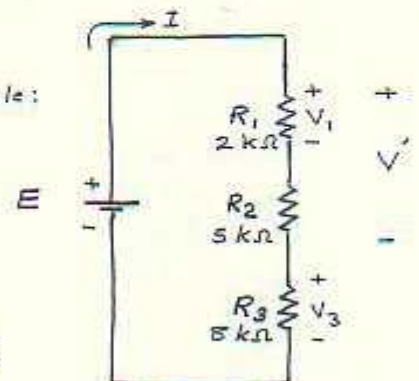

$$V' = \frac{E \cdot R'}{R_T} \quad \Leftarrow \quad R' = (2+5) \times 10^3 \Omega$$

$$= \frac{(45) \cdot (7 \times 10^3)}{(2+5+8) \times 10^3}$$

$$= \underline{21 \text{ V}}$$

EE2


تعطيان :
 $E = V_3 + V'$
 $45 \text{ V} = 24 \text{ V} + 21 \text{ V}$
 $45 \text{ V} = 45 \text{ V}$

نلاحظ ان فرق الجهد بين طرفي اي عنصر من عناصر دائرة الترانزستور يتناسب مع مقاومة ذلك العنصر ، أي ان المقاومة الكبيرة يقابلها فرق جهد كبير والمقاومة الصغيرة يقابلها فرق جهد صغير ، وفي جميع الاحوال يجب ان يكون مجموع فروق الجهد مساوياً الى مرتبة المقدار .

NOTATION


ground potential

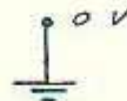It is common , for safety purposes and as a reference to ground electrical and electronic systems. The symbol for the ground connection is :



with its defined potential level (zero volts). As a consequence, the cct. might need to be redrawn in the ordinary form so as to be analyzed.

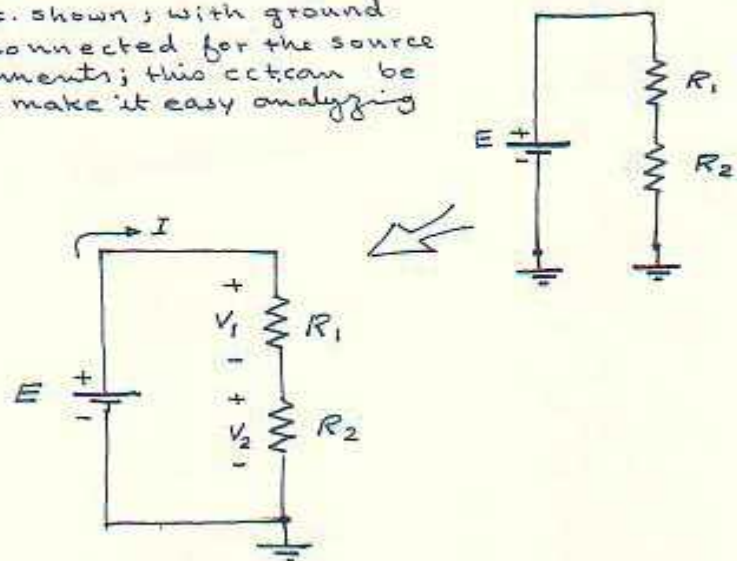Example : For the cct. shown , with ground potentials connected for the source and to elements; this cct. can be redrawn to make it easy analyzing it.




4

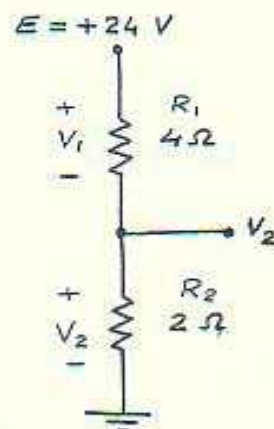Example

EE2

: Using the voltage divider rule, determine the voltages V_1 and V_2 for the ckt shown:




Solution

: Redrawing the ckt. with the standard battery symbol, then the ckt. will be as shown below:

$$\therefore V_1 = \frac{R_1 E}{R_T} = \frac{(4) \cdot (24)}{4 + 2} = 16 \text{ V}$$


and
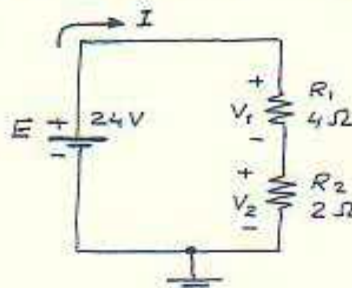
$$V_2 = \frac{R_2 E}{R_T} = \frac{(2) \cdot (24)}{4 + 2} = 8 \text{ V}$$



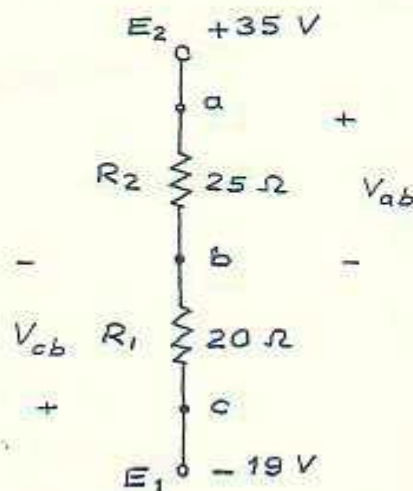Example

: For the ckt. shown, determine V_{ab} , V_{cb} and V_b .



Solution

The cct. is redrawn as shown;

$$\therefore I = \frac{E_1 + E_2}{R_T} = \frac{19 + 35}{20 + 25}$$

$$= 1.2 \text{ A}$$

$$V_{ab} = IR_2 = (1.2)(25)$$


$$= 30 \text{ V}$$

$$\text{and } V_{cb} = -V_{bc} = -IR_1$$

$$= -(1.2)(20)$$

$$= -24 \text{ V}$$

$$V_c = -E_1 = -19 \text{ V}$$

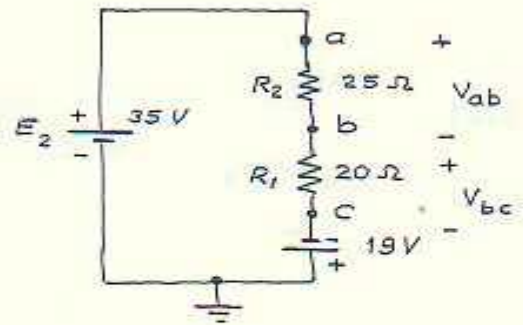


ملحظة ١/ يمكنه الخ باستخدام
voltage divider rule
مع ملحظة ان $V_{cb} = -V_{bc}$


ملحظة ٢/ ان V_{ab} تعني
فرق جهد النقطة a عن النقطة
b ، فإذا كانت V_{ab} موجبة فان
هنا يعني ان V_a اكبر من V_b
والعكس صحيح .

ملحظة ٣/ ان V_a تعني جهد النقطة a
بالنسبة الى الارض .


Internal Resistance of Voltage Sources

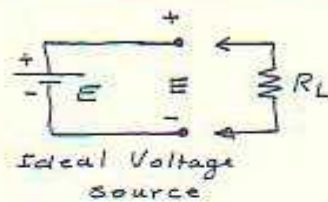

①

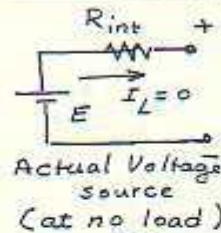

②

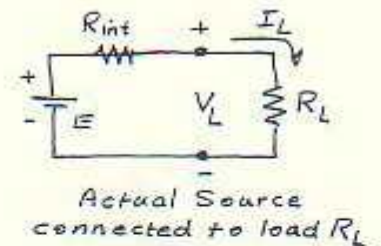

③

- Applying KVL on figure ③ :

$$E - I_L R_{in} - V_L = 0$$

- Applying KVL on figure ② :

$$E = V_{NL}$$

Substituting, then :

$$V_{NL} - I_L R_{in} - V_L = 0$$

$$\therefore V_L = V_{NL} - I_L R_{in}$$

2.2 Parallel Circuits

EE2

: Two branches or elements or networks are in parallel if they have two points in common.

For the parallel cct. shown; using KCL, we have:

$$I = I_1 + I_2 + I_3$$


$$= \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$\text{since } V_1 = V_2 = V_3 = E = V$$

$$\therefore I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\therefore \frac{V}{R_T} = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$
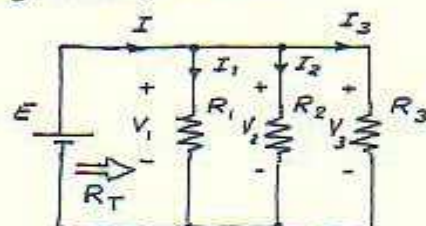
$$\therefore \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



$$E = V_1 = V_2 = V_3$$

$$I = \frac{E}{R_T} = \frac{V}{R_T}$$

In general, for N resistors connected in parallel, then:

$$\boxed{\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}}$$

Notation

Conductance G


For parallel networks, it is common to use the idea of conductance in the cct. analysis. The conductance (G) is defined as:

$$G = \frac{1}{R} \quad \text{Siemens (S)}$$

So, we can write the total conductance G_T for the parallel cct shown, as:

$$G_T = G_1 + G_2 + G_3$$

$$\Rightarrow R_T = \frac{1}{G_T}$$

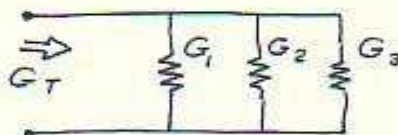

NOTE that, the total resistance R_T of parallel resistors is always less than the value of the smallest resistor.

Special Cases

EE2

The general relation for the total resistance of parallel resistors is:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

* Case 1

For equal resistors in parallel, i.e., when

$$R_1 = R_2 = R_3 = \dots = R_N = R$$

$$\text{then; } \frac{1}{R_T} = \underbrace{\frac{1}{R} + \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R}}_N$$

$$\therefore \frac{1}{R_T} = N \left(\frac{1}{R} \right) \Rightarrow \boxed{R_T = \frac{R}{N}}$$

* Case 2

For two resistors in parallel, then R_T is given as:

$$\boxed{R_T = \frac{R_1 R_2}{R_1 + R_2}}$$

This means that, the total resistance of the two parallel resistors is the product of the two divided by their sum.


* Case 3

For three resistors in parallel, then R_T is given as:

$$\boxed{R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}}$$

Example

Determine the total resistance for the network shown:

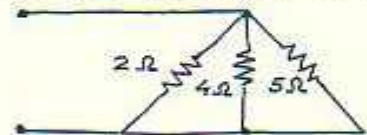Solution


Redraw the ckt. to be as shown;

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{2} + \frac{1}{4} + \frac{1}{5}$$

$$= 0.5 + 0.25 + 0.2$$

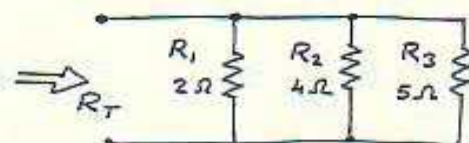
$$= 0.95 \Rightarrow \therefore R_T = \frac{1}{0.95} = \underline{1.053 \Omega}$$



Example

For the parallel network shown;

- Calculate R_T
- Determine I_T
- Calculate I_1 and I_2
- Determine the power to each resistive load.
- Determine the power delivered by the source and compare it with the total power dissipated by the resistive elements.

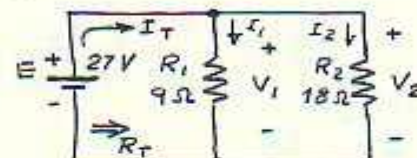Solution

$$a. \quad R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(9)(18)}{9 + 18} = \frac{162}{27} = 6 \Omega$$

$$b. \quad I_T = \frac{E}{R_T} = \frac{27}{6} = 4.5 A$$

$$c. \quad I_1 = \frac{V_1}{R_1} = \frac{E}{R_1} = \frac{27}{9} = 3 A$$

and

$$I_2 = \frac{V_2}{R_2} = \frac{E}{R_2} = \frac{27}{18} = 1.5 A$$

$$I_T = I_1 + I_2 \quad \text{أو صفاً :}$$

$$d. \quad P_1 = I_1 V_1 = E I_1 = (27)(3) = 81 W$$

$$P_2 = I_2 V_2 = E I_2 = (27)(1.5) = 40.5 W$$

$$e. \quad P_s = E I_T = (27)(4.5) = 121.5 W$$

$$P_s = P_1 + P_2 = 81 + 40.5 = 121.5 W$$

* لاحظ ان مجموع القدرة المستهلكة في المقاومتين R_1 و R_2 يساوي القدرة التي يخرجها المصدر E

2.2.1 Current Divider Rule


Consider the parallel cct. shown;

$$\text{We have; } I = \frac{V}{R_T} \Rightarrow V = I R_T$$

$$\text{and } R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{but } I_1 = \frac{V}{R_1} = \frac{I R_T}{R_1} = I \cdot \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{1}{R_1}$$
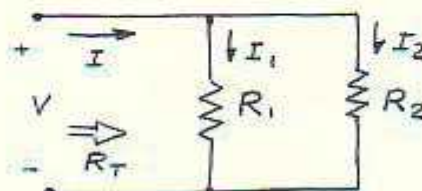
$$\therefore \boxed{I_1 = I \cdot \frac{R_2}{R_1 + R_2}}$$




Similarly, for I_2 , we have:

$$I_2 = \frac{V}{R_2} = \frac{I R_T}{R_2} = I \cdot \frac{\frac{R_1 R_2}{R_1 + R_2}}{R_2} \quad \boxed{EE1}$$

$$\therefore I_2 = I \cdot \frac{R_1}{R_1 + R_2}$$

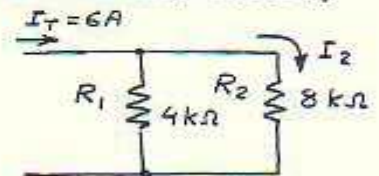Example

: Determine the current I_2 for the network shown;




Solution:
$$I_2 = I_T \cdot \frac{R_1}{R_1 + R_2}$$

$$= 6 \cdot \frac{4 \times 10^3}{(4 + 8) \times 10^3} = 6 \cdot \frac{4}{12} = \underline{2 \text{ A}}$$

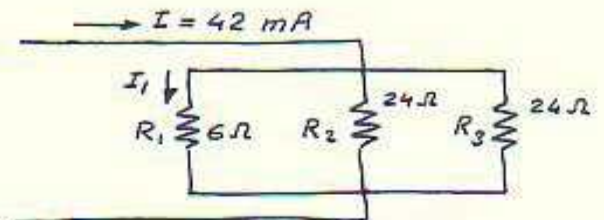Example

: Find the current I_1 for the network shown;



Solution:

$$I_1 = I \cdot \frac{R_T}{R_1}$$

$$R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

or

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{6} + \frac{1}{24} + \frac{1}{24}$$


$$\Rightarrow R_T = 4 \Omega$$

$$\therefore I_1 = 42 \times 10^{-3} \cdot \frac{4}{6}$$

$$= 28 \times 10^{-3} = \underline{28 \text{ mA}}$$

2.2.2 Voltage Sources in Parallel

EE2

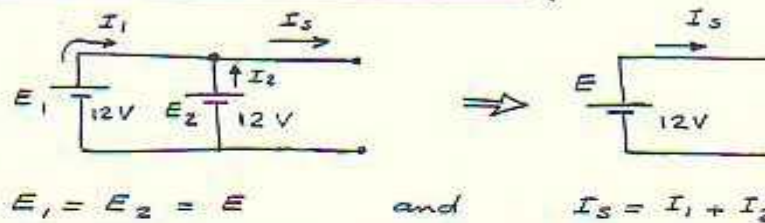

To increase the current rating of the source, two or more batteries in parallel of the same terminal voltage would be used.


2.3 Open and Short Circuits

Principle: We often need to apply the open and short circuits in the analysis of electric networks.

* Open Circuit

Open circuit : An open circuit is simply two isolated terminals not connected by an element of any kind.

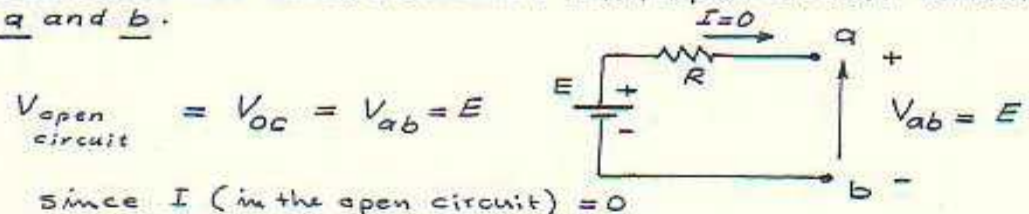Consider the circuit shown; with open circuit terminals a and b . $I=0$




In general

Open circuit : An open circuit CAN HAVE a potential difference (voltage) across its terminals but the current is always ZERO.

* Short Circuit

Short circuit: A short circuit is a direct connection of zero ohms across an element or combination of elements.

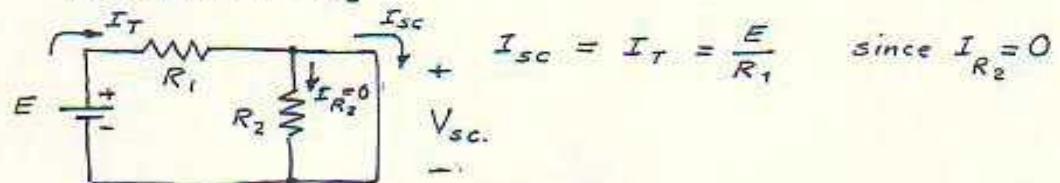Consider the circuit shown, with a short circuit across the resistor R_2



$$V_{short} = V_{sc} = 0$$


EE2

In general:

A short circuit CAN CARRY a current of any level but the potential difference (voltage) across its terminals is always ZERO.

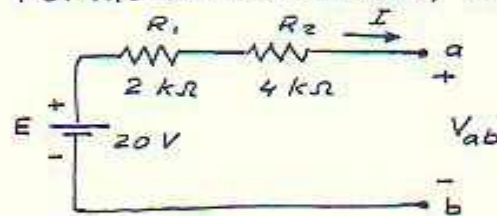Examples:

(a). For the network shown, determine V_{ab} .




Solution: - We have an open ckt across the terminal a and b, the

$$I = 0 \Rightarrow V_1 = 0 \text{ and } V_2 = 0$$

$$\text{- Applying KVL} \Rightarrow V_{ab} = E = 20V$$

(b). Calculate I and V for the network shown;

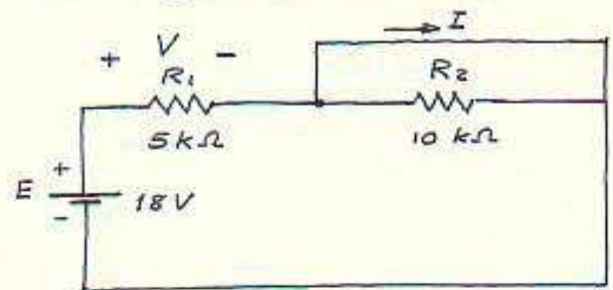Solution:


- We have a short ckt. across R_2

\Rightarrow No current through R_2

$$\Rightarrow I = \frac{E}{R_T} = \frac{E}{R_1 + 0} = \frac{18}{5k\Omega}$$

$$= \underline{3.6 \text{ mA}}$$

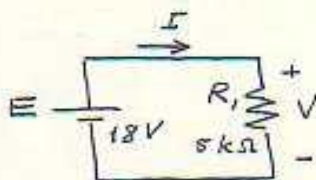Note: the ckt can be redrawn to be as shown



$$\therefore V = IR_1 = E = \underline{18V}$$

2.4 Source Transformation

EE2

It is often necessary or convenient to have a voltage source rather than a current source or a current source rather than a voltage source.

In the ckt. shown, we have a voltage source connected to a load resistance R_L

We have :


$$I_L = \frac{E}{R_T} = \frac{E}{R_S + R_L}$$

Multiplying the numerator by $(R_S/R_S = 1)$, we have :

$$I_L = \frac{(R_S/R_S) E}{R_S + R_L} = \frac{R_S (E/R_S)}{R_S + R_L}$$


$$I = \frac{E}{R_S}$$
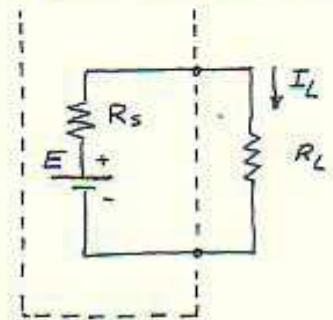
$$\therefore I_L = \frac{R_S \cdot I}{R_S + R_L}$$



Voltage Source


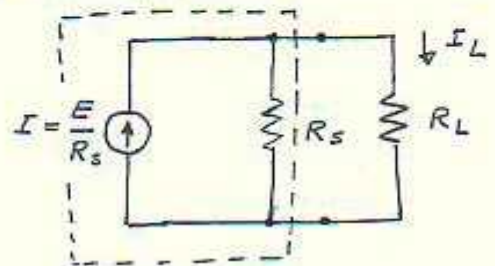
This is a current divider equation, which can be represented by the circuit below; which is the equivalent ckt. of the voltage source.



Current source

In general

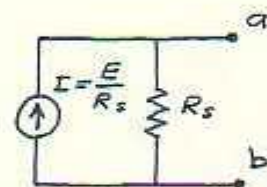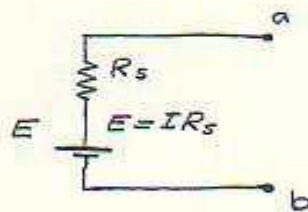A voltage source with voltage E and series resistor R_S can be replaced by a current source with a current I and parallel resistor R_S as shown :



← current to voltage source

voltage source to current source →

Example

Convert the voltage source, in the ckt below, to a current source, then calculate the current through the load for each source.

EE2

Solution

* For the voltage source ckt;



$$I_L = \frac{E}{R_s + R_L} = \frac{6}{2 + 4}$$

$$= \underline{1 \text{ A}}$$

* For the current source ckt;

$$I_L = \frac{I R_s}{R_s + R_L} = \frac{(3)(2)}{2 + 4}$$

$$= \underline{1 \text{ A}}$$

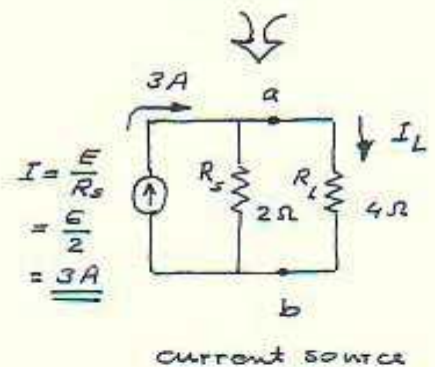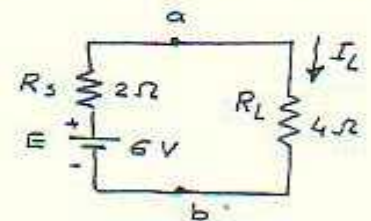

نفسه ان I_L متساوي في الطالين وهذا صحيح.

Example

Convert the current source, in the ckt. shown, to a voltage source and determine I_L for each source.

Solution

current divider rule \Rightarrow

* For the current source ckt;



$$I_L = \frac{I \cdot R_s}{R_s + R_L} = \frac{(9 \times 10^{-3})(3 \times 10^3)}{(3 + 6) \times 10^3}$$

$$= 3 \times 10^{-3} = \underline{3 \text{ mA}}$$

* For the voltage source ckt;

$$I_L = \frac{E}{R_s + R_L} = \frac{E}{(3 + 6) \times 10^3} = \frac{27}{9 \times 10^3}$$
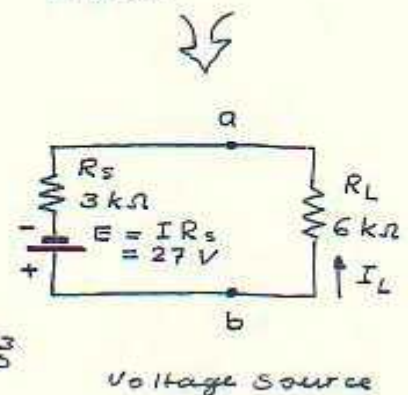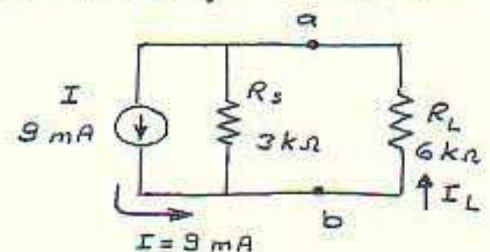
$$= 3 \times 10^{-3} = \underline{3 \text{ mA}}$$



2.3 Series-Parallel Circuits

EE2

Example

: For circuit shown,

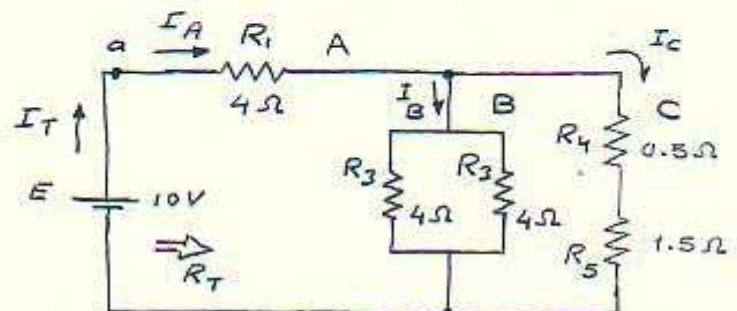


Fig (1)

Solution:

$$R_1 = R_A = 4\Omega$$

$$R_B = R_2 \parallel R_3 = \frac{R_N}{N} = \frac{4}{2} = 2\Omega$$

$$R_C = R_4 + R_5 = 0.5 + 1.5 = 2\Omega$$

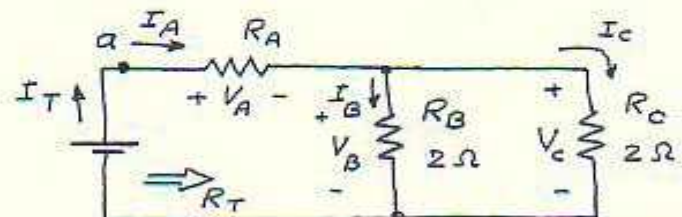


Fig (2)

$$R_{B \parallel C} = \frac{R_N}{N} = \frac{2}{2} = 1\Omega$$

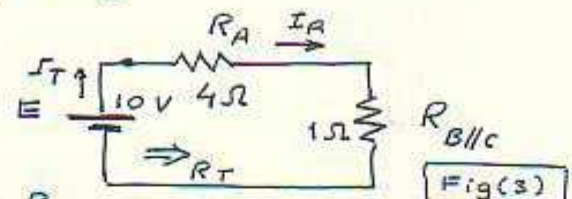


Fig (3)

From Fig. 3 $\Rightarrow \therefore R_T = R_A + R_{B \parallel C} = 4 + 1 = 5\Omega$

$\hookrightarrow \therefore I_T = \frac{E}{R_T} = \frac{10}{5} = 2\text{ A}$

From Fig (2) $I_B = I_C = \frac{I_A}{2} = \frac{2}{2} = 1\text{ A}$

From Fig (1) $\Rightarrow I_{R_4} = I_{R_5} = I_C = 1\text{ A}$

From fig (2) $\Rightarrow V_A = I_A R_A = (2)(4) = 8\text{ V}$

$V_B = I_B R_B = (1)(2) = 2\text{ V}$

$V_C = I_C R_C = (1)(2) = 2\text{ V}$


For check

KVL $\sum V = 0 \Rightarrow E - V_A - V_B = 0 \Rightarrow 10 = 8 + 2$
 $\therefore 10\text{ V} = 10\text{ V}$

Wye - Delta Transformation


EE2

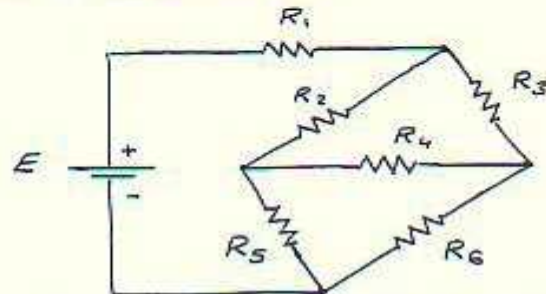: There are some cases often arises in circuit analysis, when the resistors are neither in parallel nor in series. For example, consider the circuit shown:




In this circuit, $R_1, R_2, R_3, \dots, R_6$ are neither in series nor in parallel.

* Wye (Y or star) connection

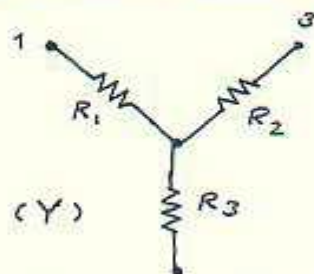

Y or star circuit connection


\Rightarrow
Equivalent

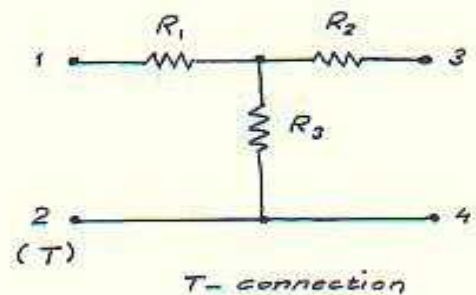


T-connection

Y and T connections

* Delta (Δ or π) circuit connection

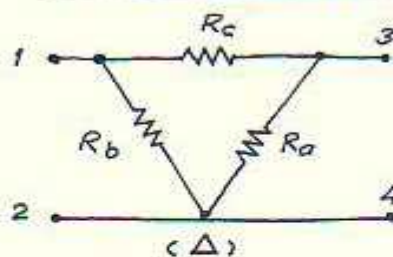Delta circuit connection & its equivalent π -connection

\Rightarrow

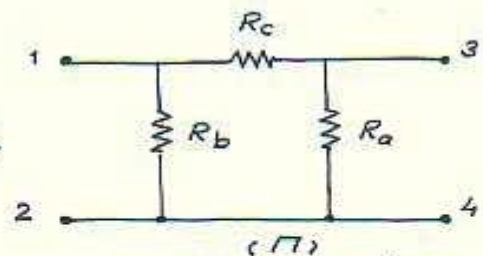 π -connection

Δ Y * Delta to Wye Transformation

EE2



- We have Δ and want to get its equivalent star circuit

- Consider the Δ circuit shown; to be transformed into its equivalent star shown below:

$$R_{12} = \frac{R_b (R_a + R_c)}{R_a + R_b + R_c}$$

$$R_{13} = \frac{R_c (R_a + R_b)}{R_a + R_b + R_c}$$
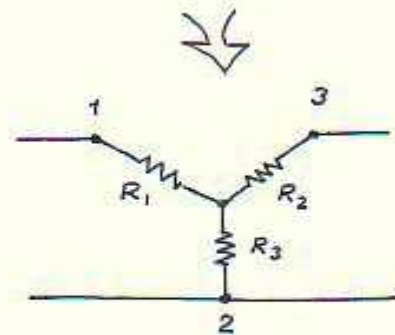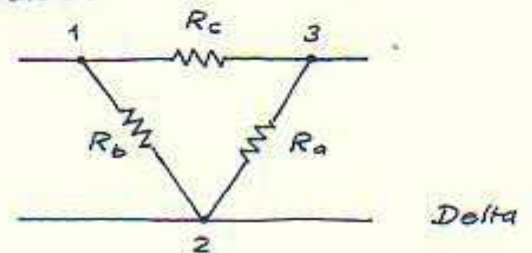
$$R_{23} = \frac{R_a (R_b + R_c)}{R_a + R_b + R_c}$$



$$R_{12} = R_1 + R_3$$

$$R_{13} = R_1 + R_2$$

$$R_{23} = R_2 + R_3$$

$$\therefore R_1 + R_3 = \frac{R_b (R_a + R_c)}{R_a + R_b + R_c} \quad \dots (1)$$

$$\text{and} \quad R_1 + R_2 = \frac{R_c (R_b + R_c)}{R_a + R_b + R_c} \quad \dots (2)$$

$$R_2 + R_3 = \frac{R_a (R_b + R_c)}{R_a + R_b + R_c} \quad \dots (3)$$

Subtraction Eq.(3) from Eq.(1) and adding the resulting equation to Eq.(1) results in:

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

Similarly;

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

and;

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

IN GENERAL

Each resistor in the Y network is the product of the resistors in the two adjacent Δ branches, divided by the sum of the three resistors

* Wye to Delta Transformation

- We have Y connected circuit and want to get its equivalent Δ .
- Consider the Y circuit shown, its equivalent Δ is shown below;

Using the previous sets of equations, then we have:

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

and

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

IN GENERAL

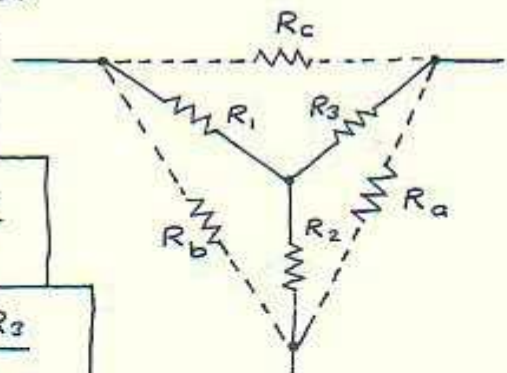Each resistor in the Δ network is the sum of all possible products of Y resistors taken two at a time, divided by the opposite Y resistor.



Notes

- * The Y and Δ networks are said to be balanced when:

$$R_1 = R_2 = R_3 = R_Y$$

and

$$R_a = R_b = R_c = R_\Delta$$

- * Under balance condition, the conversion equations become:


$$R_Y = \frac{R_\Delta}{3}$$

or

$$R_\Delta = 3R_Y$$

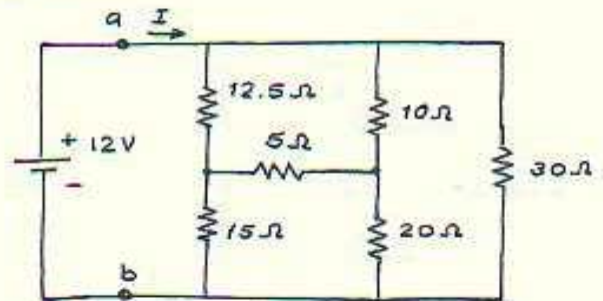Example

Obtain the equivalent resistance R_{ab} for the circuit shown and use it to find the current I



Solution

- * We can't use the relations of series connected or parallel connected resistors to obtain R_{ab} .
- * We try to use Δ -Y transformations or Y- Δ to get R_{ab} .


* If we transform the Y consisting of :

$$R_1 = 10\ \Omega$$

$$R_2 = 20\ \Omega$$

and $R_3 = 5\ \Omega$

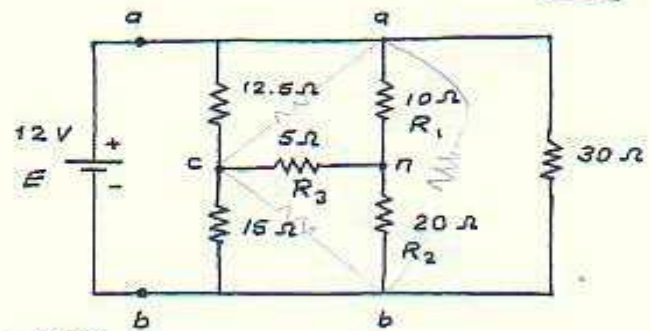\therefore the equivalent Δ circuit contains :



$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$= \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{10} = \frac{350}{10}$$

$$= 35\ \Omega$$

Similarly;

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2} = \frac{350}{20} = 17.5\ \Omega$$

and:

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3} = \frac{350}{5} = 70\ \Omega$$

$$\therefore R_{ab} = (7.3 + 10.5) \parallel 30$$



$$= \frac{17.8 \times 21}{17.8 + 21}$$

$$\Rightarrow R_{ab} = 9.632\ \Omega$$

$$\therefore I = \frac{E}{R_{eq}} = \frac{E}{R_{ab}}$$

$$= \frac{12}{9.632}$$

$$\Rightarrow I = 1.246\ \text{A}$$

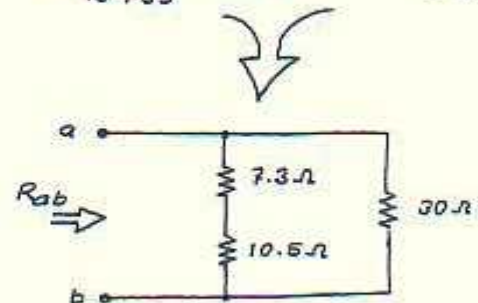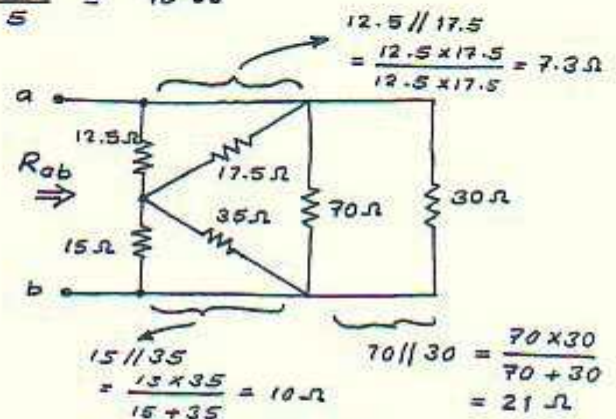

Tutorial Sheet No 2

TS2

ملاحظة: جميع أسئلة الكتاب والدولة المحولة فيه مطلوبة

Example 1

Three resistors are connected in series across a 12 V battery. The first resistor has a value of 1Ω , the second has a voltage drop of 4 V, and the third has a power dissipation of 12 W.

Calculate the value of the circuit current.

Solution

We have

$$P_3 = I^2 R_3 = 12 \text{ W} \quad \text{--- (1)}$$

and

$$V_2 = I R_2 = 4 \text{ V} \quad \text{--- (2)}$$


From (2)

$$\therefore I = \frac{4}{R_2}$$

From (1) & (2)

$$\left(\frac{4}{R_2}\right)^2 R_3 = 12$$

$$\therefore R_3 = \frac{3}{4} R_2^2$$

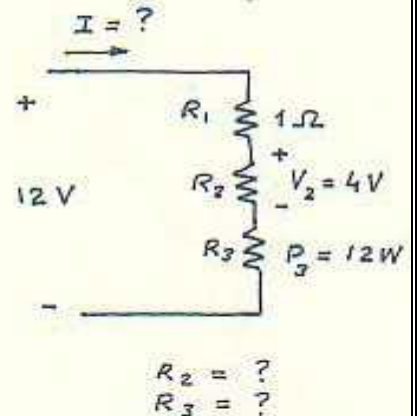

From the circuit shown, we have:

$$12 = I (R_1 + R_2 + R_3) = I (1 + R_2 + R_3)$$

Substituting for I and R_3 , we have:

$$12 = \frac{4}{R_2} \left(1 + R_2 + \frac{3}{4} R_2^2\right)$$

$$\therefore 3R_2^2 - 8R_2 + 4 = 0$$

$$\therefore R_2 = \frac{8 \pm \sqrt{64 - 48}}{6} = 2\Omega \text{ or } \frac{2}{3}\Omega$$

$$\therefore R_3 = \frac{3}{4} R_2^2 \Rightarrow R_3 = 3\Omega \text{ or } \frac{1}{3}\Omega$$


$$\therefore I = \frac{12}{R_1 + R_2 + R_3} = \frac{12}{1 + 2 + 3} = 2 \text{ A}$$

or

$$I = \frac{12}{1 + \left(\frac{2}{3}\right) + \left(\frac{1}{3}\right)} = 6 \text{ A}$$

Practice Problem

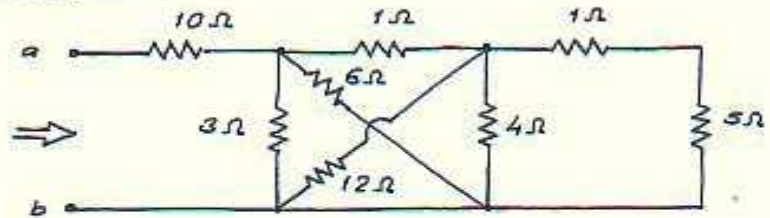_____ : Calculate the equivalent resistance R_{ab} in the circuit shown.




Answer

_____ : $R_{ab} = 11.2 \Omega$

Practice Problem

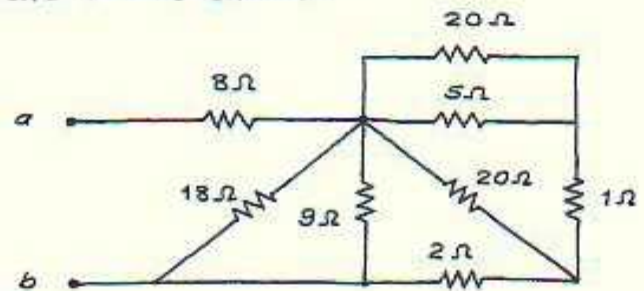_____ : Find R_{ab} for the circuit shown:



Answer

_____ : $R_{ab} = 11 \Omega$

Practice Problem


_____ : Find V_1 and V_2 in the circuit shown. Also calculate I_1 and I_2 and the power dissipated in the 12Ω and 40Ω resistors.

Answer

_____ : $V_1 = 5V$, $V_2 = 10V$


$I_1 = 416.7 \text{ mA}$, $I_2 = 250 \text{ mA}$

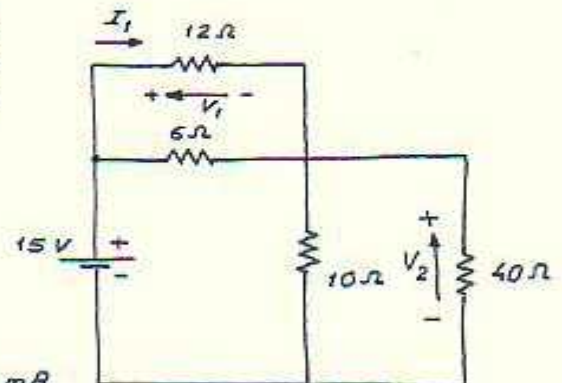$P_1 = 2.083 \text{ W}$, $P_2 = 2.5 \text{ W}$



Practice Problem

: Find the currents and voltages in the circuit shown, using Kirchhoff's laws.

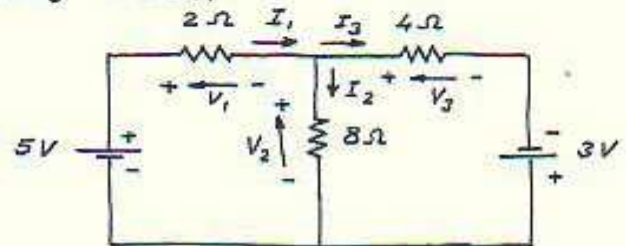
Answer

: $V_1 = 3V$, $V_2 = 2V$, $V_3 = 5V$

$I_1 = 1.5A$, $I_2 = 0.25A$, $I_3 = 1.25A$


Example

: Find R_{eq} for the circuit shown.

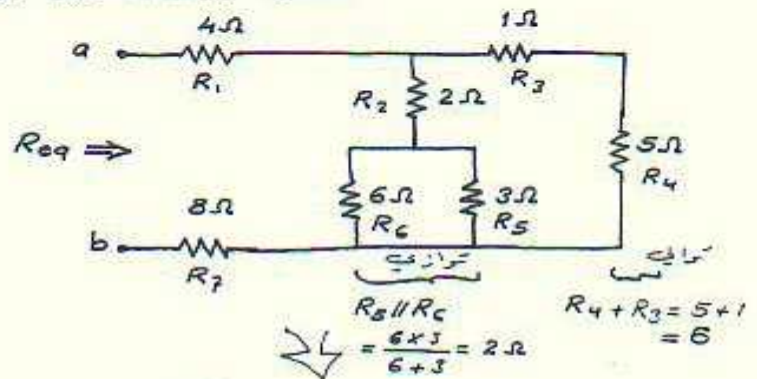Solution

$$\therefore R_{eq} = R_{ab} = 4 + 2.4 + 8$$


$$= \underline{14.4 \Omega}$$

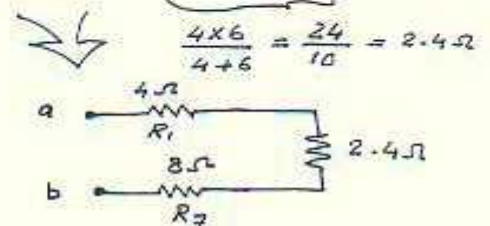

Example

TS2

: What is the value of the unknown resistor R in the circuit shown, if the voltage drop across the $500\ \Omega$ resistor is 2.5 V ? All resistors are in Ohms.

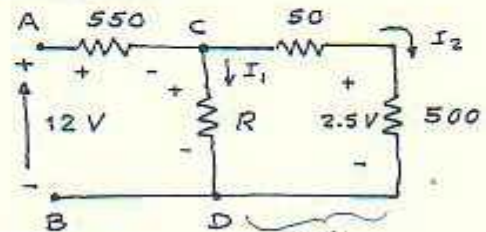Solution

Using the voltage divider rule;

* The voltage drop across the $50\ \Omega$ resistor is:

$$V_{50\ \Omega} = 2.5 \times \frac{50}{500} \\ = 0.25\text{ V}$$

$$\therefore V_{CD} = 2.5 + 0.25 \\ = 2.75\text{ V}$$



$$* V_{550\ \Omega} = 12 - V_{CD} \\ = 12 - 2.75 = 9.25\text{ V}$$

$$\therefore I_T = \frac{V_{550\ \Omega}}{550} = \frac{9.25}{550} = 0.0168\text{ A}$$

$$I_2 = \frac{V_{500}}{500} = \frac{2.5}{500} = 0.005\text{ A}$$

$$\therefore I_1 = I_T - I_2 = 0.0168 - 0.005 = 0.0118\text{ A}$$

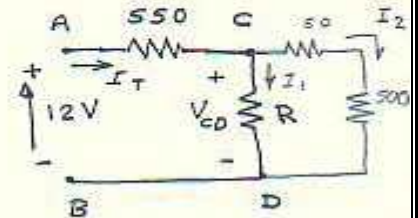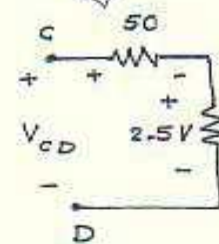
$$\therefore R = \frac{V_{CD}}{I_1} = \frac{2.75}{0.0118} = 233\ \Omega$$



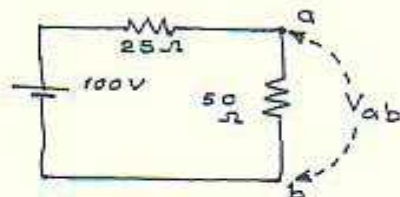
Example

TS2


: For the networks shown, find V_{ab} (with polarity).




(a)

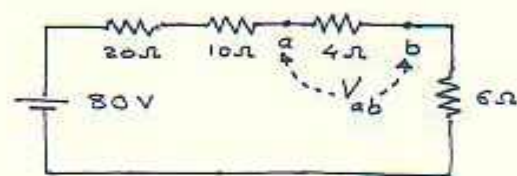

(b)

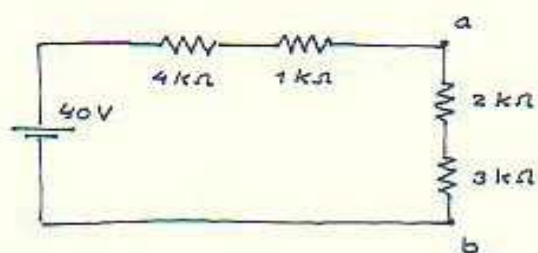


(c)

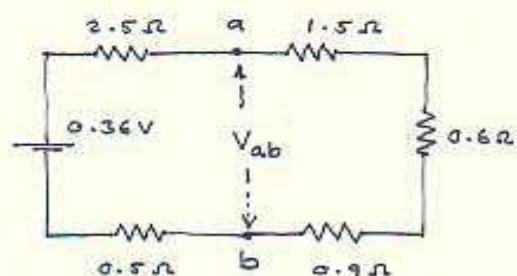

Solution


: (a). Using the voltage divider rule; then
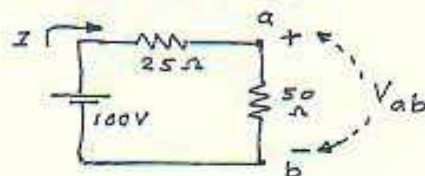
$$\therefore V_{ab} = 100 \cdot \frac{50}{25+50} = 66.67 \text{ V}$$




(b). Using the voltage divider rule, then:
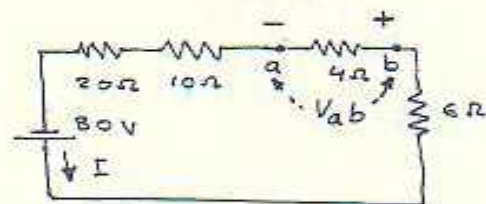
$$\therefore V_{ab} = 80 \cdot \frac{4}{20+10+4+6} = 8 \text{ V}$$



(c). Using the voltage divider rule, then:
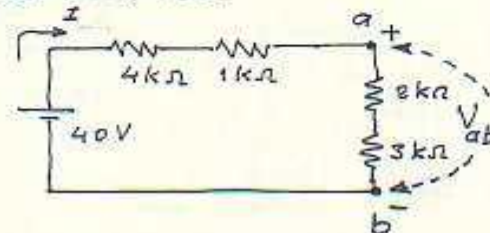
$$V_{ab} = \frac{(2+3) \times 10^3}{(4+1+2+3) \times 10^3} \times 40 = 20 \text{ V}$$




(d). Using the voltage divider rule, then;

TS2


$$V_{ab} = 0.36 \frac{(1.5 + 0.6 + 0.9)}{2.5 + 1.5 + 0.6 + 0.9 + 0.5}$$

$$= 0.18 \text{ V}$$

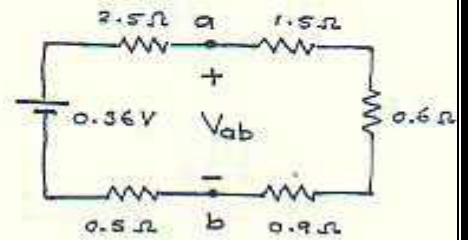

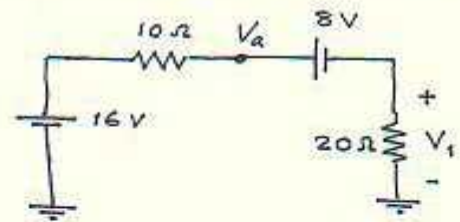Example

: Determine the voltage V_a and V_1 , for the network shown.



Solution

: Redraw the circuit to be as shown;

using KVL

$$V_a = 8 + V_1$$

$$= 8 + I(20)$$


$$I = ?$$

$$I = \frac{16 - 8}{20 + 10}$$

$$= \frac{8}{30}$$

$$\therefore V_a = 8 + \frac{8}{30}(20) = 8 + \frac{16}{3} = \frac{40}{3} \text{ V}$$

$$= 13.33 \text{ V}$$

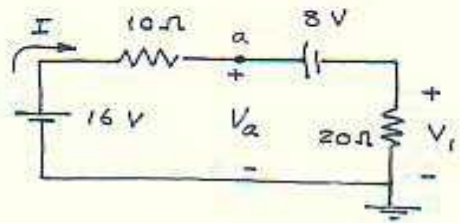

OR

using KVL


$$16 = I(10) + V_a \Rightarrow 16 = \frac{8}{30}(10) + V_a$$

$$\therefore V_a = 16 - \frac{8}{3} = \frac{40}{3} = 13.33 \text{ V}$$


$$V_1 = I(20) = \frac{8}{3}(20) = \frac{16}{3} = 5.33 \text{ V}$$

Example

TS2

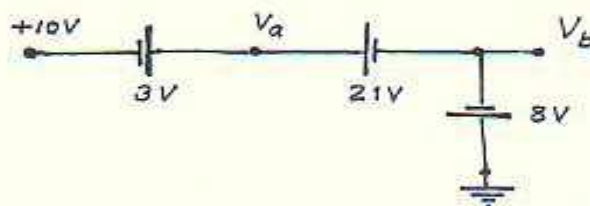: Determine the voltage V_{ab} for the network shown;Solution

: Redraw the ckt. to be as shown;

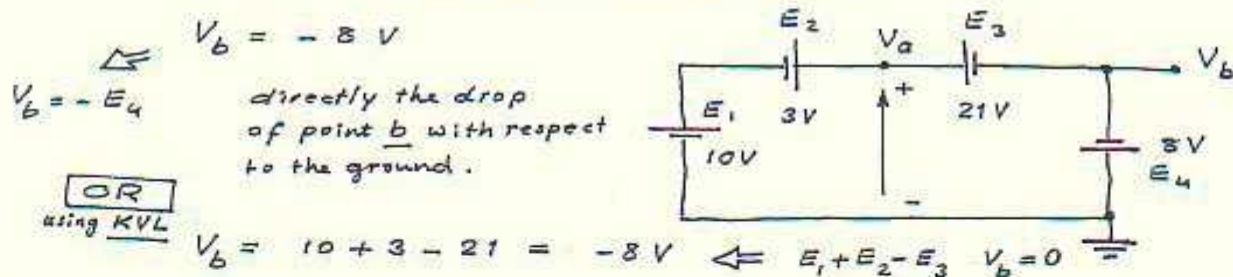


KVL

$$V_a = 10 + 3 = 13 \text{ V} \quad \leftarrow E_1 + E_2 - V_a = 0$$

$$\therefore V_{ab} = V_a - V_b \\ = 13 - (-8) = 21 \text{ V}$$

$$\begin{aligned} \text{OR } V_a - E_3 + E_4 &= 0 \\ \therefore V_a &= E_3 - E_4 \\ &= 21 - 8 = 13 \text{ V} \end{aligned}$$

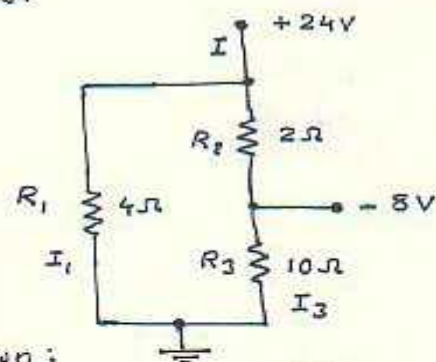Example: For the network shown, find the currents I_1 , I_2 , and I_3 and indicate their directions.Solution


: Redraw the ckt to be as shown;

$$I_3 = \frac{V_b}{R_3} = \frac{-8}{10} = -0.8 \text{ A}$$

$$I_1 = \frac{V_a}{R_2} = \frac{24}{4} = 6 \text{ A}$$


$$I_2 = \frac{V_a - V_b}{R_2} = \frac{24 + 8}{2} = 16 \text{ A}$$
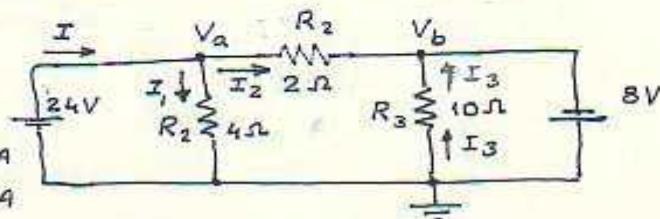
$$I = I_1 + I_2 = 6 + 16 = 24 \text{ A}$$



Example

TS2: For the network shown, determine the voltages V_1 , V_2 and the current I .

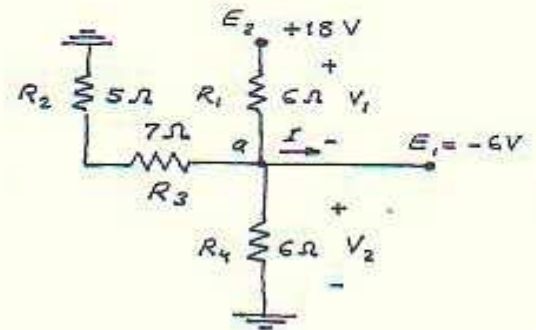Solution

Redraw the network to be as shown;

$$V_2 = -E_1 = -6V$$

Applying KVL, we have;

$$-E_1 + V_1 - E_2 = 0$$

$$\therefore V_1 = E_1 + E_2 = 18 + 6$$


$$= 24V$$

Applying KCL, then:

$$I = I_1 + I_2 + I_3$$

$$\therefore I = 4 + 1 + 0.5$$

$$= \underline{5.5A}$$

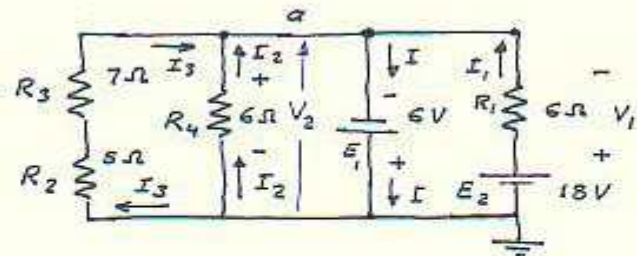


$$I_1 = \frac{V_1}{R_1} = \frac{24}{6} = 4A$$

$$I_2 = \frac{V_2}{R_4} = \frac{6}{6} = 1A$$


$$I_3 = \frac{E_1}{R_1 + R_3} = \frac{6}{7+5} = 0.5A$$

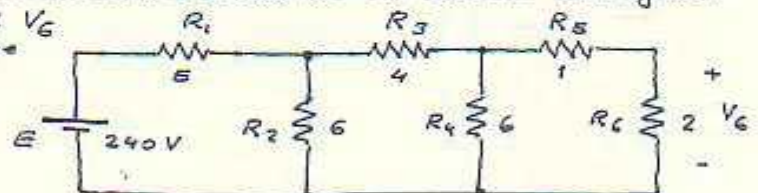Example

For the network shown, determine all current through all branches, and V_G . All resistors are in Ohms.






Solution:

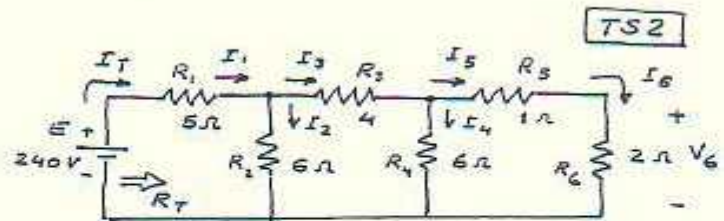

$$I_T = \frac{E}{R_T}$$

$$\Rightarrow R_T = ?$$

Find R_T

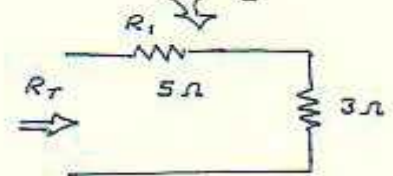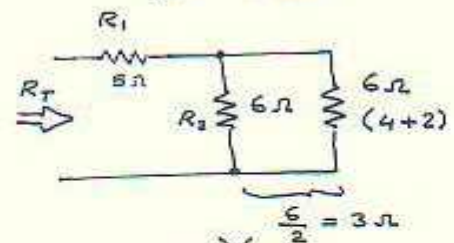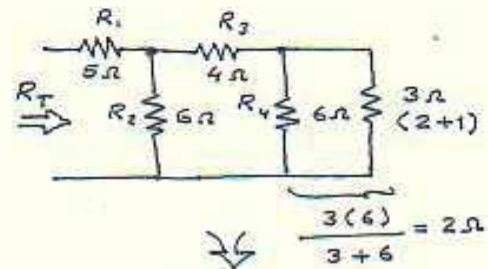


$$\therefore R_T = 5 + 3 = \underline{8\Omega}$$

$$\therefore I_T = \frac{240}{8} = \underline{30\text{ A}}$$

$$I_1 = I_T = 30\text{ A}$$
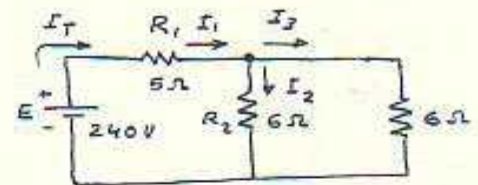
$$I_3 = \frac{I_T}{2} = \frac{30}{2} = \underline{15\text{ A}}$$




Using the current division rule;

$$I_C = I_3 \frac{6}{3+6}$$

$$= 10\text{ A}$$

$$\therefore V_6 = I_C R_6 = (10)(2)$$

$$= \underline{20\text{ V}}$$

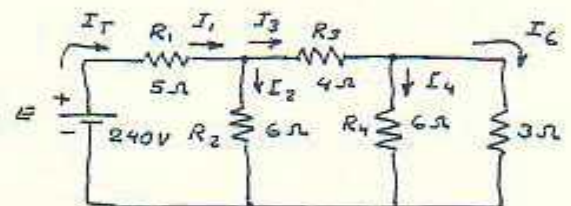

$$I_1 = I_2 + I_3 \Rightarrow I_2 = I_1 - I_3 = 30 - 15 = 15\text{ A}$$

$$I_3 = I_4 + I_6 \Rightarrow I_4 = I_3 - I_6 = 15 - 10 = 5\text{ A}$$


$$I_5 = I_6 = 10\text{ A}$$

Example

TS2





For the network shown;

- (a) Determine the currents I_T , I_1 , I_3 and I_4 .
 (b) Calculate V_a and V_{bc} .

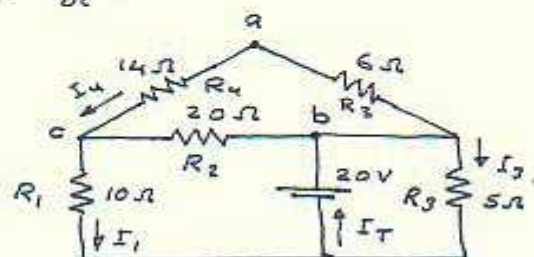Solution

Redraw the circuit to be as shown,
 we notice that the circuit consists of only
 series - parallel combination.
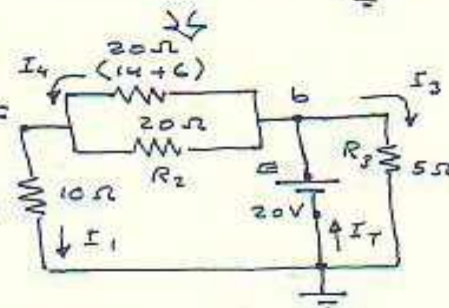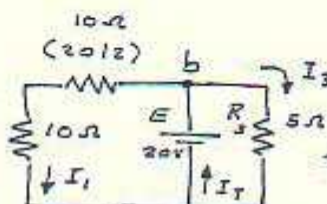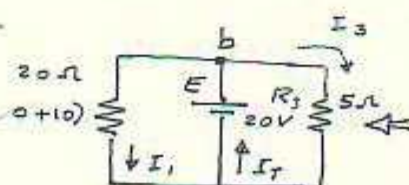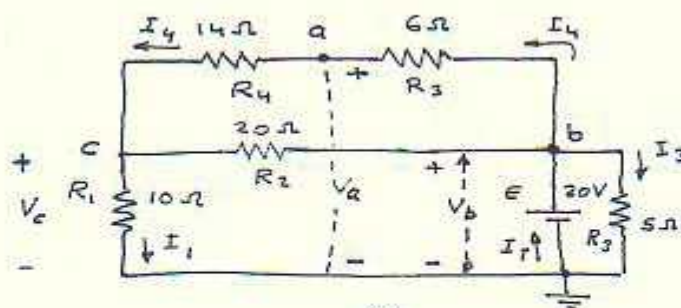
$$I_T = \frac{E}{R_T} \Rightarrow R_T = ?$$



$$\therefore R_T = \frac{20(5)}{20+5} = 4 \Omega$$

$$I_T = \frac{20}{4} = 5 A$$

$$I_1 = \frac{E}{20} = \frac{20}{20} = 1 A$$

$$I_3 = \frac{E}{5} = \frac{20}{5} = 4 A$$

$$I_4 = \frac{I_1}{2} = \frac{1}{2} = 0.5 A$$

$$V_b = 20 V$$

$$V_a = ? \quad \text{Applying KVL}$$

$$V_a = I_4 R_4 + I_1 R_1 = 0.5(14) + 1(10) = 17 V$$

$$\text{OR } V_a = V_b - I_4 R_6 = 20 - (0.5)(6) = 17 V$$


$$V_c = I_1 R_1 = (1)(10) = 10 V$$

$$\therefore V_{bc} = V_b - V_c = 20 - 10 = 10 V$$

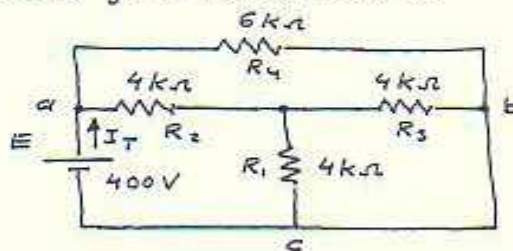Example

TS2

For the circuit shown, find the current I .



Solution

- There is no series or parallel circuit elements to be simplified.



- Convert the star labeled (abc) to a delta

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$\text{since } R_1 = R_2 = R_3 = 4k\Omega$$

$$\therefore R_A = 3R_1 = 3(4k\Omega) = 12k\Omega$$
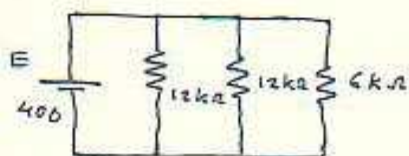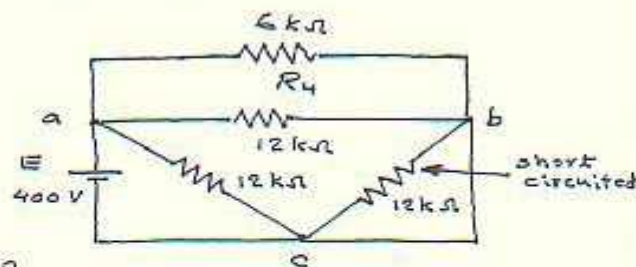
$$\text{and } R_A = R_B = R_C = 12k\Omega$$



$$\therefore R_T = 12k\Omega // 12k\Omega // 6k\Omega$$

$$\begin{array}{c} \underbrace{\hspace{1.5cm}} \\ 6k\Omega \\ \underbrace{\hspace{1.5cm}} \\ 3k\Omega \end{array}$$


$$\therefore R_T = 3k\Omega$$

$$\therefore I_T = \frac{E}{R_T} = \frac{400}{3 \times 10^3} = 133.33 \text{ mA}$$


Example

_____ : For the circuit shown, calculate I and V .

T52

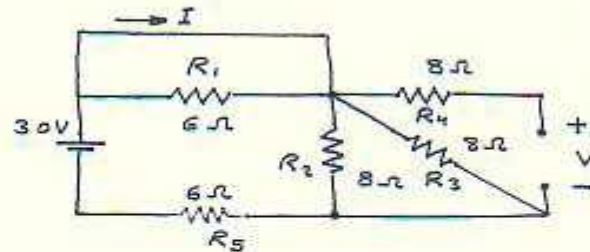Solution

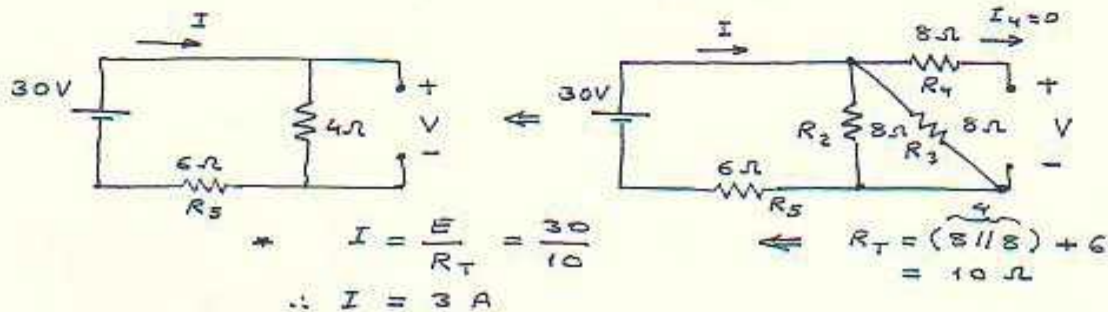
- Because of the short circuit ($R_1 = 6\Omega$) is cancelled.
- Because of the open circuit, the current in R_4 is zero.
- The circuit will be as shown.



$\therefore \text{ and } V = IR_2 = 3(4)$
 $= 12\text{ V}$

Practice Problem

_____ : For the bridge network shown, find R_{ab} and I .

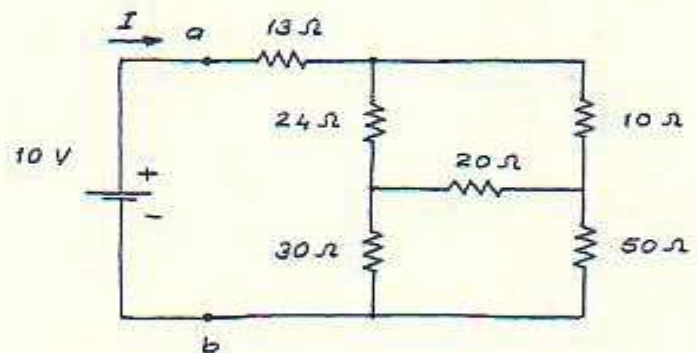Answer


$R_{ab} = 40\Omega$

$I = 0.25\text{ A}$

Example

T52

For the network shown;

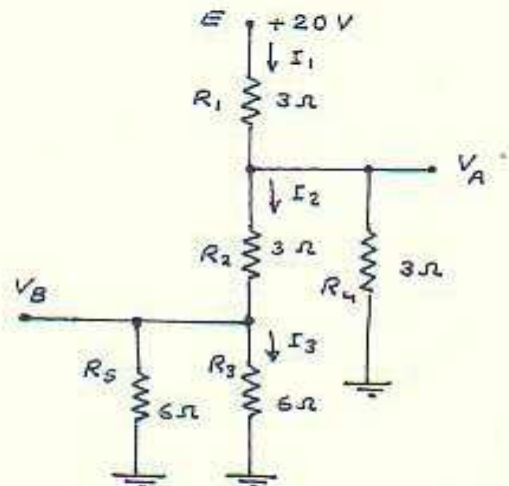(a). Calculate the values of I_1 , I_2 and I_3 .(b) Determine V_A and V_B .Solution

Redraw the circuit to be as shown below;

$$(a). \quad I_1 = \frac{E}{R_T}$$

$$R_T = 3 + 2 = 5\Omega$$

$$\therefore I_1 = \frac{20}{5} = 4\text{ A}$$

Using Current Division rule $I_2 = I_1 \cdot \frac{3}{3+6} = 4 \cdot \frac{3}{3+6}$

$$\therefore I_2 = 1.333\text{ A}$$



$$I_3 = \frac{I_2}{2} = \frac{1.333}{2} = 0.6665\text{ A}$$

$$(b). \quad V_A = I_4 R_4$$

$$\begin{aligned} I_4 &= I_1 - I_2 \\ &= 4 - 1.333 \\ &= 2.667\text{ A} \end{aligned}$$

$$\therefore V_A = (2.667)(3) = 8\text{ V}$$
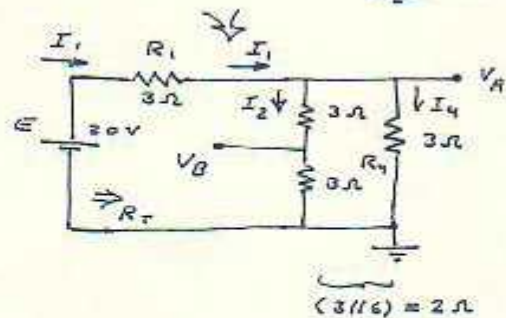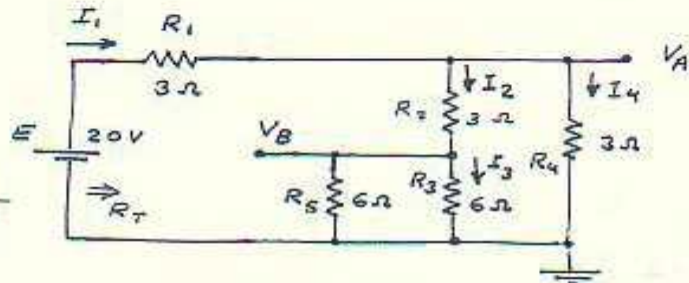
$$\begin{aligned} V_B &= I_3 R_3 = (0.6665)(6) \\ &= 4\text{ V} \end{aligned}$$



$$(3/16) = 2\Omega$$