



Ministry of Higher Education & Scientific Research

University of Technology

Communication Eng. Department

2<sup>nd</sup> Semester - Final Examination (2016/2017)

Subject: Fund.Elect.Eng.II

Date: / / 2017

Division: (Wireless) & (Optical) Comm. Eng.

Time: 3Hrs

Year: First

Examiner: Hussain A. Hammas


Number of pages: 2




29 MAY 2017

**Attempt Five Questions Only**  
**ALL Questions Carry Equal Marks**

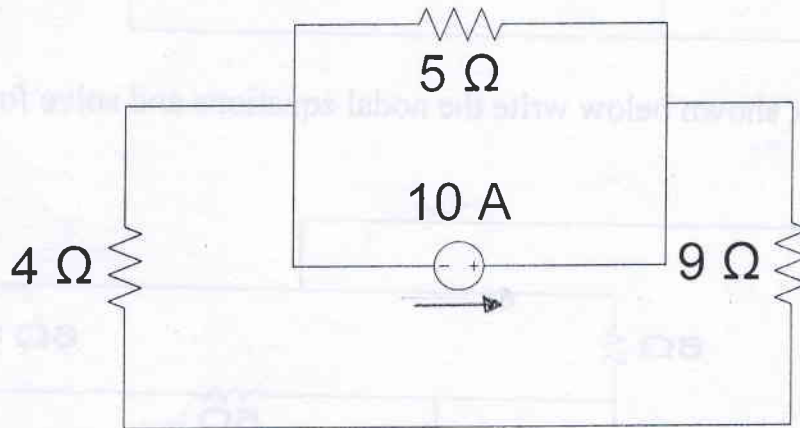**Q1:** Using Norton theorem to find the current through the  $9\Omega$  resistor in the circuit shown.



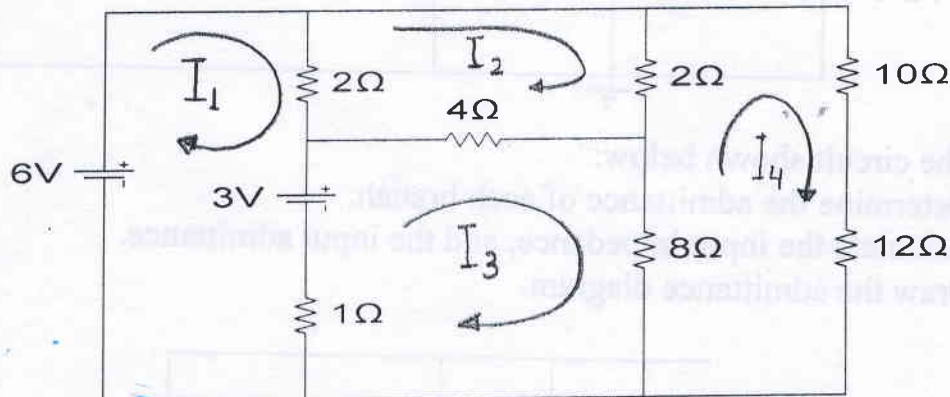**Q2:** Use the loop current analysis to determine the currents  $I_1$ ,  $I_2$ ,  $I_3$  and  $I_4$  in the circuit Shown.




**Q3: a)** Draw the non- interlinked 3-phase six wire system.


**b)** An RLC circuit consists of a series resistance of  $1K\Omega$ , an inductance of  $100mH$ , and a capacitor of  $10 Pf$ . If a voltage of  $100V$  is applied across the combination, find the half power points and the HPBW of the resonance frequency response.

اقلب الورقة

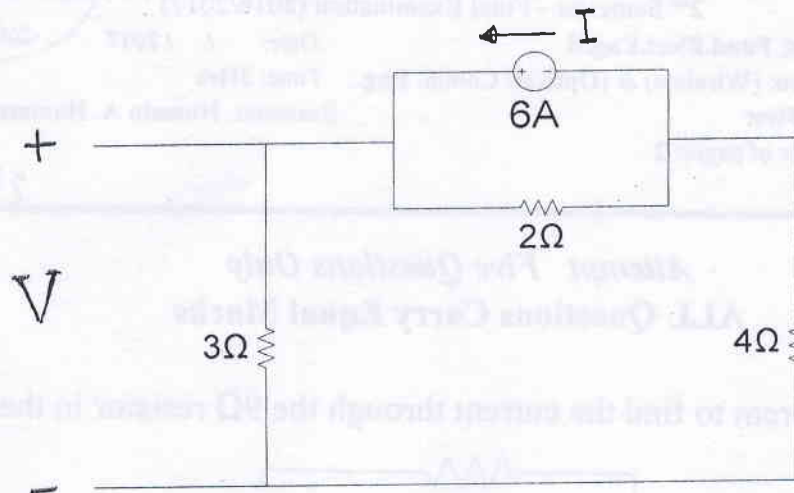**Q4:** For the circuit shown, determine the voltage  $V$  is the reciprocity theorem satisfied?



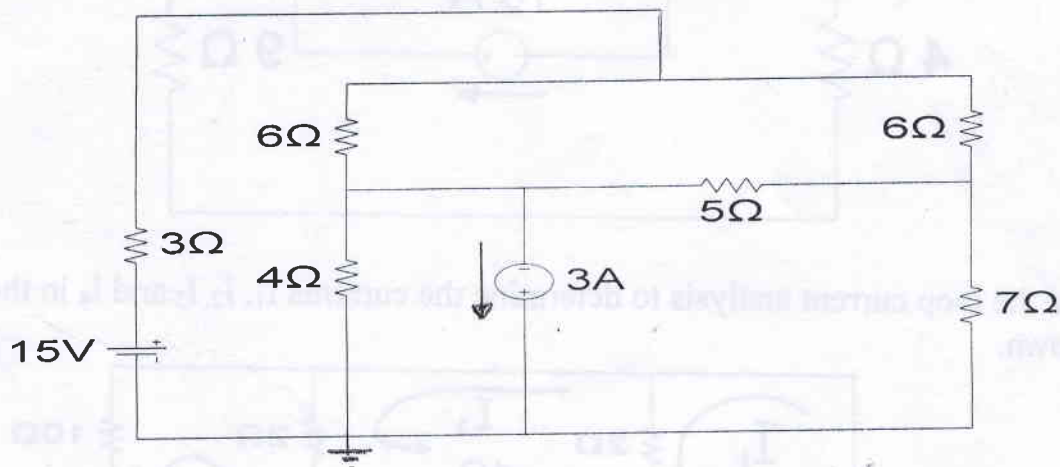**Q5:** For the network shown below write the nodal equations and solve for the nodal Voltages.



**Q6:** For the circuit shown below:

- Determine the admittance of each branch.
- Calculate the input impedance, and the input admittance.
- Draw the admittance diagram.

